

IIIT BANGALORE

VLS 502

Analog CMOS VLSI Design

Project Report

Submitted By:-

Bibin B Jacob- MT2024513

Utkarsh Jain- MT2024538

Vaibhav Naresh Dachewar- MT2024539

Submitted To:-

Prof. Sakshi Arora

Assistant Professor,
VLSI Lab,

International Institute of Information Technology - Bangalore

Externally compensated LDO

1. Specifications

In this project we have designed an LDO subject to different conditions. For this design we are designing the LDO for both externally and internally compensated LDO. For the below figure we are considering 45nm technology node. Our aim is to design the LDO for a max and a min load condition.

Table 1: Specifications Summary

| Parameter | Value |
|--------------------|-------|
| Vin | 1.4V |
| Vout | 1V |
| PSRR | 60dB |
| Iload (min) | 2mA |
| Iload (max) | 10mA |
| Cload | 1uF |
| Iquiescent | 50uA |
| Transient duration | 1u |

2. Purpose of an LDO

Low Drop-Out (LDO) regulators are critical components in Very Large Scale Integration (VLSI) circuits, where the demand for stable power supply is paramount due to the increasing complexity and sensitivity of integrated circuits. In VLSI applications, LDOs help maintain consistent voltage levels, which is essential for the reliable operation of digital, analog, and mixed-signal components within a chip.

Key Purposes of an LDO

- **Voltage Regulation:** Maintains a stable output voltage despite variations in input voltage or load current, ensuring consistent operation of sensitive electronic components.
- **Low Noise Power Supply:** Provides clean, low-ripple power, which is essential for noise-sensitive applications such as RF circuits, audio devices, and ADCs/DACs.
- **Load Current Stability:** Supports a range of load currents while maintaining stability, which is vital in circuits with dynamic power requirements.
- **Protection for Downstream Components:** Safeguards sensitive downstream components from voltage fluctuations and overvoltage conditions.
- **Power Efficiency at Low Dropout:** Operates efficiently when the difference between input and output voltage is minimal, reducing energy loss compared to traditional linear regulators.

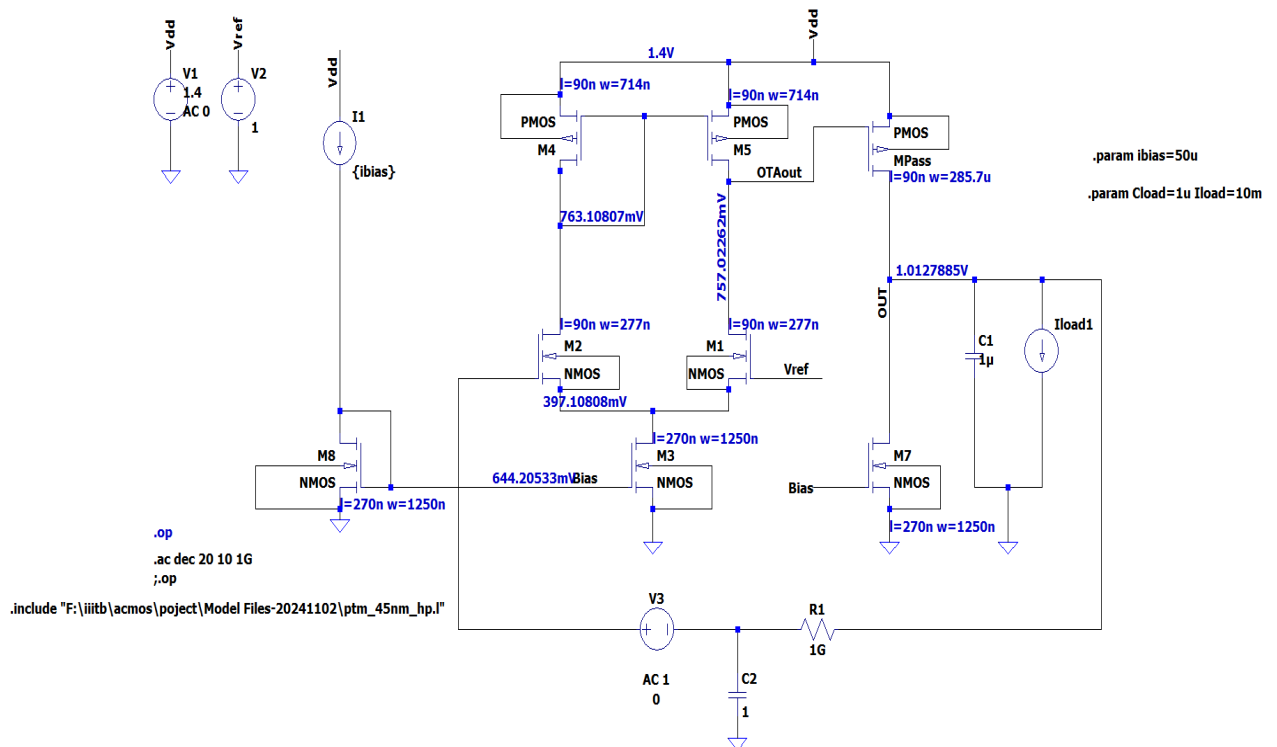


Figure 1: LDO schematic

3. Relevance of Techplots

We include all techplots generated.

- **Github Link:** <https://github.com/BibinBJacob/AnalogProject>
Technology node : 45 nm
- f_T improves with shorter channel lengths, making circuits faster with scaling.
- Compared to 180 nm the FOMs
- We chose the V_{ds} to be 0.4 mV, and we expect that to result in some error because the V_{ds} across every MOSFET might not be the same after sizing the circuit under a particular load. It is very possible that the V_{ds} across the MOSFETs can change under different values of load current. The above phenomenon can be understood from the output log files mentioned below.

NMOS Techplots

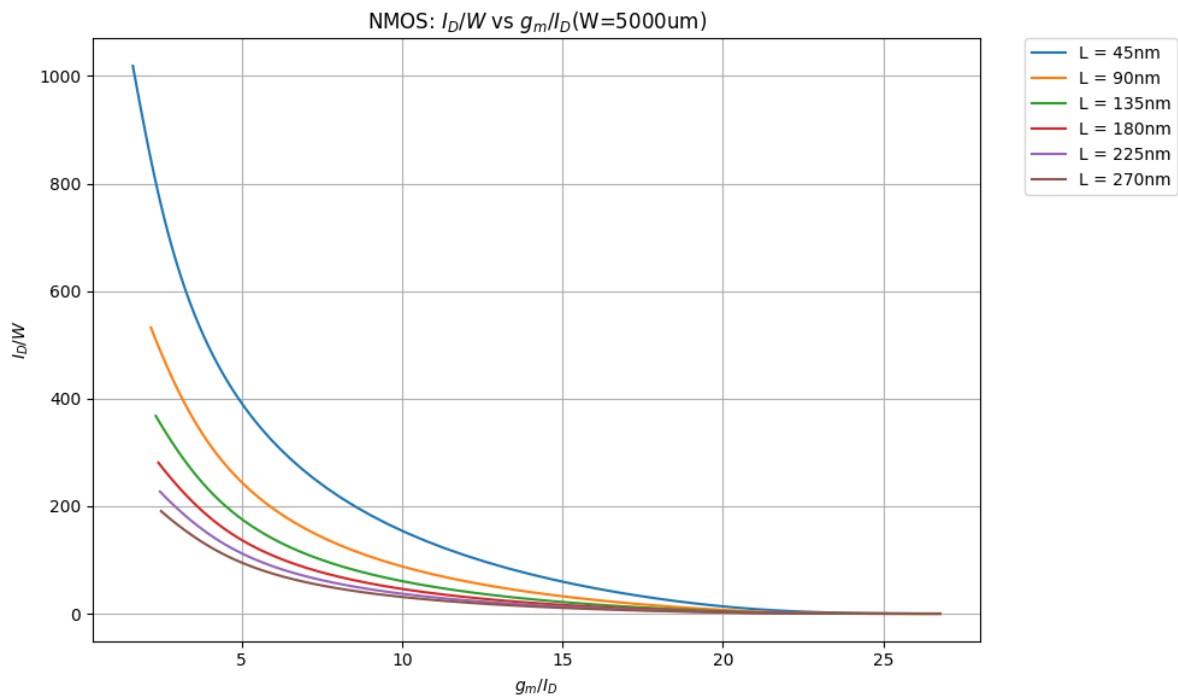


Figure 2: I_D/W vs g_m/I_D

 


Figure 3: gmro vs gm/Id

 


Figure 4: fT vs gm/Id

PMOS Techplots

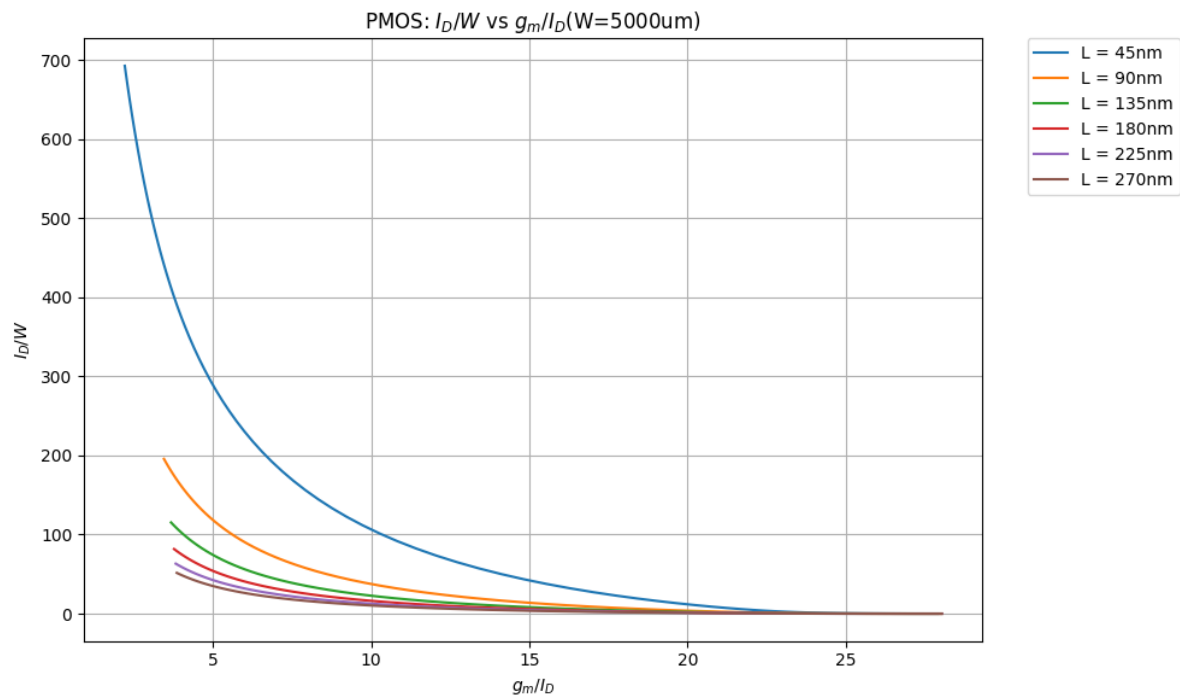


Figure 5: I_D/W vs g_m/I_D

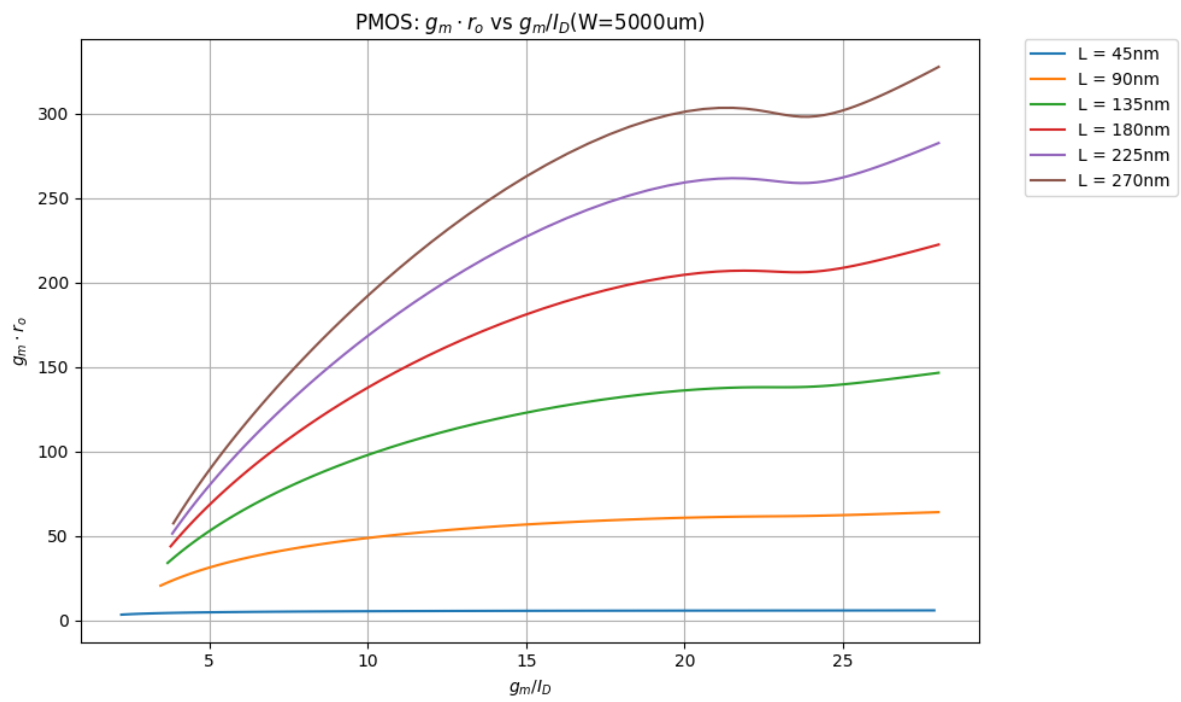


Figure 6: gmro vs gm/Id

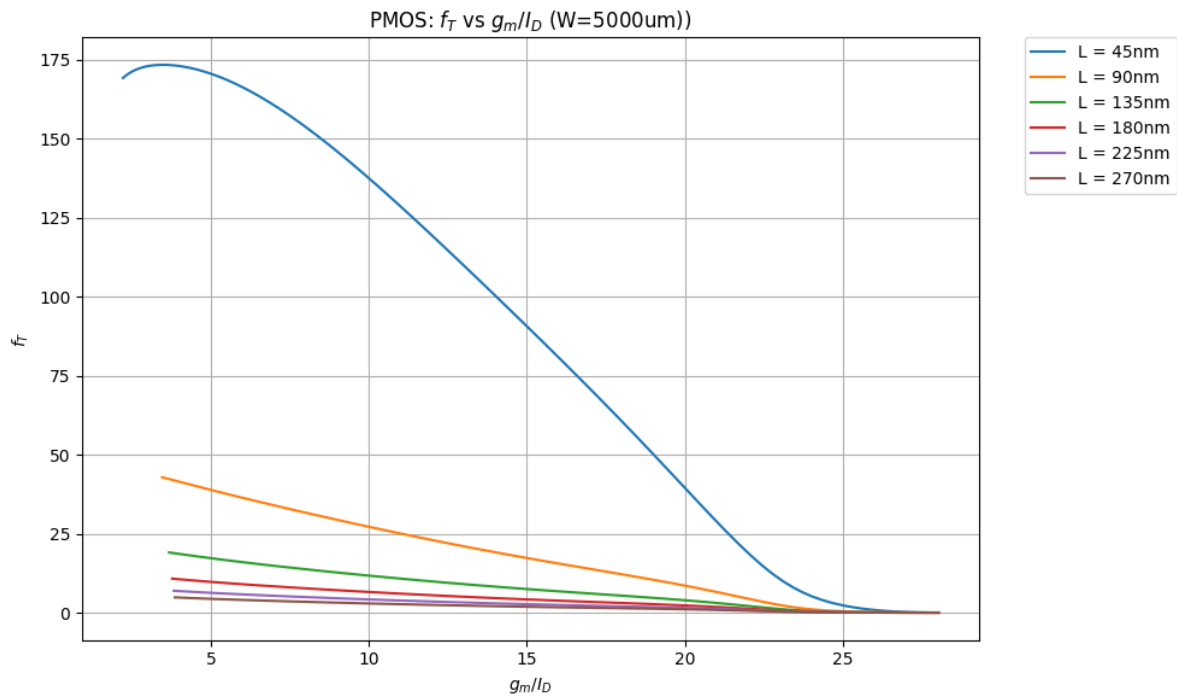
Figure 7: f_T vs g_m/I_D

Table 2: Key Differences Between 180nm and 45nm Technology Nodes for NMOS

| Parameter | 180nm Technology Node | 45nm Technology Node |
|---------------------------|-----------------------|----------------------|
| gmro | 20 | 7 |
| I_d/W ($\mu A/\mu m$) | 28 | 154 |
| f_T (Hz) | 1.6×10^{10} | 19×10^{10} |

Table 3: Observations on Technology Scaling Effects

| Parameter | Observation |
|-----------|--|
| gmro | As the channel length decreases, the output resistance (r_o) decreases significantly, which dominates the intrinsic gain ($gmro$). As a result, the overall value of $gmro$ decreases. |
| I_d/W | With reduced channel length, the drain current (I_d) increases due to higher mobility and lower channel resistance. Consequently, I_d/W increases, which is evident from the data. |
| f_T | A decrease in channel length increases the transconductance (g_m), which directly leads to an increase in the unity-gain cutoff frequency (f_T). This trend is observed in the values. |

4. FET Sizes

We Provide the sizes of the passFET, differential amplifier, and mirror transistors. here we also Include small-signal parameters and figures of merit (FOMs). Discuss loop gain under heavy and light load conditions.

Table 4: FET Sizes and Parameters

| Transistor | Size (W/L) | g_m/I_d | $g_m * r_o$ | I_d/W | f_t |
|---------------------|----------------|-----------|-------------|---------|--------|
| PassFET pmos | 285.7u/90n | 10 | 50 | 35 | 28 GHz |
| Diff-Amp pmos | 714n/90n | 10 | 40 | 35 | 28 GHz |
| Diff-Amp nmos | 277.7n/90n | 10 | 40 | 90 | 60 GHz |
| Current Mirror nmos | 1250n/270n | 10 | 154.1 | 40 | 10 GHz |

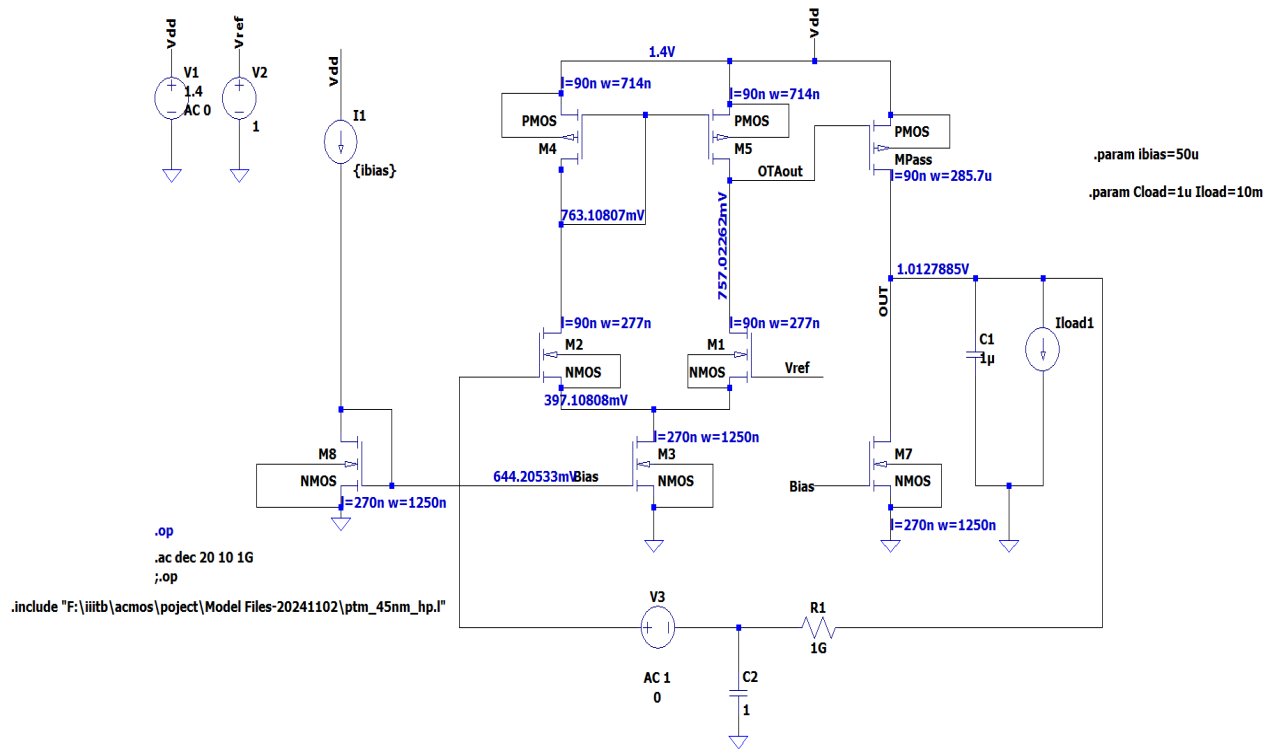


Figure 8: FET sizes and characteristics.

5. Stability Analysis

For Heavy load we get the following curve:

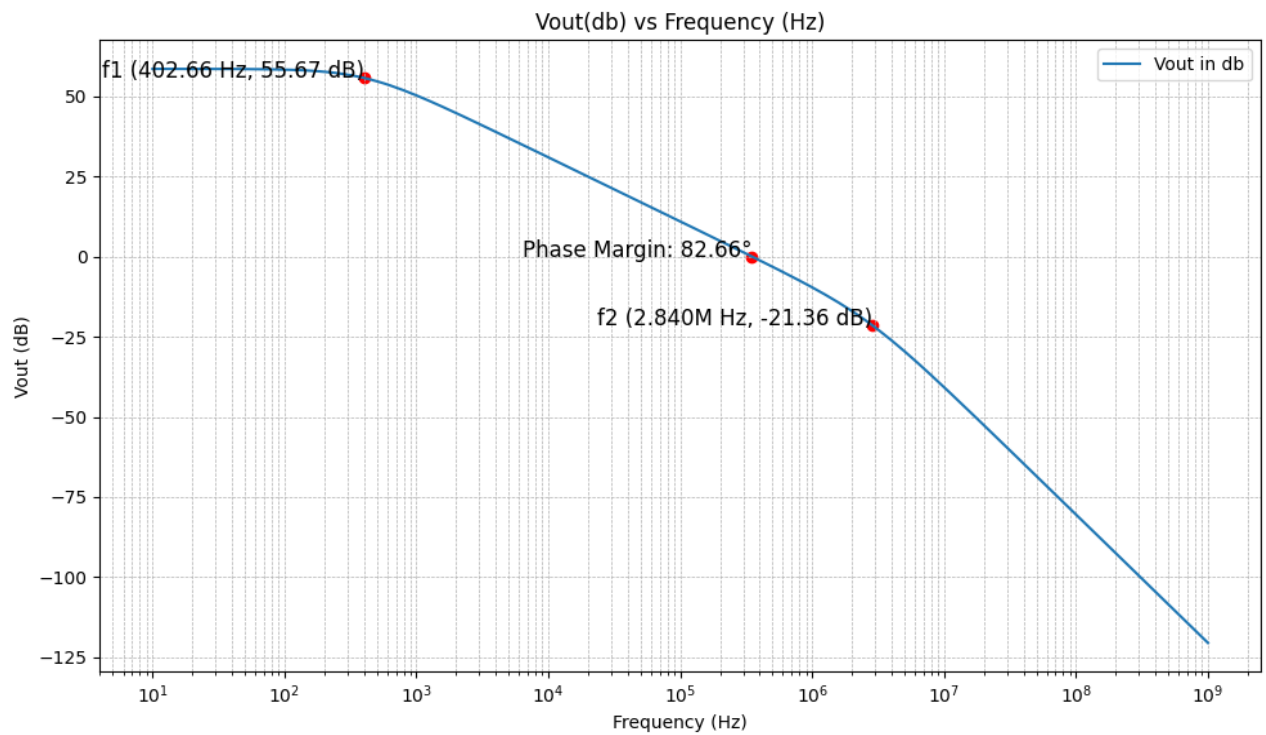


Figure 9: Pole location

For Light load we get the following curve

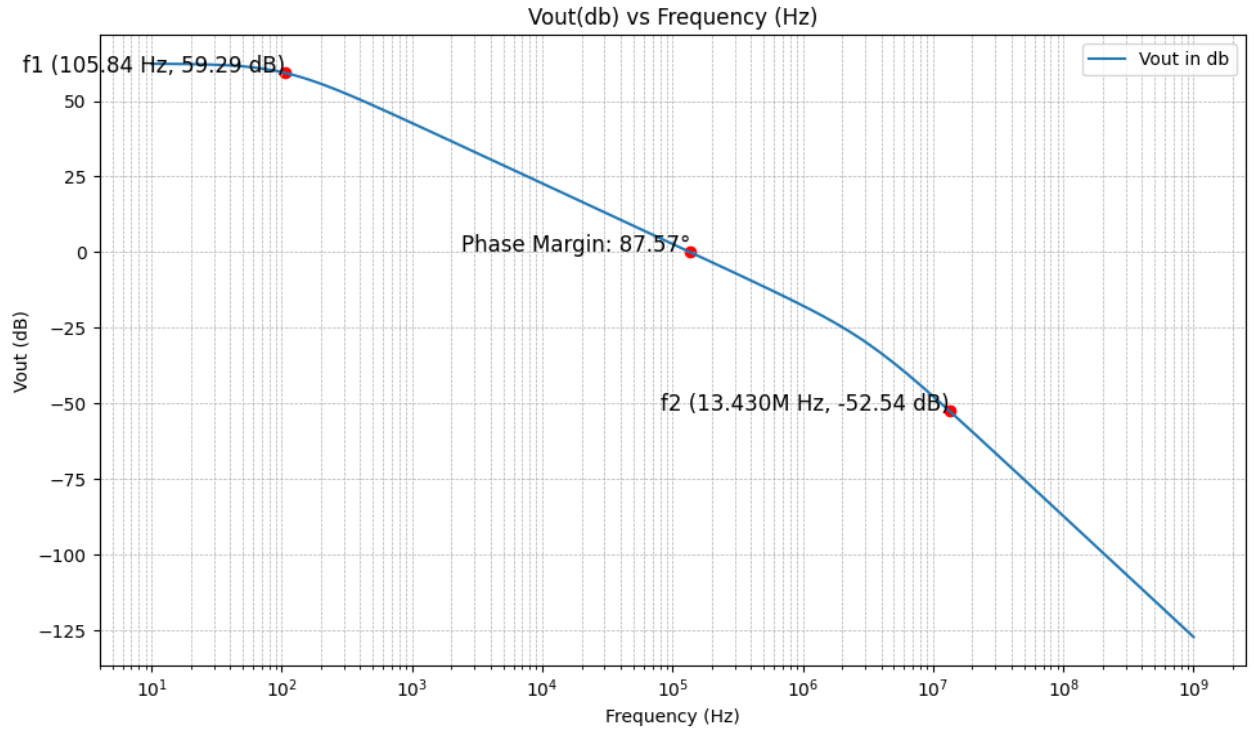


Figure 10: Pole location

From the above analysis we can see that the unity gain bandwidth is closer to the second pole for the heavy load case than the light load case. From the phase margin also we observe a smaller phase margin of 82.62 degrees for the heavy load case and 87.55 for light load case. From this analysis we can say that when we apply light load we get a more stable system.

Table 5: Key Metrics under Heavy and Light Load Conditions

| Parameter | Heavy Load | Light Load |
|----------------------------|------------|------------|
| DC Loop Gain (dB) | 58.52 | 62.30 |
| Unity Gain Bandwidth (kHz) | 402 | 105.8 |
| Phase Margin (degrees) | 82.62 | 87.55 |
| Pole 1 (Hz) | 402.6 | 105.8 |
| Pole 2 (MHz) | 2.84 | 13.43 |

6. PSRR Explanation

LDOs are essential components in the power supply of most ICs. They provide a ripple-free, stable fixed output voltage; isolating it from the input noise. An LDO has several important performance specifications and the power supply rejection ratio (PSRR) is one of them. PSRR is a quantitative measure of the attenuation of input ripples by the LDO at its output. These ripples can originate from various parts of the circuit, like DC/DC converters or shared power supplies of other circuit blocks. PSRR is expressed as $PSRR = 20\log(v_{out}/v_{in})$, where v_{out} and v_{in} refer to magnitudes of input and output ripples. In Figure 12, the PSRR of LDO is divided into two distinct regions (region 1 and region 2). Region 1 covers the low and mid frequency range till the regulator bandwidth frequency (ω_{reg}), where PSRR primarily depends on the loop gain (LG) of the regulator. Region 2 starts after ω_{reg} , where PSRR is independent of LG and is dominated by output parasitics, PCB impedance, etc.

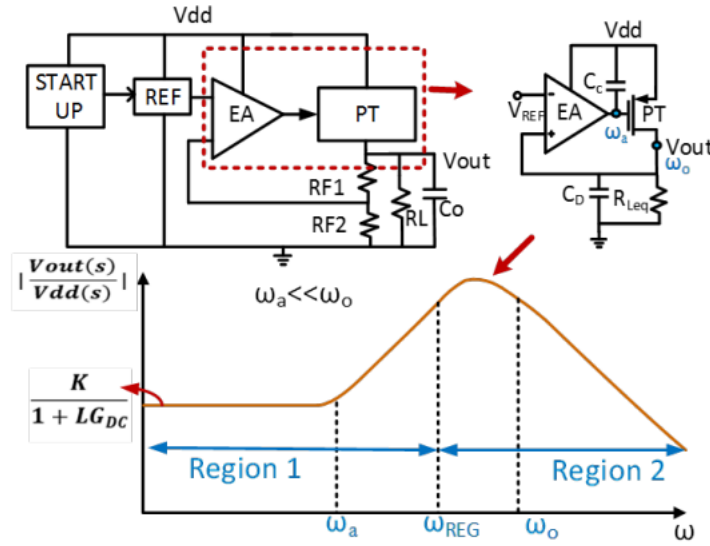


Figure 11: : Block diagram of a low drop-out (LDO) regulator and its associated PSRR curve (linear scale)

6 Power Supply Rejection Ratio (PSRR)

PSRR is a critical parameter in LDO design, dictating how well the regulator can suppress variations in the input supply voltage.

$$PSRR = \frac{PSRR_{OL}(s)}{1 + A_{lg}(s)} \quad (1)$$

where:

- $PSRR_{OL}(s)$ is the open-loop PSRR.
- $A_{lg}(s)$ is the loop gain of the system.

Figure 12: PSRR block diagram.

7. PSRR Simulation Results

we have made three schematics in LTSpice to calculate the three conditions. We have made a simulation artifact for the same.

Case 1 : Loop Gain Analysis

Case 2 : Open Loop PSRR Calculation

Case 3 : Closed Loop PSRR Calculation

Heavy Load (10ma)

Schematic

Case 1:- Loop gain analysis:-


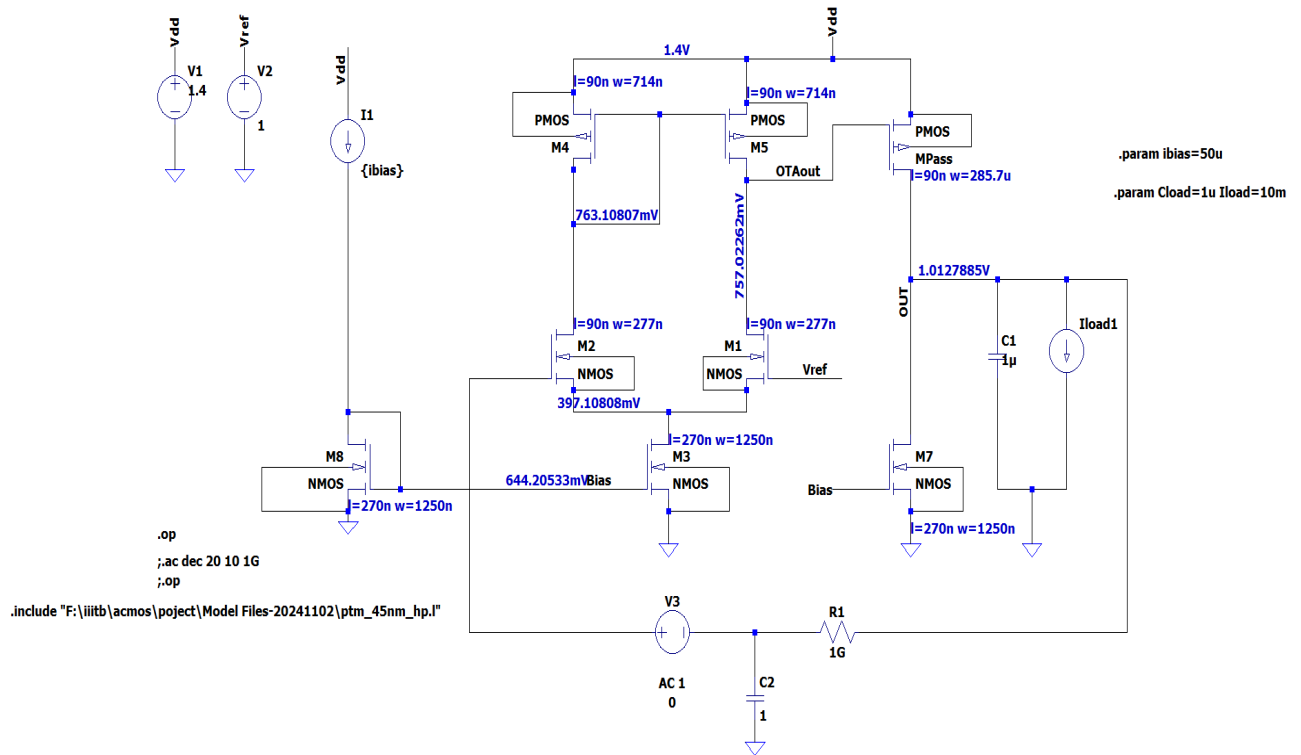


Figure 13: Schematic

Explanation of the artifact used:-

In order to calculate the loop gain we have given a RC circuit in the feedback loop alongwith a AC source with amplitude 1 (as we want to maintain an AC voltage of 1V) at the output. At the same time we also need to bias the circuit and provide a dc voltage to the gate of the nmos in the differential amplifier and for this we are giving the RC circuit which will prevent the flow of dc current to ground but will send any AC signal at the output to ground at high frequency. Also the drop across the resistor will be very less as we have given a very high resistance with very negligible current (since current going into the gate of the mosfet is zero). Thus we will bias the circuit and also calculate the loop gain.

Output Log File:-

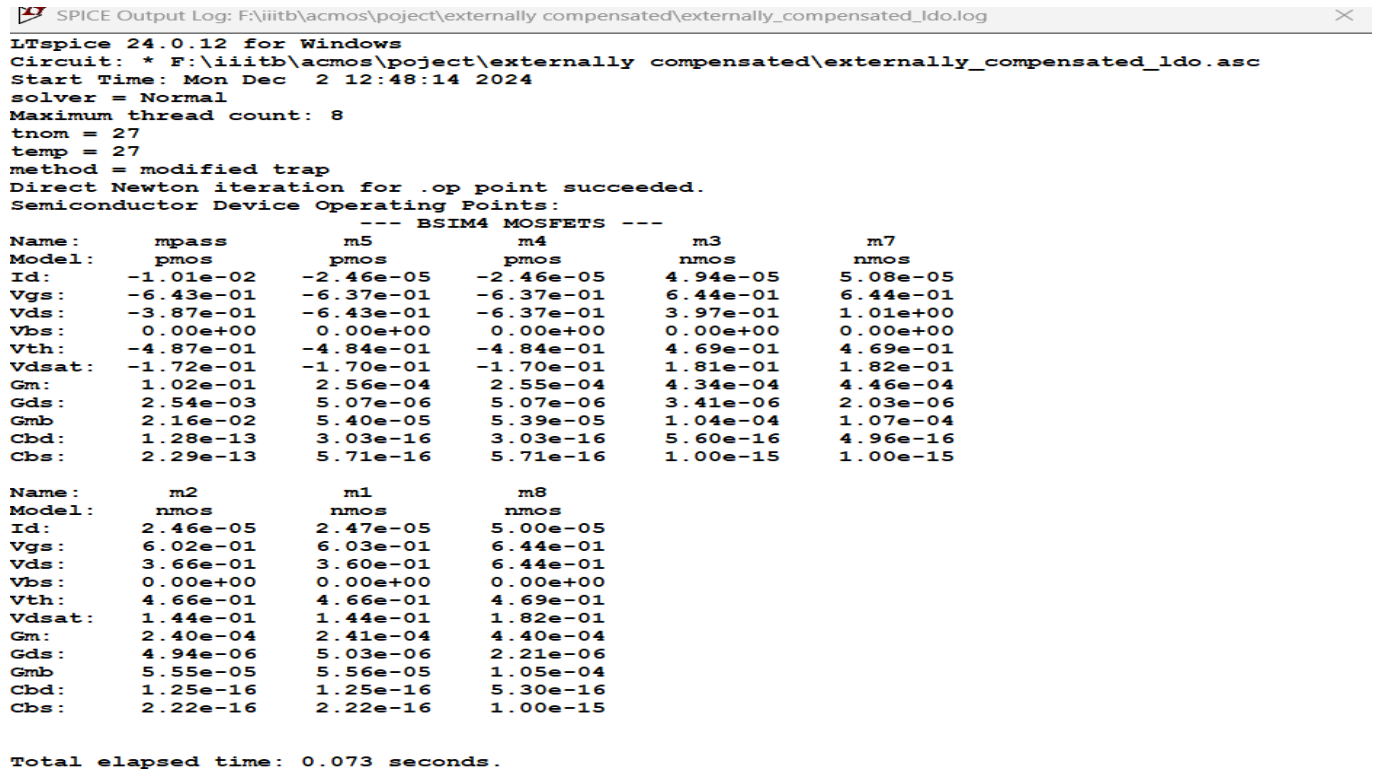

```

SPICE Output Log: F:\iiitb\acmos\project\externally compensated\externally_compensated_1do.log
LTspice 24.0.12 for Windows
Circuit: * F:\iiitb\acmos\project\externally compensated\externally_compensated_1do.asc
Start Time: Mon Dec 2 12:48:14 2024
solver = Normal
Maximum thread count: 8
tnom = 27
temp = 27
method = modified trap
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM4 MOSFETS ---
Name:      mpass      m5      m4      m3      m7
Model:      pmos      pmos      pmos      nmos      nmos
Id:         -1.01e-02  -2.46e-05  -2.46e-05  4.94e-05  5.08e-05
Vgs:        -6.43e-01  -6.37e-01  -6.37e-01  6.44e-01  6.44e-01
Vds:        -3.87e-01  -6.43e-01  -6.37e-01  3.97e-01  1.01e+00
Vbs:        0.00e+00  0.00e+00  0.00e+00  0.00e+00  0.00e+00
Vth:        -4.87e-01  -4.84e-01  -4.84e-01  4.69e-01  4.69e-01
Vdsat:      -1.72e-01  -1.70e-01  -1.70e-01  1.81e-01  1.82e-01
Gm:         1.02e-01  2.56e-04  2.55e-04  4.34e-04  4.46e-04
Gds:        2.54e-03  5.07e-06  5.07e-06  3.41e-06  2.03e-06
Gmb:        2.16e-02  5.40e-05  5.39e-05  1.04e-04  1.07e-04
Cbd:        1.28e-13  3.03e-16  3.03e-16  5.60e-16  4.96e-16
Cbs:        2.29e-13  5.71e-16  5.71e-16  1.00e-15  1.00e-15

Name:      m2      m1      m8
Model:      nmos      nmos      nmos
Id:         2.46e-05  2.47e-05  5.00e-05
Vgs:        6.02e-01  6.03e-01  6.44e-01
Vds:        3.66e-01  3.60e-01  6.44e-01
Vbs:        0.00e+00  0.00e+00  0.00e+00
Vth:        4.66e-01  4.66e-01  4.69e-01
Vdsat:      1.44e-01  1.44e-01  1.82e-01
Gm:         2.40e-04  2.41e-04  4.40e-04
Gds:        4.94e-06  5.03e-06  2.21e-06
Gmb:        5.55e-05  5.56e-05  1.05e-04
Cbd:        1.25e-16  1.25e-16  5.30e-16
Cbs:        2.22e-16  2.22e-16  1.00e-15

Total elapsed time: 0.073 seconds.

```

Figure 14: Output Log Details

From the above file we can verify that all the devices are in saturation as follows:

Transistor Operating Regions Table

This document provides a table summarizing the operating regions of several transistors based on their parameters.

| Transistor | Type | V_{ds} (V) | V_{gs}/V_{sg} (V) | V_t (V) | $V_{gs}/V_{sg} - V_t$ (V) | Operating Region |
|------------|------|--------------|---------------------|-----------|---------------------------|------------------|
| M1 | NMOS | 0.36 | 0.602 | 0.466 | 0.136 | Saturation |
| M2 | NMOS | 0.366 | 0.602 | 0.466 | 0.163 | Saturation |
| M3 | NMOS | 0.397 | 0.644 | 0.469 | 0.334 | Saturation |
| M4 | PMOS | 0.637 | 0.637 | 0.469 | 0.168 | Saturation |
| M5 | PMOS | 0.643 | 0.637 | 0.484 | 0.159 | Saturation |
| Mpass | PMOS | 0.387 | 0.643 | 0.487 | 0.156 | Saturation |
| M7 | NMOS | 1.01 | 0.644 | 0.469 | 0.541 | Saturation |
| M8 | NMOS | 0.644 | 0.644 | 0.489 | 0.155 | Saturation |

Table 6: Transistor Parameters and Operating Regions

Output loop gain:-

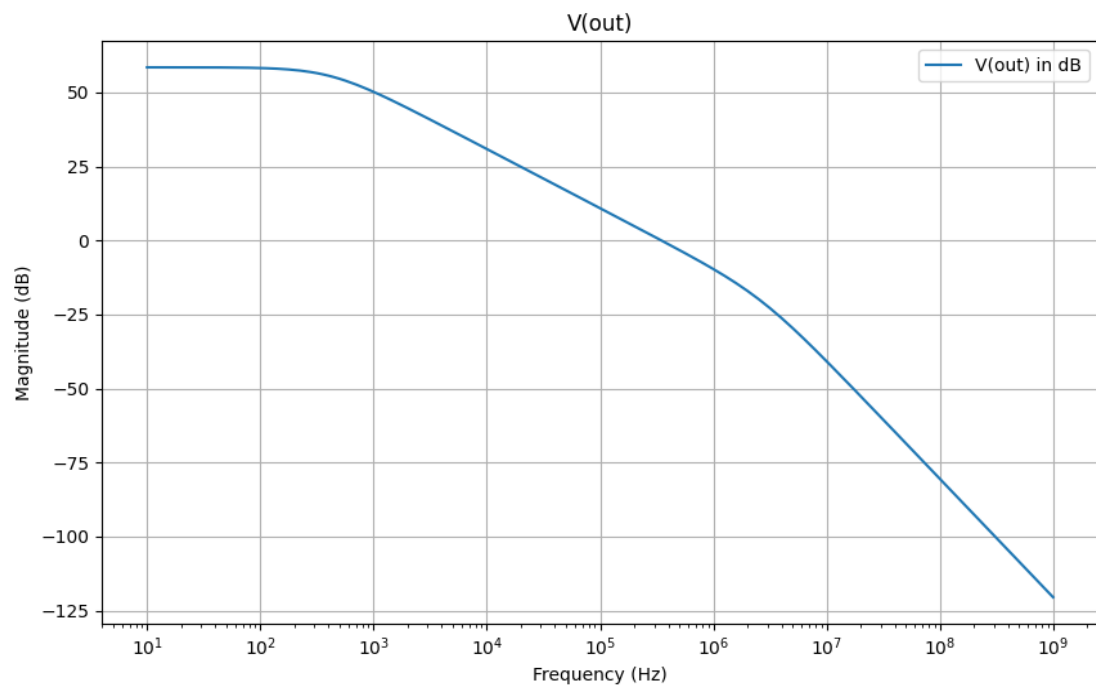


Figure 15: Output loop gain

OTA loop gain:-

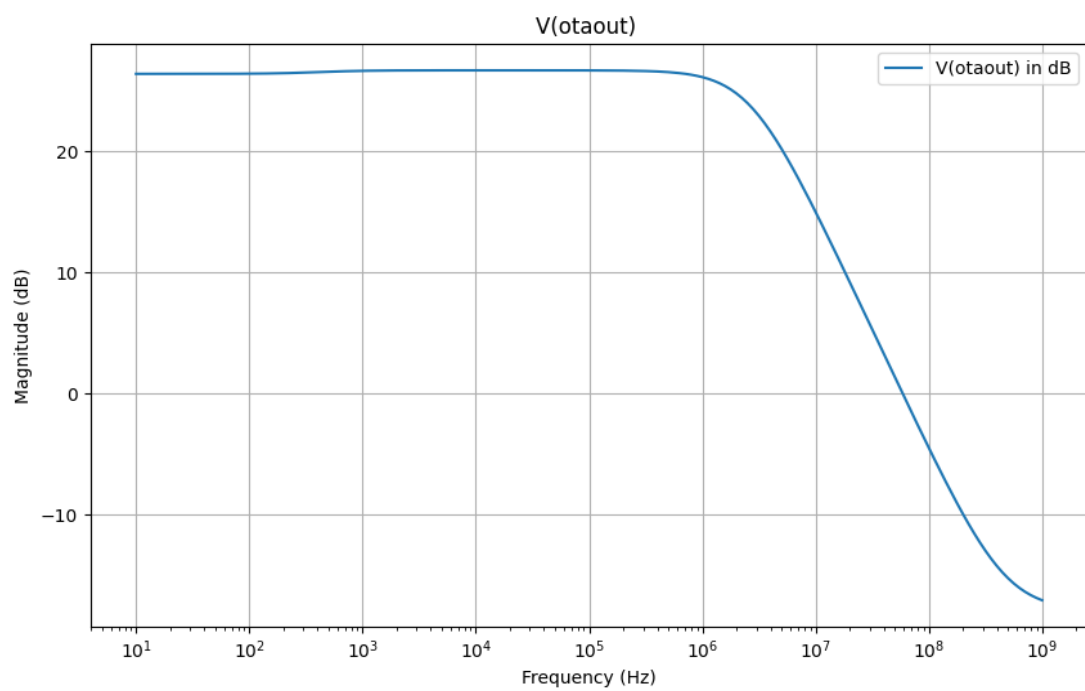


Figure 16: OTA loop gain

Phase margin

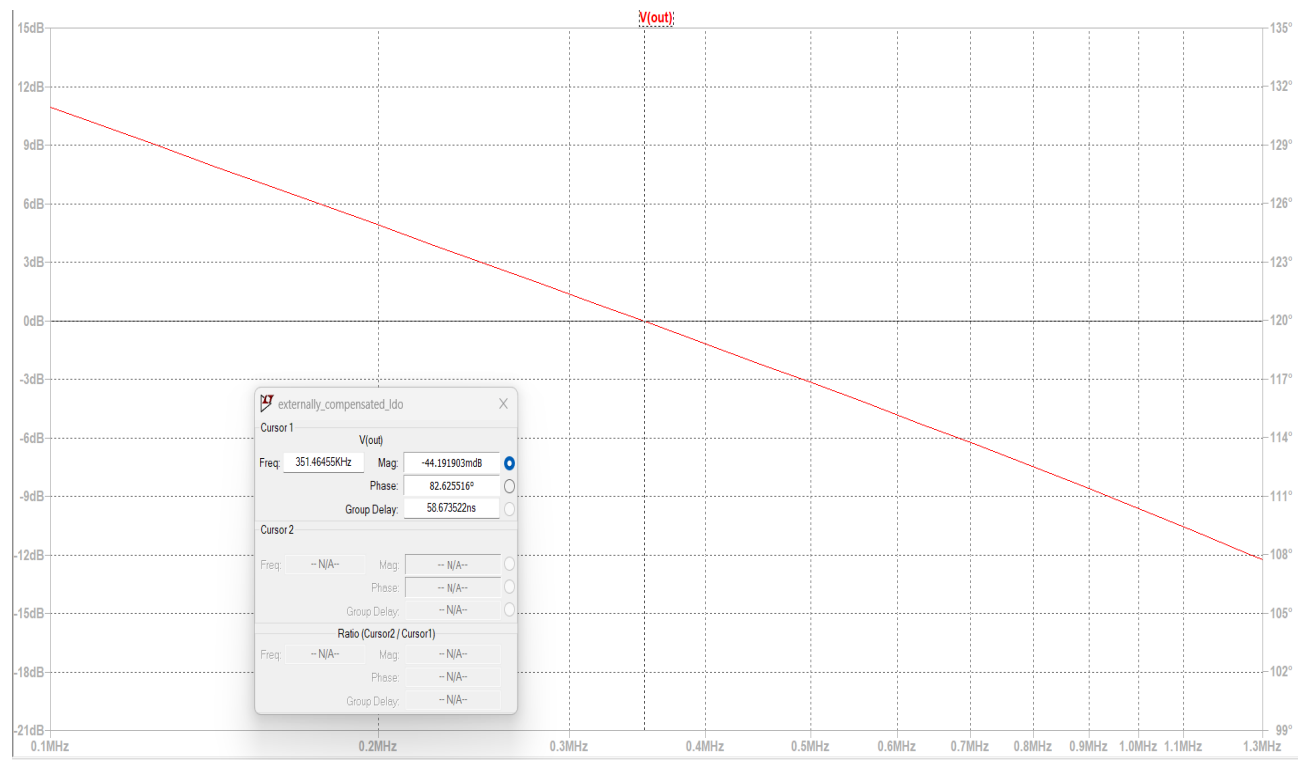


Figure 17: Phase Margin

The phase margin is 82.62

The output voltage (Loop gain) comes out to be close to 58.52db . The formula for loop gain is $A_{diff} \cdot A_{pass}$ where A_{diff} is differential amplifier gain and A_{pass} is the passfet gain.

Case 2:- Open Loop PSRR calculation

Schematic

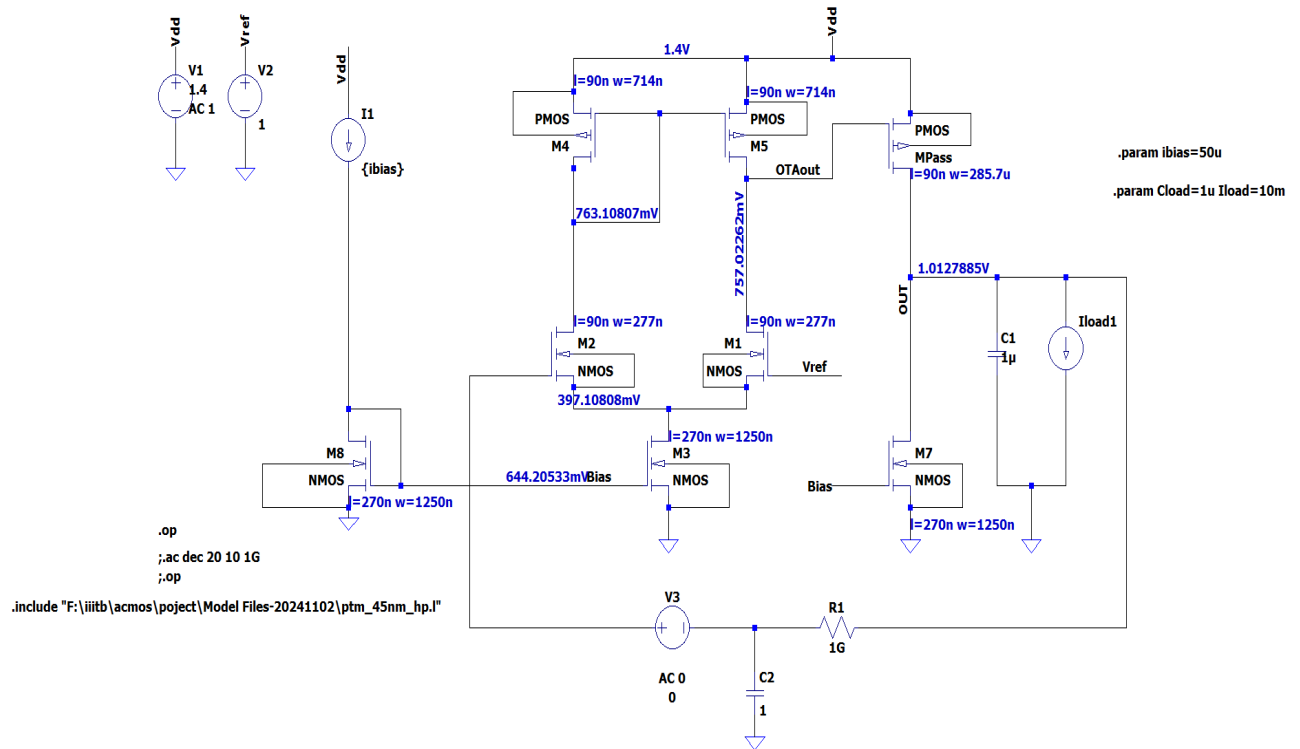


Figure 18: Schematic

Explanation of the artifact used:-

In order to calculate the open loop PSRR we need to send an AC signal from the source which in our case is VDD. Here we are giving an AC 1 signal in the source. This signal is given to the source of the passfet and the source of pmos in the diffamp. We will ideally want very bad PSRR in the diffamp as we want the OTA output to have all the AC noise such that V_{sg} of pmos = 0 (small signal analysis). Thus all the noise will get rejected and we will get a noise free dc voltage at the output of the LDO. Here in order to calculate the open loop PSRR we have a RC circuit to bias the differential amplifier. You can see AC 0 in the circuit indicating that there is an open loop in the circuit . From here we have calculated the open loop PSRR in the circuit. Since there is no feedback in the circuit we can thus say that there will be noise at the output and thus the rejection will be very poor.

Open loop psrr plots:-

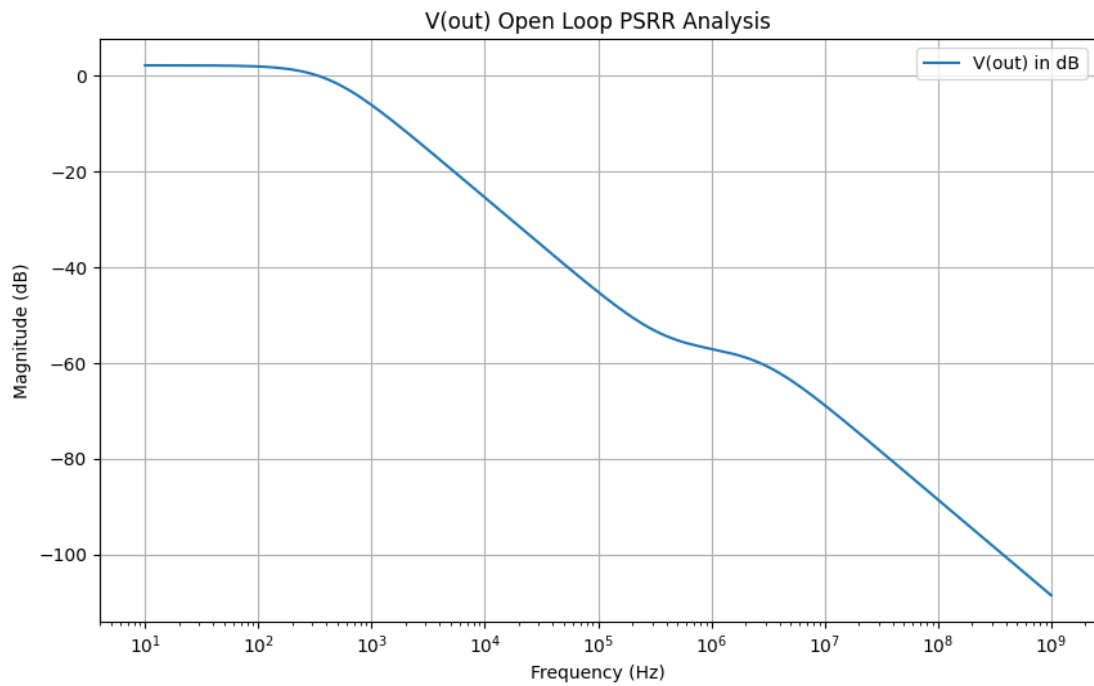


Figure 19: Open loop psrr for Output

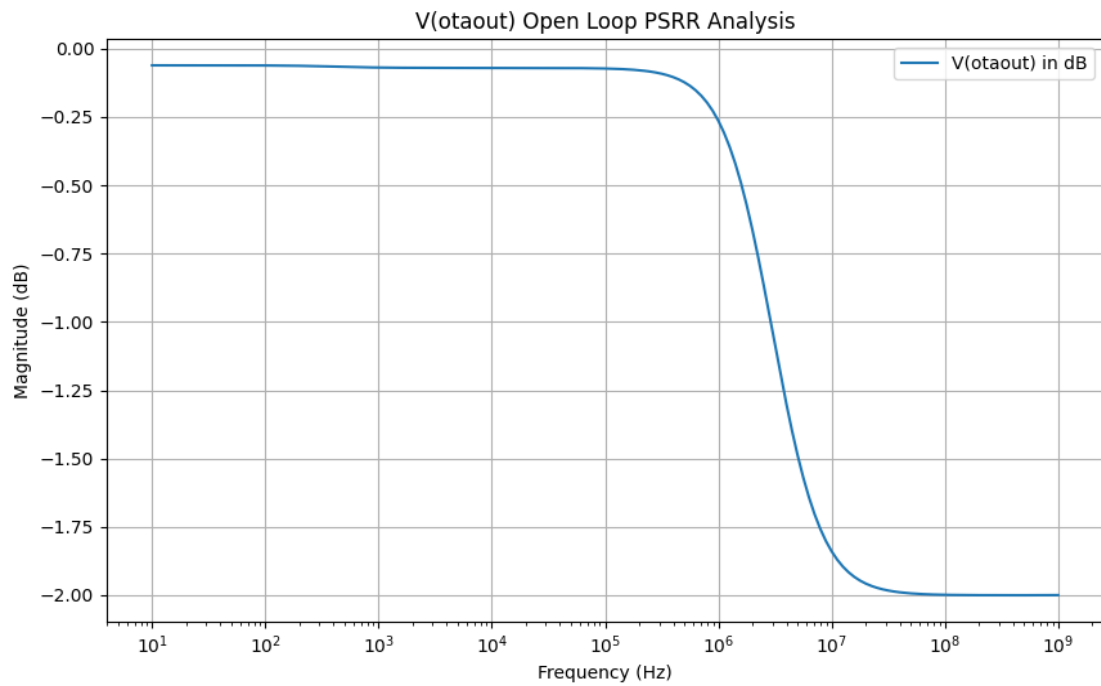


Figure 20: open loop psrr for OTA

Case 3:- Closed Loop PSRR Calculation

.op
 ;ac dec 20 10 1G
 ;op
 .include "F:\iitb\acmos\project\Model Files-20241102\ptm_45nm_hp.l"

Explanation of the artifact used:-

19

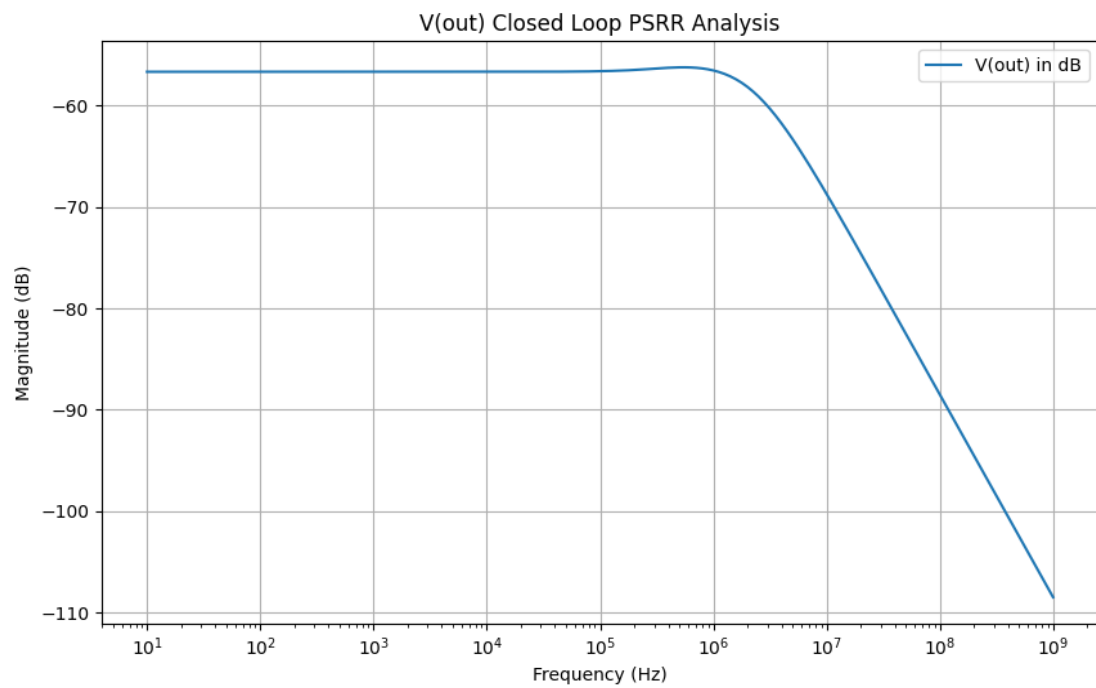
Close loop PSRR:-

Figure 22: close loop psrr for output

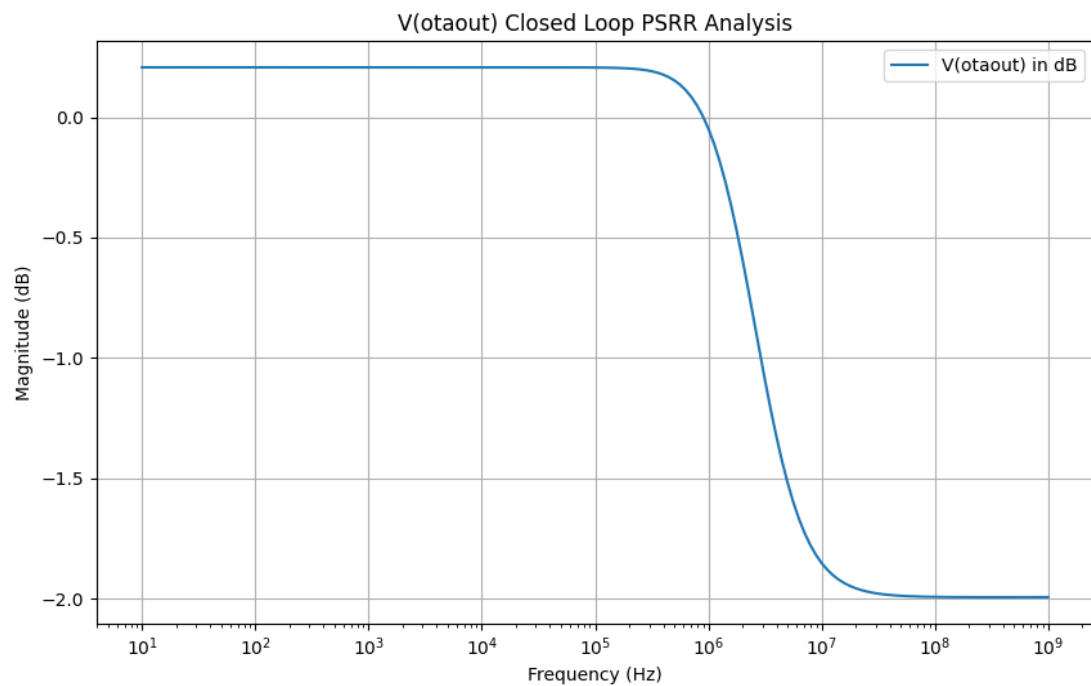


Figure 23: close loop psrr for OTA

Light Load (2ma)

Case 1:- Loop gain analysis

Schematic


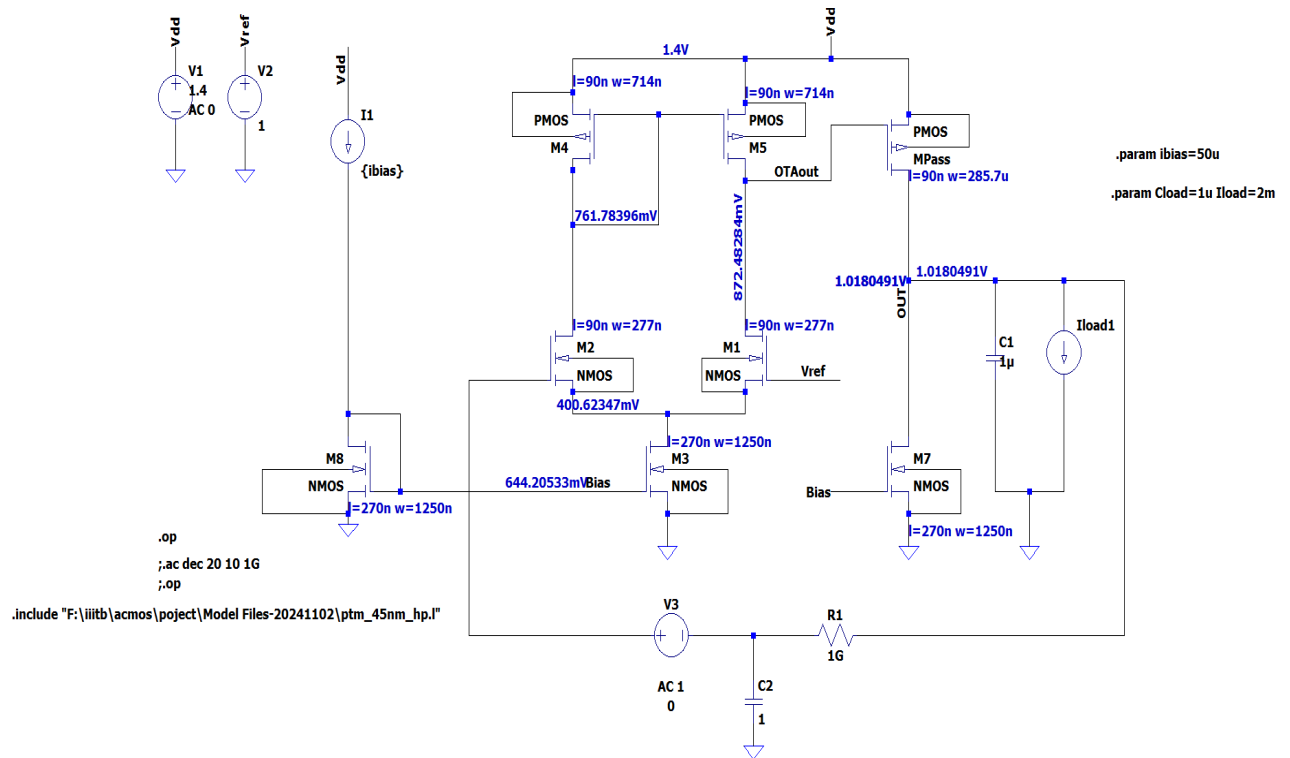


Figure 24: Schematic

Output Log File:-

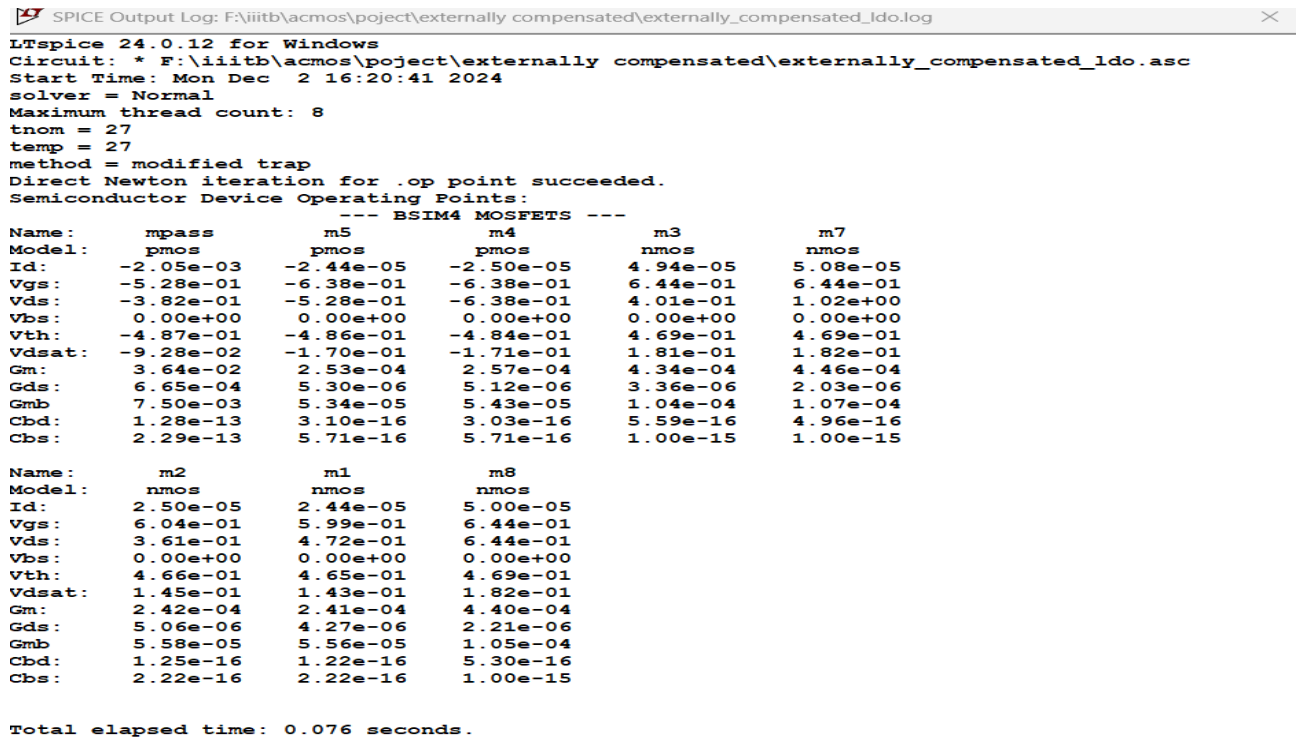

```

SPICE Output Log: F:\iiitb\acmos\project\externally compensated\externally_compensated_ido.log
LTspice 24.0.12 for Windows
Circuit: * F:\iiitb\acmos\project\externally compensated\externally_compensated_ido.asc
Start Time: Mon Dec 2 16:20:41 2024
solver = Normal
Maximum thread count: 8
tnom = 27
temp = 27
method = modified trap
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM4 MOSFETS ---
Name:      mpass      m5      m4      m3      m7
Model:      pmos      pmos      pmos      nmos      nmos
Id:         -2.05e-03  -2.44e-05  -2.50e-05  4.94e-05  5.08e-05
Vgs:        -5.28e-01  -6.38e-01  -6.38e-01  6.44e-01  6.44e-01
Vds:        -3.82e-01  -5.28e-01  -6.38e-01  4.01e-01  1.02e+00
Vbs:         0.00e+00  0.00e+00  0.00e+00  0.00e+00  0.00e+00
Vth:        -4.87e-01  -4.86e-01  -4.84e-01  4.69e-01  4.69e-01
Vdsat:      -9.28e-02  -1.70e-01  -1.71e-01  1.81e-01  1.82e-01
Gm:          3.64e-02  2.53e-04  2.57e-04  4.34e-04  4.46e-04
Gds:          6.65e-04  5.30e-06  5.12e-06  3.36e-06  2.03e-06
Gmb:          7.50e-03  5.34e-05  5.43e-05  1.04e-04  1.07e-04
Cbd:          1.28e-13  3.10e-16  3.03e-16  5.59e-16  4.96e-16
Cbs:          2.29e-13  5.71e-16  5.71e-16  1.00e-15  1.00e-15

Name:      m2      m1      m8
Model:      nmos      nmos      nmos
Id:          2.50e-05  2.44e-05  5.00e-05
Vgs:          6.04e-01  5.99e-01  6.44e-01
Vds:          3.61e-01  4.72e-01  6.44e-01
Vbs:           0.00e+00  0.00e+00  0.00e+00
Vth:          4.66e-01  4.65e-01  4.69e-01
Vdsat:         1.45e-01  1.43e-01  1.82e-01
Gm:           2.42e-04  2.41e-04  4.40e-04
Gds:           5.06e-06  4.27e-06  2.21e-06
Gmb:           5.58e-05  5.56e-05  1.05e-04
Cbd:           1.25e-16  1.22e-16  5.30e-16
Cbs:           2.22e-16  2.22e-16  1.00e-15

Total elapsed time: 0.076 seconds.

```

Figure 25: Output Log Details

Transistor Operating Regions Table

This document provides a table summarizing the operating regions of several transistors based on their parameters.

| Transistor | Type | V_{ds} (V) | V_{gs}/V_{sg} (V) | V_t (V) | $V_{gs}/V_{sg} - V_t$ (V) | Operating Region |
|------------|------|--------------|---------------------|-----------|---------------------------|------------------|
| M1 | NMOS | 0.47 | 0.59 | 0.46 | 0.13 | Saturation |
| M2 | NMOS | 0.36 | 0.64 | 0.46 | 0.18 | Saturation |
| M3 | NMOS | 0.40 | 0.64 | 0.46 | 0.18 | Saturation |
| M4 | PMOS | 0.63 | 0.63 | 0.48 | 0.15 | Saturation |
| M5 | PMOS | 0.52 | 0.63 | 0.48 | 0.15 | Saturation |
| Mpass | PMOS | 0.38 | 0.52 | 0.48 | 0.41 | Saturation |
| M7 | NMOS | 1.02 | 0.64 | 0.468 | 0.15 | Saturation |
| M8 | NMOS | 0.64 | 0.64 | 0.46 | 0.18 | Saturation |

Table 7: Transistor Data Table

Loop gain plot:-

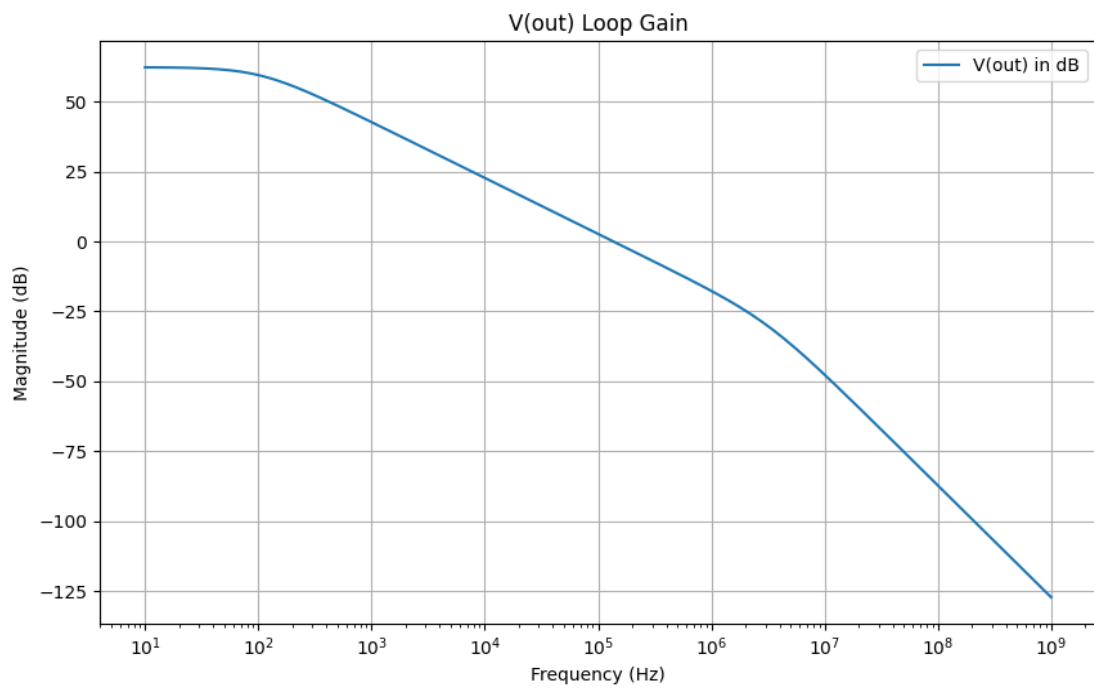


Figure 26: loop gain of output

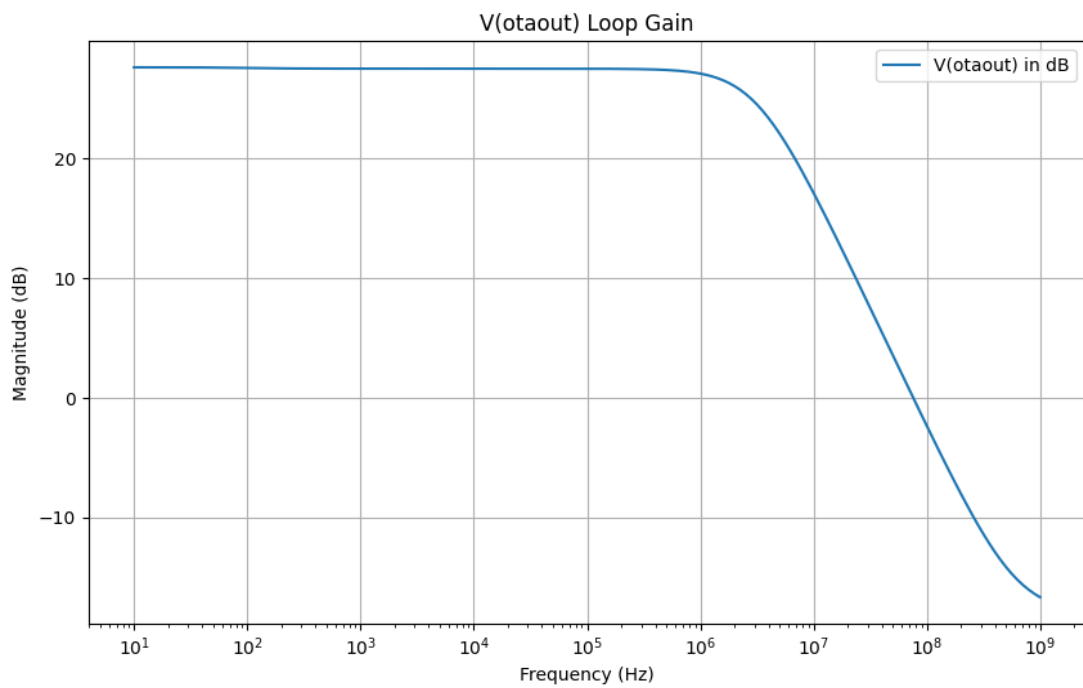


Figure 27: loop gain of OTA

 


Figure 28: Phase Margin

The phase margin obtained is 87.55 degrees. This value is more than that of the value obtained for heavy load. Thus proving the point that for light load we get a better phase margin as the 1st pole and the 2nd pole are far apart.

The circuit schematic shows a 1T1C1R1 memristor-based 1-bit 1T1C1R1 memristor array. The circuit includes a PMOS network (M4, M5, M7) and an NMOS network (M1, M2, M3, M8). It features a biasing circuit with a current source I1 and a voltage source V1. The output is connected to a load capacitor C1 and a load resistor R1. The circuit is simulated using SPICE, with the output voltage Vout shown as a plot.

Key components and parameters:

- PMOS Network:** M4, M5, M7. M4 and M5 are PMOS transistors with $I_D = 90n$ and $w = 714n$. M7 is a PMOS transistor with $I_D = 90n$ and $w = 285.7u$.
- NMOS Network:** M1, M2, M3, M8. M1, M2, and M3 are NMOS transistors with $I_D = 90n$ and $w = 277n$. M8 is an NMOS transistor with $I_D = 270n$ and $w = 1250n$.
- Biasing Circuit:** A current source I1 and a voltage source V1 (1.4V) are used for biasing. The biasing circuit includes a PMOS transistor (M4) and an NMOS transistor (M2).
- Output Stage:** The output is connected to a load capacitor C1 (1pF) and a load resistor R1 (1GΩ).
- Simulation Parameters:**
 - .param ibias=50u
 - .param Cload=1u Iload=2m
 - .ac dec 20 10 1G
 - .op

The output voltage Vout is shown as a plot, indicating the circuit's response to the input signal.

Open loop PSRR plots:-



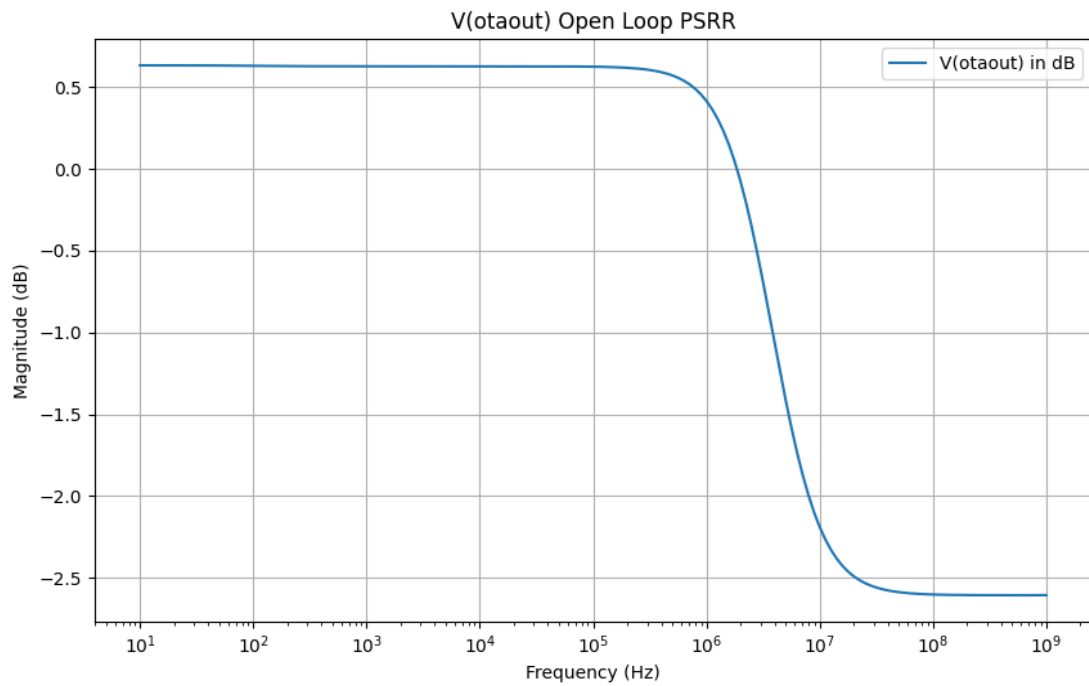


Figure 31: Open loop psrr of OTA

Case 3:- Closed loop PSRR calculation

Schematic

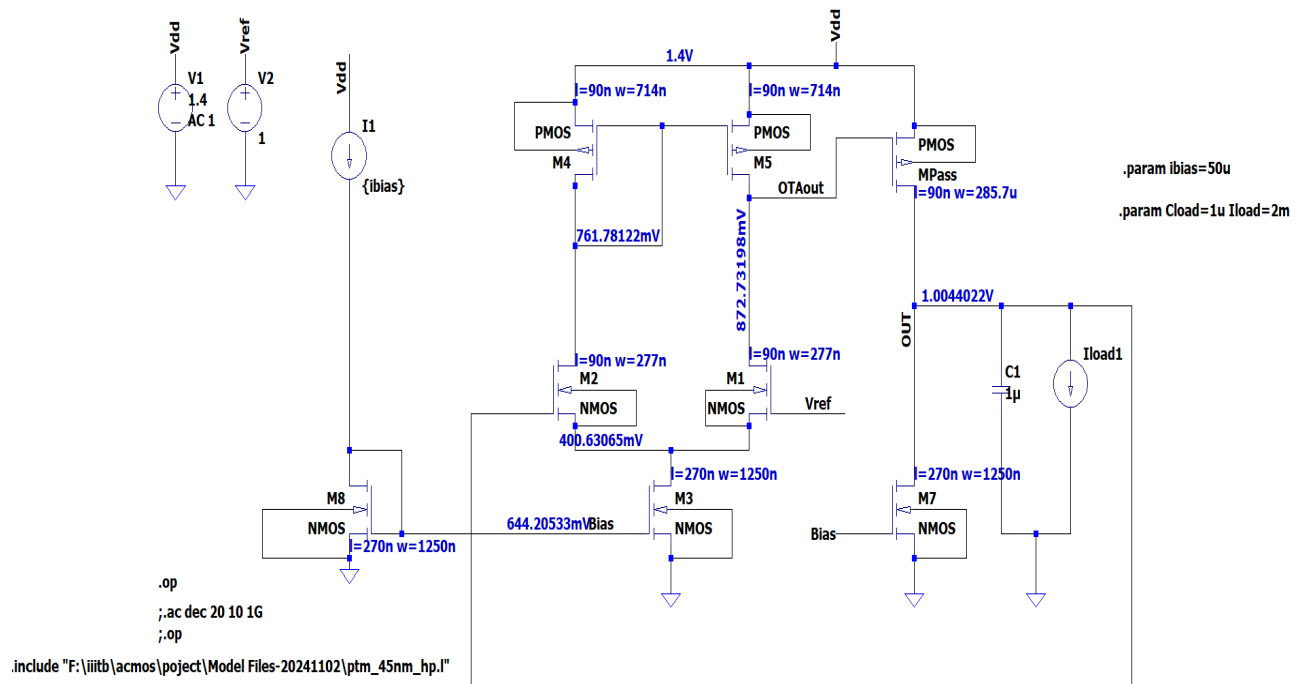


Figure 32: Schematic

Close loop PSRR plots:-

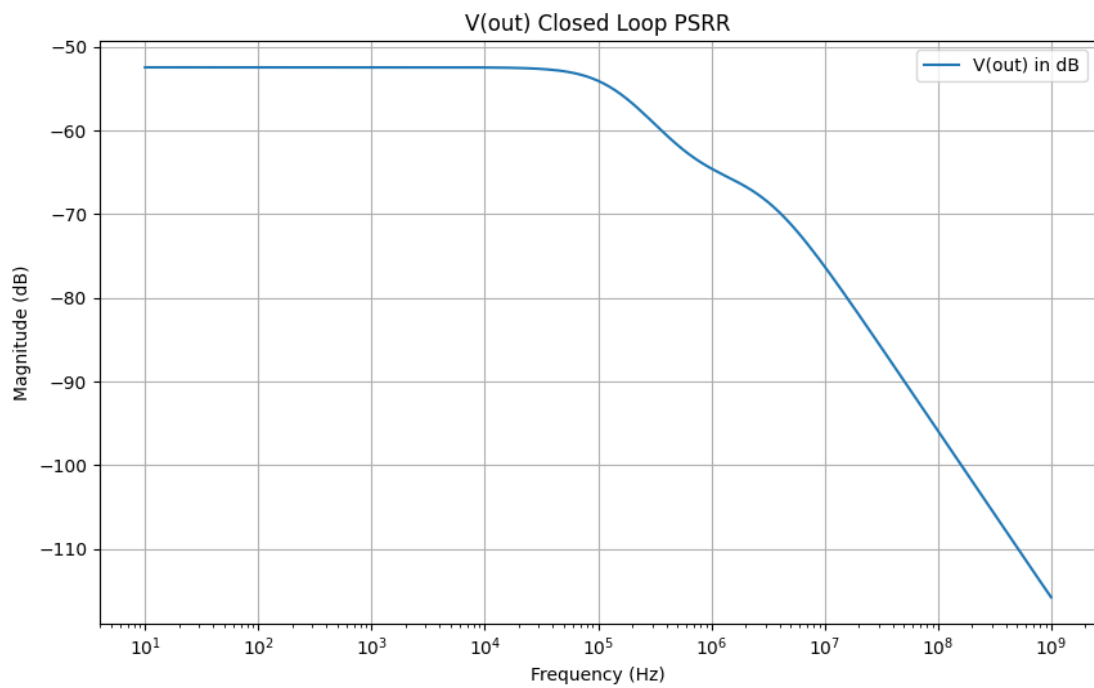


Figure 33: close loop psrr of output

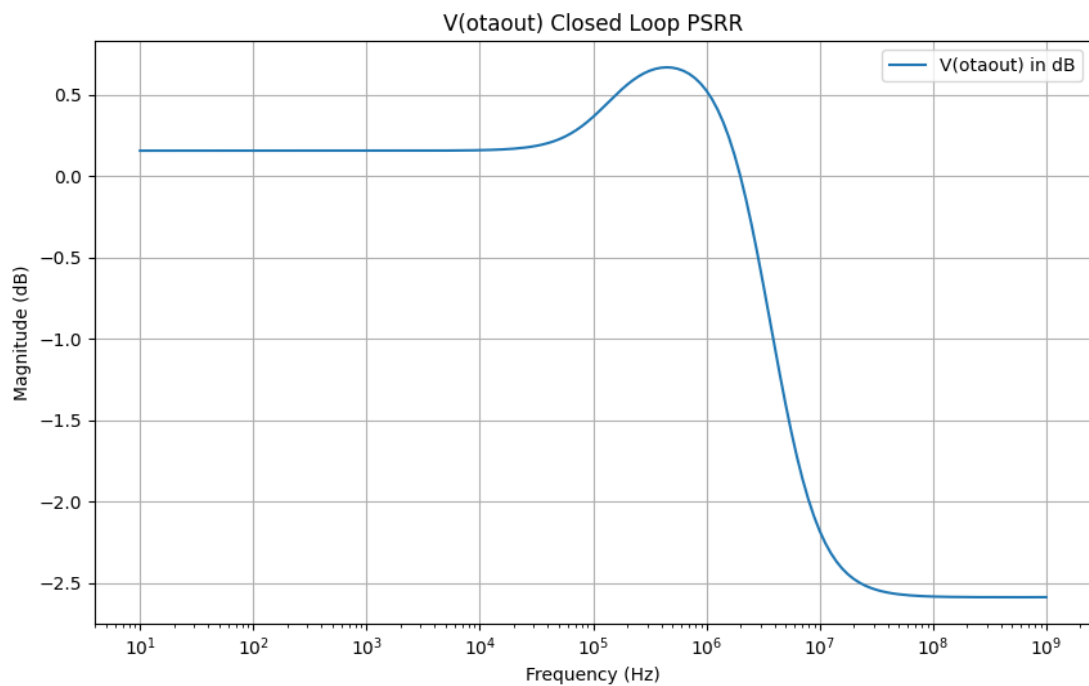


Figure 34: close loop psrr of OTA

We have given a pulse at the load with a rise time and fall time of 1u. Also the period of the pulse is 10m with a 50% duty cycle. From the below figure we can understand that the output is able to settle within the specified range of time. We are not able to observe any overshoot or undershoot in the output.

28

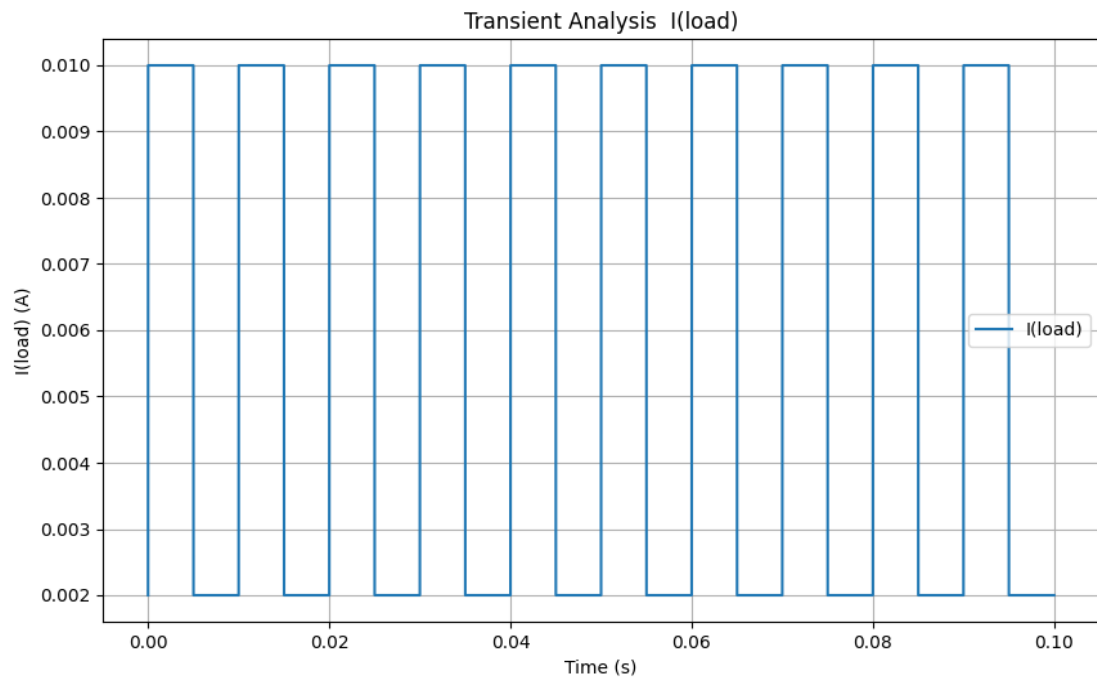
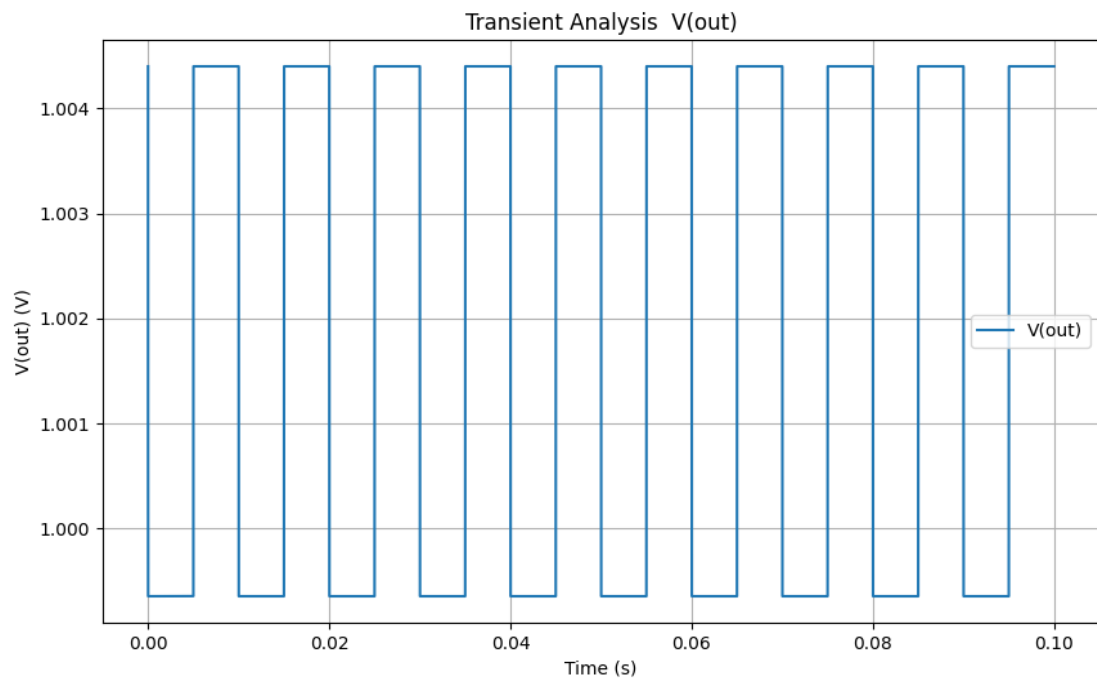
Plots:-Figure 36: I_{load} 

Figure 37: output voltage

9. Simulation vs. Hand Calculations

For Passfet HEAVY LOAD

Hand Calculation

- $r_o = 500 \Omega$
- $g_m = 0.1 \text{ A/V}$
- W_{p1} (first pole location) = 2k
- $g_m r_o = 50$
- $C_L = 1u$
- $C_g g = 0.568p$

Simulation Results from SPICE Error Log:

- $r_o = 1/g_{ds} = 393 \Omega$
- $g_m = 0.102 \text{ A/V}$
- W_{p1} (first pole location) = 2.54k
- $g_m r_o = 40.086$

Table 8: Hand Calculation vs Simulation Results

| Parameter | Hand Calculation | Simulation Result | % Difference |
|-------------------|------------------|-------------------|--------------|
| r_o (ohm) | 500.00 | 395.25 | 21.0% |
| g_m (A/V) | 0.1 | 0.102 | 1.9% |
| $g_m * r_o$ | 50 | 40.316 | 19.36% |
| W_{p1} (Hz) | 2k | 2.53k | 20.94% |
| W_{p2} (Hz) | 22M | 17.85M | 18.86% |
| W_{ugb} (Hz) | 2M | 2.53M | 20.94% |
| r_{odiff} (ohm) | 80k | 98.619k | 18.87% |
| g_{mdiff} (A/V) | 250u | 255u | 1.96% |

| max width= | | | | | | | | |
|------------|-----------|-----------|-----------|----------|----------|----------|----------|----------|
| Name | mpass | m5 | m4 | m3 | m7 | m2 | m1 | m8 |
| Model | pmos | pmos | pmos | nmos | nmos | nmos | nmos | nmos |
| Id | -1.01E-02 | -2.46E-05 | -2.46E-05 | 4.94E-05 | 5.08E-05 | 2.46E-05 | 2.47E-05 | 5.00E-05 |
| Vgs | -6.43E-01 | -6.37E-01 | -6.37E-01 | 6.44E-01 | 6.44E-01 | 6.02E-01 | 6.03E-01 | 6.44E-01 |
| Vds | -3.87E-01 | -6.43E-01 | -6.37E-01 | 3.97E-01 | 1.01E+00 | 3.66E-01 | 3.60E-01 | 6.44E-01 |
| Vbs | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 |
| Vth | -4.87E-01 | -4.84E-01 | -4.84E-01 | 4.69E-01 | 4.69E-01 | 4.66E-01 | 4.66E-01 | 4.69E-01 |
| Vdsat | -1.72E-01 | -1.70E-01 | -1.70E-01 | 1.81E-01 | 1.82E-01 | 1.44E-01 | 1.44E-01 | 1.82E-01 |
| Gm | 1.02E-01 | 2.56E-04 | 2.55E-04 | 4.34E-04 | 4.46E-04 | 2.40E-04 | 2.41E-04 | 4.40E-04 |
| Gds | 2.54E-03 | 5.07E-06 | 5.07E-06 | 3.41E-06 | 2.03E-06 | 4.94E-06 | 5.03E-06 | 2.21E-06 |
| Gmb | 2.16E-02 | 5.40E-05 | 5.39E-05 | 1.04E-04 | 1.07E-04 | 5.55E-05 | 5.56E-05 | 1.05E-04 |
| Cbd | 1.28E-13 | 3.03E-16 | 3.03E-16 | 5.60E-16 | 4.96E-16 | 1.25E-16 | 1.25E-16 | 5.30E-16 |
| Cbs | 2.29E-13 | 5.71E-16 | 5.71E-16 | 1.00E-15 | 1.00E-15 | 2.22E-16 | 2.22E-16 | 1.00E-15 |
| ro | 3.94E+02 | 1.97E+05 | 1.97E+05 | 2.93E+05 | 4.93E+05 | 2.02E+05 | 1.99E+05 | 4.52E+05 |
| gm*ro | 4.02E+01 | 5.05E+01 | 5.03E+01 | 1.27E+02 | 2.20E+02 | 4.86E+01 | 4.79E+01 | 1.99E+02 |

Table 9: Updated Transistor Parameter Table

For Passfet LIGHT LOAD

Hand Calculation

- $r_o = 2500 \Omega$
- $g_m = 0.02 \text{ A/V}$
- W_{p1} (first pole location) = 400
- $g_m r_o = 50$
- $C_L = 1u$
- $C_{gg} = 0.1136p$

Simulation Results from SPICE Error Log:

- $r_o = 1/g_{ds} = 1503.7 \Omega$
- $g_m = 0.0364 \text{ A/V}$
- W_{p1} (first pole location) = 665.02
- $g_m r_o = 54.7$

Table 10: Hand Calculation vs Simulation Results

| Parameter | Hand Calculation | Simulation Result | % Difference |
|-------------------|------------------|-------------------|--------------|
| r_o (ohm) | 2500.00 | 1503.7 | 39.0% |
| g_m (A/V) | 0.02 | 0.0364 | 45% |
| $g_m * r_o$ | 50 | 54.7 | 8.5% |
| W_{p1} (Hz) | 400 | 665.02 | 39.8% |
| W_{p2} (Hz) | 110M | 84.4M | 23.2% |
| W_{ugb} (Hz) | 400k | 665.02k | 39.8% |
| r_{odiff} (ohm) | 80k | 104.2k | 23.07% |
| g_{mdiff} (A/V) | 250u | 253u | 1.185% |

| max width= | | | | | | | | |
|--------------|-----------|-----------|-----------|----------|----------|----------|----------|----------|
| Name | mpass | m5 | m4 | m3 | m7 | m2 | m1 | m8 |
| Model | pmos | pmos | pmos | nmos | nmos | nmos | nmos | nmos |
| Id | -2.05E-03 | -2.44E-05 | -2.50E-05 | 4.94E-05 | 5.08E-05 | 2.50E-05 | 2.44E-05 | 5.00E-05 |
| Vgs | -5.28E-01 | -6.38E-01 | -6.38E-01 | 6.44E-01 | 6.44E-01 | 6.04E-01 | 5.99E-01 | 6.44E-01 |
| Vds | -3.82E-01 | -5.28E-01 | -6.38E-01 | 4.01E-01 | 1.02E+00 | 3.61E-01 | 4.72E-01 | 6.44E-01 |
| Vbs | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 |
| Vth | -4.87E-01 | -4.86E-01 | -4.84E-01 | 4.69E-01 | 4.69E-01 | 4.66E-01 | 4.65E-01 | 4.69E-01 |
| Vdsat | -9.28E-02 | -1.70E-01 | -1.71E-01 | 1.81E-01 | 1.82E-01 | 1.45E-01 | 1.43E-01 | 1.82E-01 |
| Gm | 3.64E-02 | 2.53E-04 | 2.57E-04 | 4.34E-04 | 4.46E-04 | 2.42E-04 | 2.41E-04 | 4.40E-04 |
| Gds | 6.65E-04 | 5.30E-06 | 5.12E-06 | 3.36E-06 | 2.03E-06 | 5.06E-06 | 4.27E-06 | 2.21E-06 |
| Gmb | 7.50E-03 | 5.34E-05 | 5.43E-05 | 1.04E-04 | 1.07E-04 | 5.58E-05 | 5.56E-05 | 1.05E-04 |
| Cbd | 1.28E-13 | 3.10E-16 | 3.03E-16 | 5.59E-16 | 4.96E-16 | 1.25E-16 | 1.22E-16 | 5.30E-16 |
| Cbs | 2.29E-13 | 5.71E-16 | 5.71E-16 | 1.00E-15 | 1.00E-15 | 2.22E-16 | 2.22E-16 | 1.00E-15 |
| ro | 1.50E+03 | 1.89E+05 | 1.95E+05 | 2.98E+05 | 4.93E+05 | 1.98E+05 | 2.34E+05 | 4.52E+05 |
| gm*ro | 5.47E+01 | 4.77E+01 | 5.02E+01 | 1.29E+02 | 2.20E+02 | 4.78E+01 | 5.64E+01 | 1.99E+02 |

Table 11: Transistor Parameter Table

Internally Compensated LDO

1. Specifications

Table 12: Specifications Summary

| Parameter | Value |
|--------------------|-------|
| Vin | 1.4V |
| Vout | 1V |
| PSRR | 60dB |
| Iload (min) | 2mA |
| Iload (max) | 10mA |
| Cload | 2nF |
| Iquiescent | 50uA |
| Transient duration | 1u |

we have made three schematics in LTSpice to calculate the three conditions. We have made a simulation artifact for the same.

Case 1 : Loop Gain Analysis

Case 2 : Open Loop PSRR Calculation

Case 3 : Closed Loop PSRR Calculation

Light Load (2mA)

Schematic

Case 1:- Loop gain analysis:-


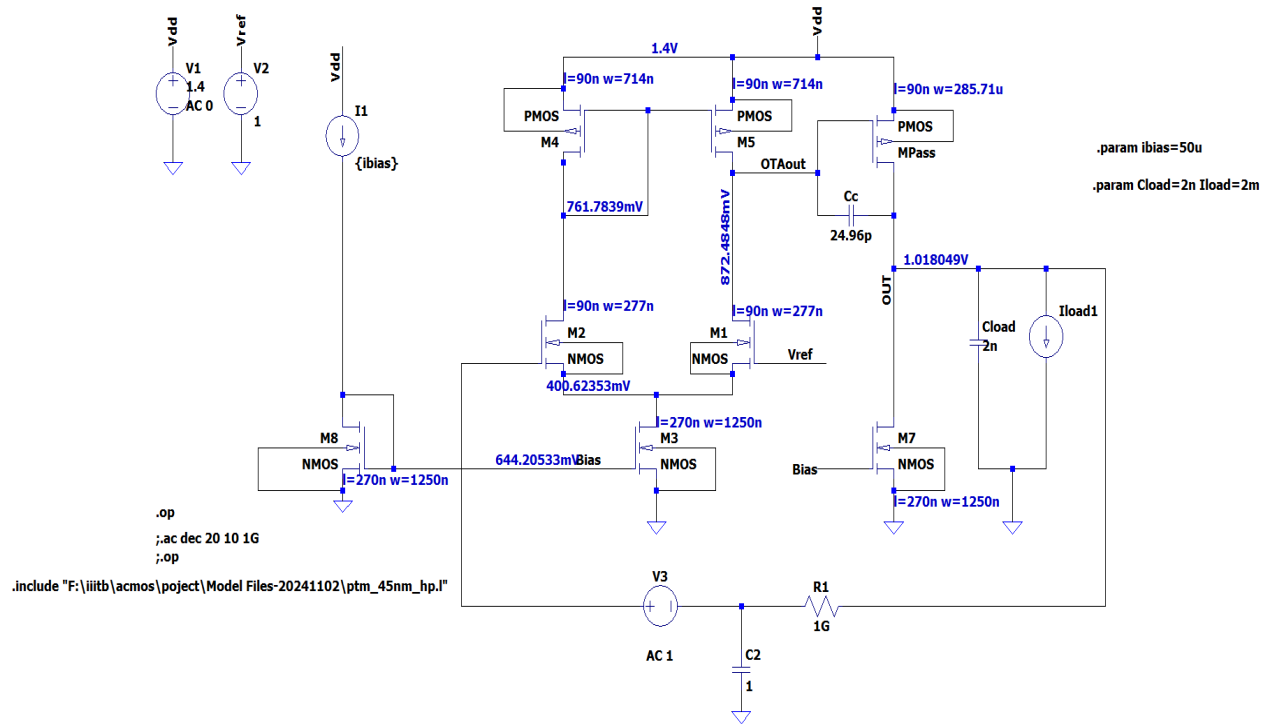


Figure 38: Schematic

Explanation of the artifact used:-

Output Log File:-

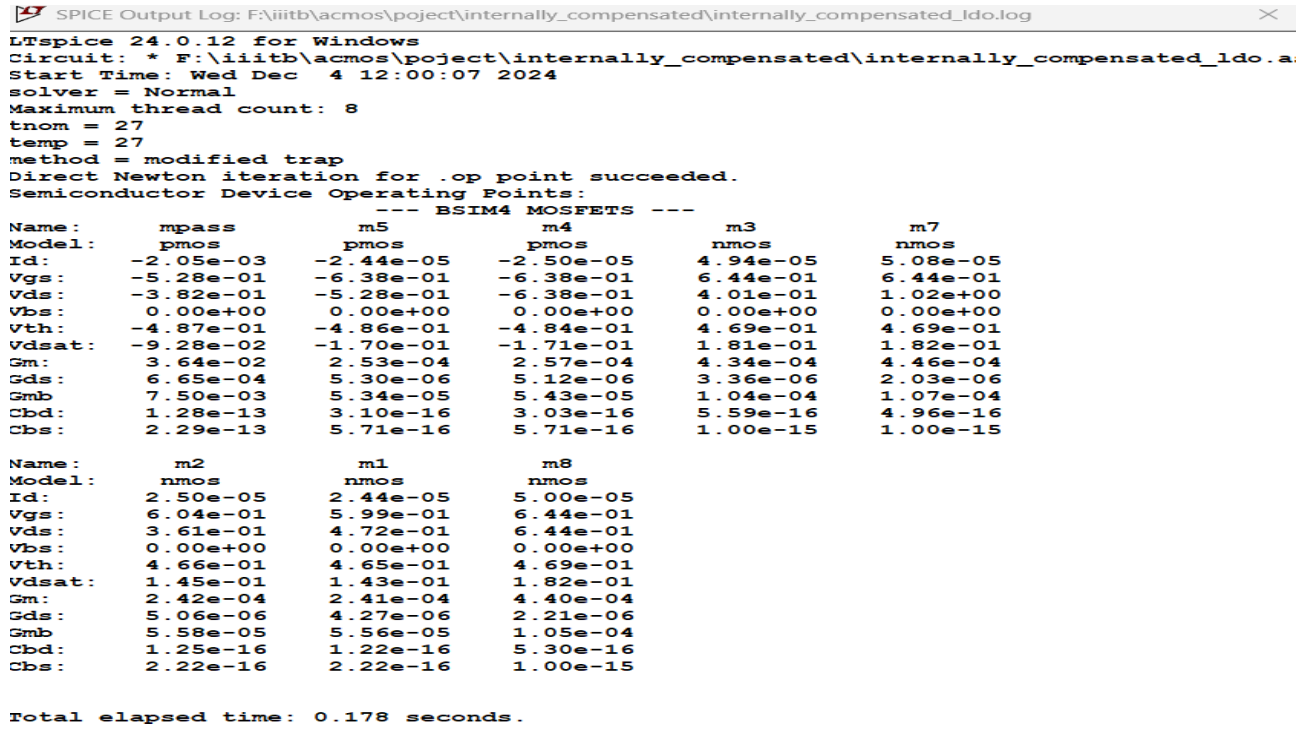

```

SPICE Output Log: F:\iiitb\acmos\project\internally_compensated\internally_compensated_ido.log
LTspice 24.0.12 for Windows
Circuit: * F:\iiitb\acmos\project\internally_compensated\internally_compensated_ido.a
Start Time: Wed Dec 4 12:00:07 2024
solver = Normal
Maximum thread count: 8
tnom = 27
temp = 27
method = modified trap
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM4 MOSFETS ---
Name:      mpass      m5      m4      m3      m7
Model:      pmos      pmos      pmos      nmos      nmos
Id:         -2.05e-03  -2.44e-05  -2.50e-05  4.94e-05  5.08e-05
Vgs:        -5.28e-01  -6.38e-01  -6.38e-01  6.44e-01  6.44e-01
Vds:        -3.82e-01  -5.28e-01  -6.38e-01  4.01e-01  1.02e+00
Vbs:        0.00e+00  0.00e+00  0.00e+00  0.00e+00  0.00e+00
Vth:        -4.87e-01  -4.86e-01  -4.84e-01  4.69e-01  4.69e-01
Vdsat:      -9.28e-02  -1.70e-01  -1.71e-01  1.81e-01  1.82e-01
Gm:         3.64e-02  2.53e-04  2.57e-04  4.34e-04  4.46e-04
Gds:        6.65e-04  5.30e-06  5.12e-06  3.36e-06  2.03e-06
Gmb:        7.50e-03  5.34e-05  5.43e-05  1.04e-04  1.07e-04
Cbd:        1.28e-13  3.10e-16  3.03e-16  5.59e-16  4.96e-16
Cbs:        2.29e-13  5.71e-16  5.71e-16  1.00e-15  1.00e-15

Name:      m2      m1      m8
Model:      nmos      nmos      nmos
Id:         2.50e-05  2.44e-05  5.00e-05
Vgs:        6.04e-01  5.99e-01  6.44e-01
Vds:        3.61e-01  4.72e-01  6.44e-01
Vbs:        0.00e+00  0.00e+00  0.00e+00
Vth:        4.66e-01  4.65e-01  4.69e-01
Vdsat:      1.45e-01  1.43e-01  1.82e-01
Gm:         2.42e-04  2.41e-04  4.40e-04
Gds:        5.06e-06  4.27e-06  2.21e-06
Gmb:        5.58e-05  5.56e-05  1.05e-04
Cbd:        1.25e-16  1.22e-16  5.30e-16
Cbs:        2.22e-16  2.22e-16  1.00e-15

Total elapsed time: 0.178 seconds.

```

Figure 39: Output Log Detail

From the above file we can verify that all the devices are in saturation as follows:

Transistor Operating Regions Table

This document provides a table summarizing the operating regions of several transistors based on their parameters.

| Transistor | Type | V_{ds} (V) | V_{gs}/V_{sg} (V) | V_t (V) | $V_{gs}/V_{sg} - V_t$ (V) | Operating Region |
|------------|------|--------------|---------------------|-----------|---------------------------|------------------|
| M1 | NMOS | 0.472 | 0.599 | 0.465 | 0.134 | Saturation |
| M2 | NMOS | 0.361 | 0.604 | 0.466 | 0.138 | Saturation |
| M3 | NMOS | 0.401 | 0.644 | 0.469 | 0.175 | Saturation |
| M4 | PMOS | 0.638 | 0.638 | 0.484 | 0.267 | Saturation |
| M5 | PMOS | 0.528 | 0.638 | 0.487 | 0.151 | Saturation |
| Mpass | PMOS | 0.382 | 0.528 | 0.487 | 0.041 | Saturation |
| M7 | NMOS | 1.02 | 0.644 | 0.469 | 0.175 | Saturation |
| M8 | NMOS | 0.644 | 0.644 | 0.469 | 0.1.75 | Saturation |

Table 13: Transistor Parameters and Operating Regions

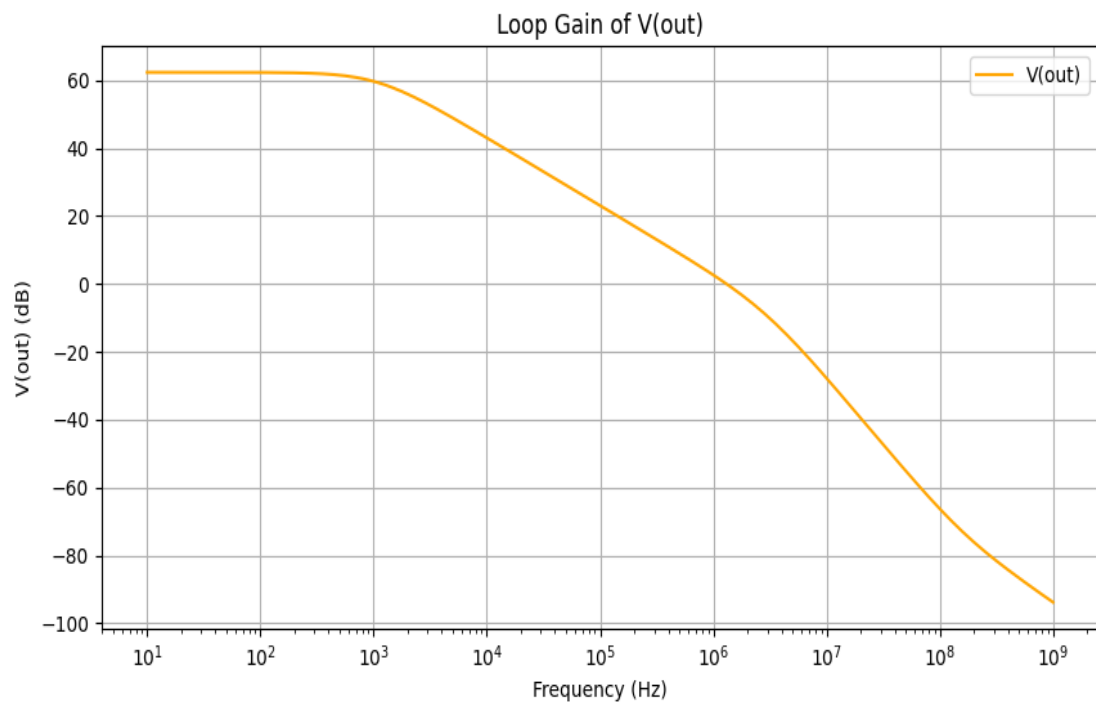
Loop gain plots:-

Figure 40: Loop gain of LDO

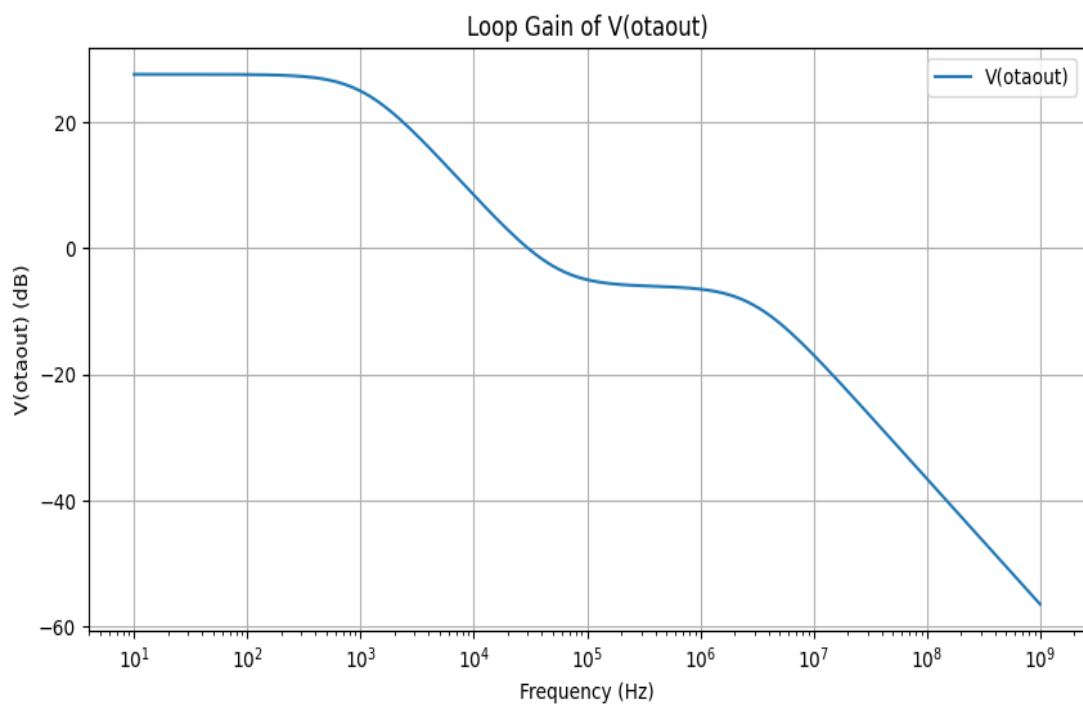


Figure 41: Loop gain of OTA

Phase margin

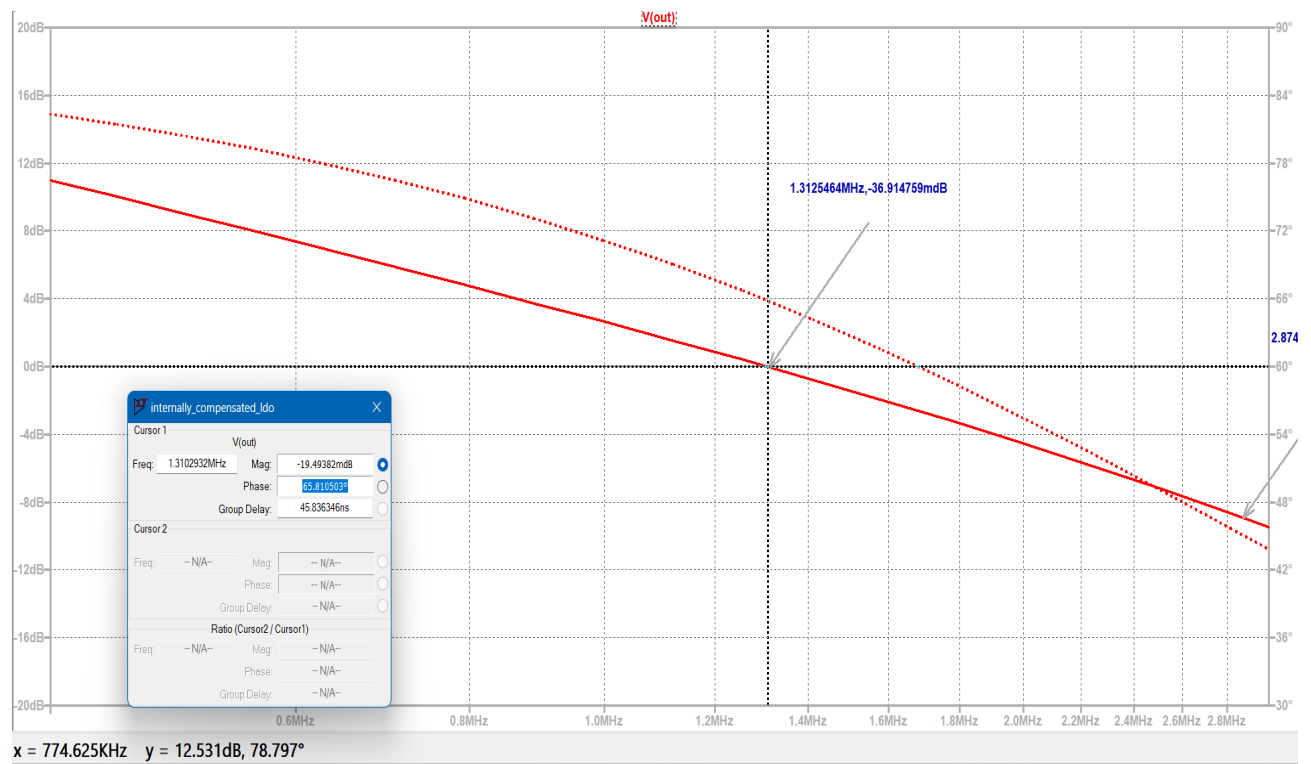


Figure 42: Phase Margin

Case 2:- Open Loop PSRR calculation

Schematic

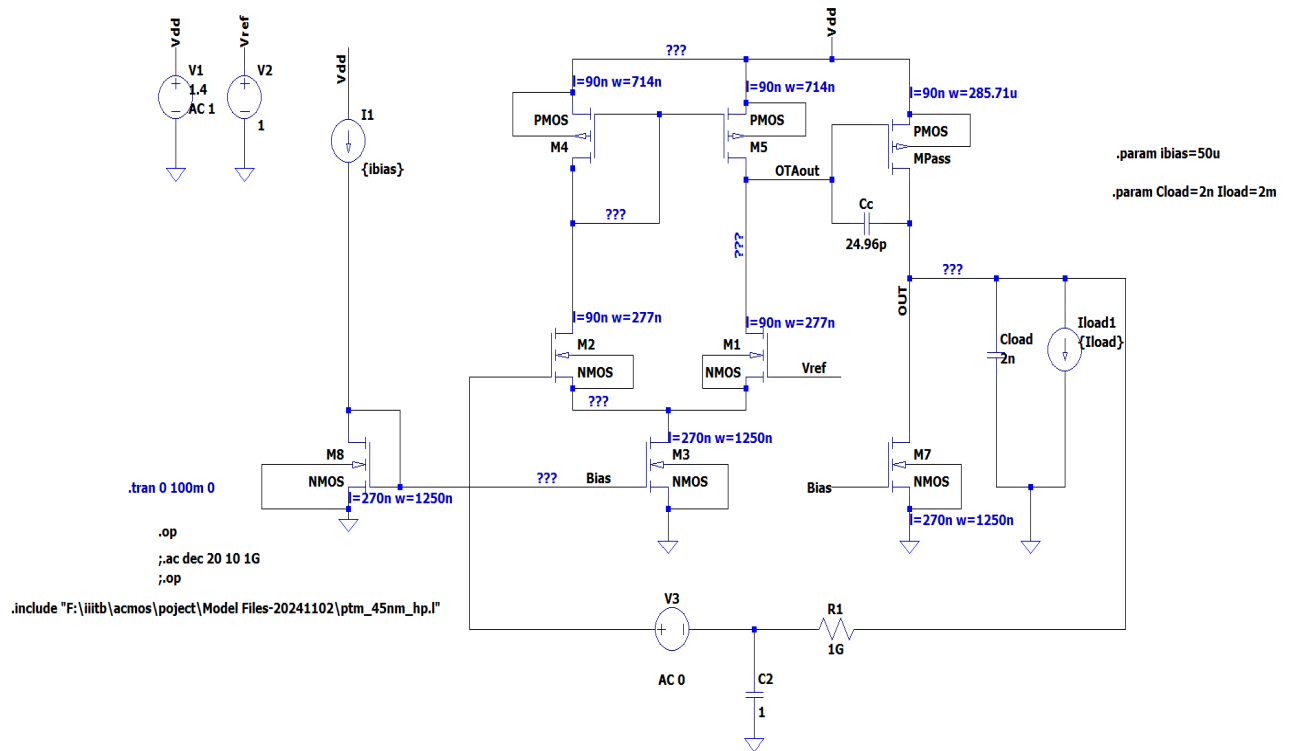


Figure 43: Schematic

Open loop PSRR plots:-

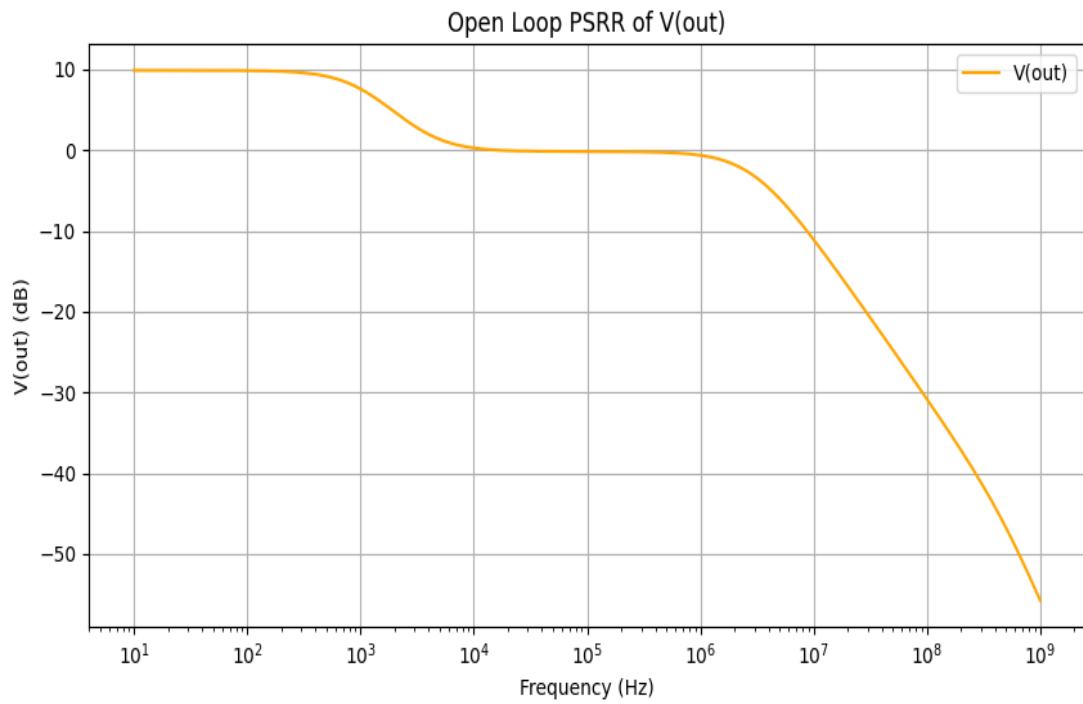


Figure 44: Open loop psrr of LDO

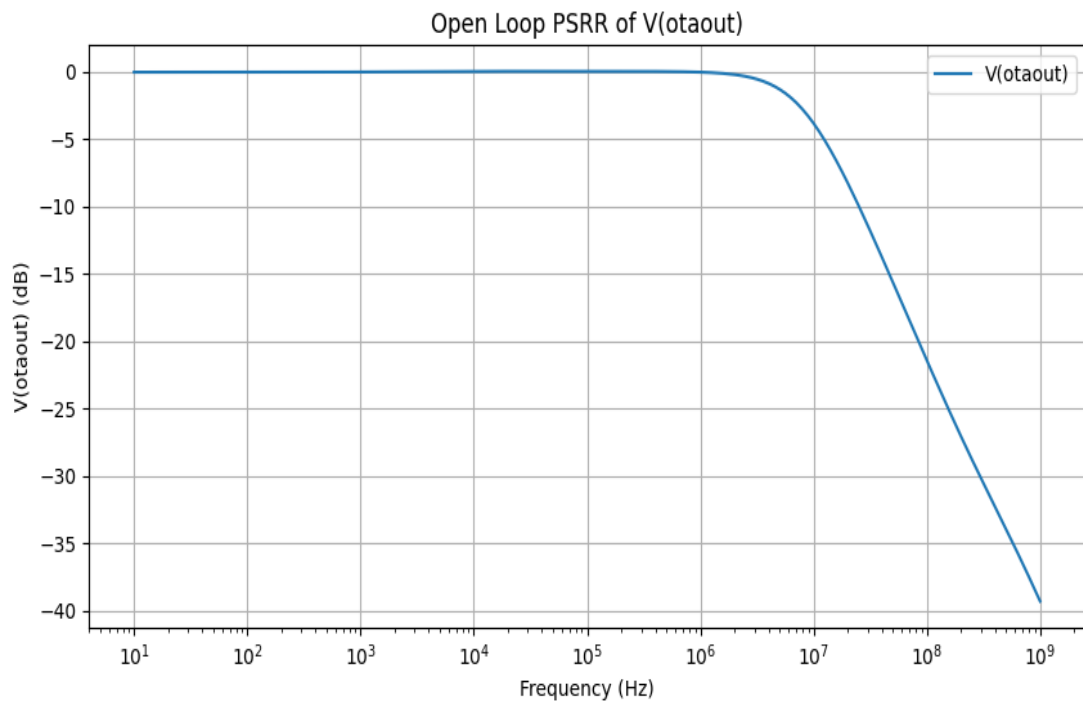


Figure 45: Open loop psrr of OTA

Case 3:- Closed loop PSRR calculation

Schematic

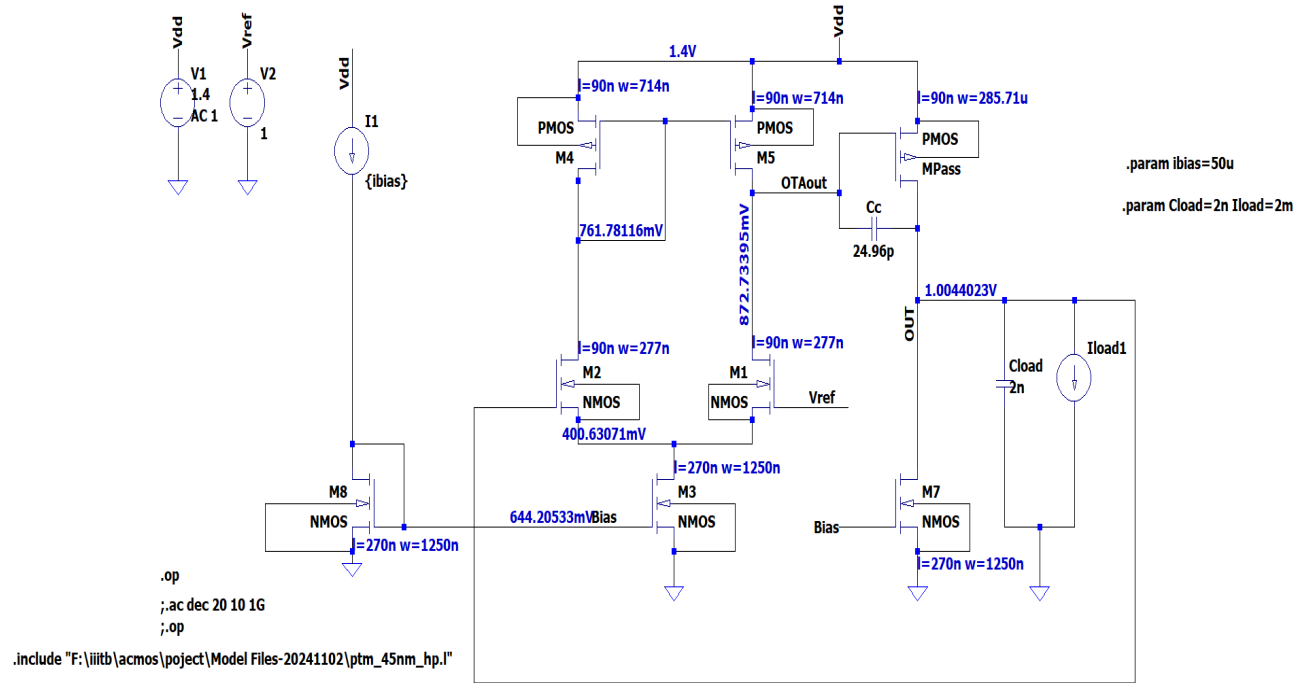


Figure 46: Schematic

Close loop psrr plots:-

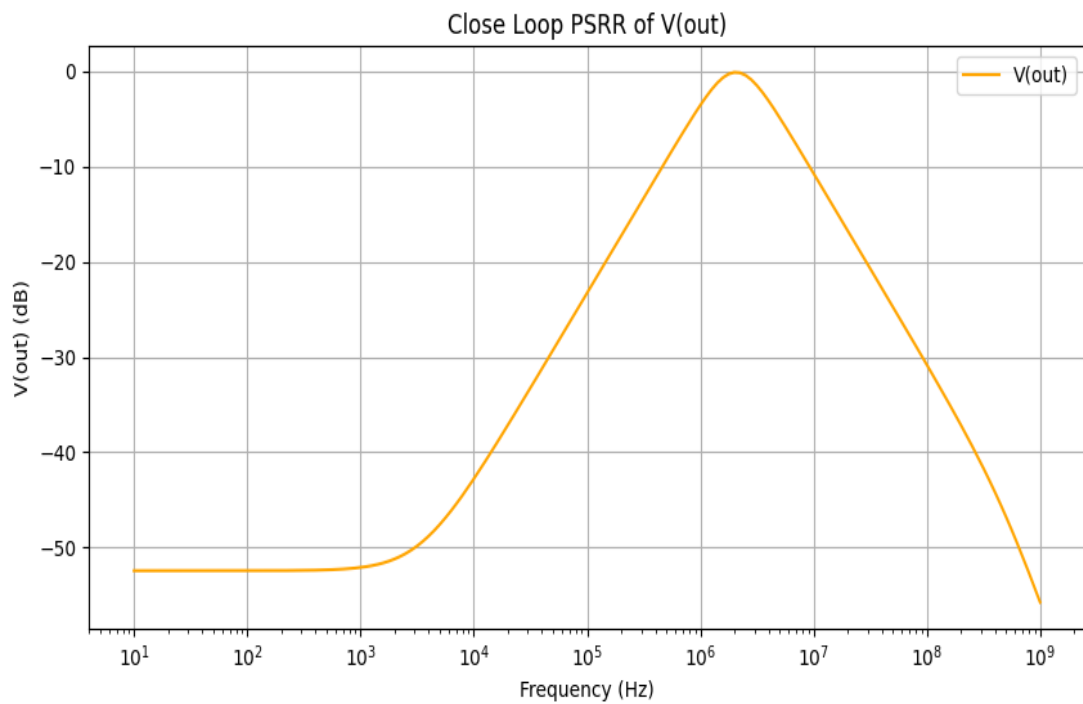


Figure 47: Close loop psrr of LDO

 


Figure 48: Close loop psrr of OTA

Heavy Load (10mA)

Schematic

Case 1:- Loop gain analysis:-

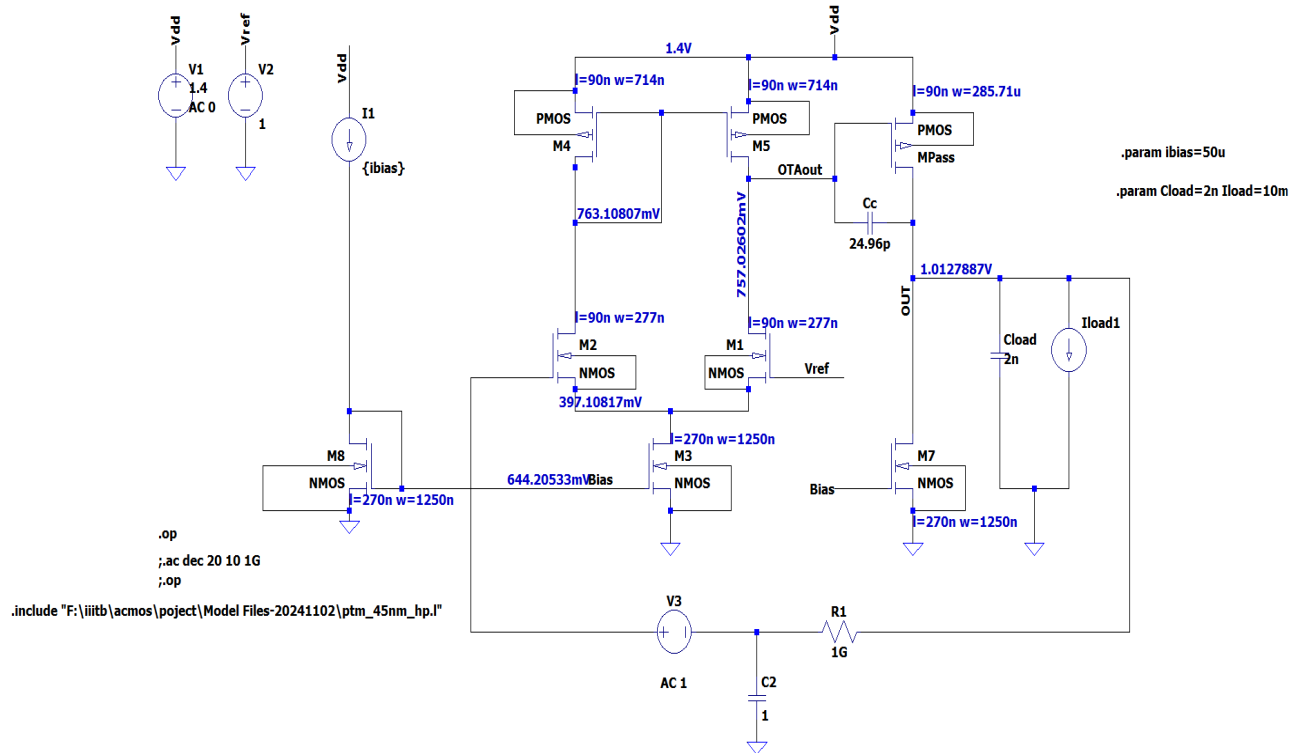


Figure 49: Schematic

Explanation of the artifact used:-

Output Log File:-

```

LTspice 24.0.12 for Windows
Circuit: * F:\iiiitb\acmos\project\internally_compensated\internally_compensated_1do.a
Start Time: Wed Dec 4 11:22:29 2024
solver = Normal
Maximum thread count: 8
tnom = 27
temp = 27
method = modified trap
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM4 MOSFETS ---
Name:      mpass      m5      m4      m3      m7
Model:     pmos      pmos      pmos      nmos      nmos
Id:        -1.01e-02   -2.46e-05  -2.46e-05   4.94e-05   5.08e-05
Vgs:       -6.43e-01   -6.37e-01  -6.37e-01   6.44e-01   6.44e-01
Vds:       -3.87e-01   -6.43e-01  -6.37e-01   3.97e-01   1.01e+00
Vbs:       0.00e+00   0.00e+00   0.00e+00   0.00e+00   0.00e+00
Vth:       -4.87e-01   -4.84e-01  -4.84e-01   4.69e-01   4.69e-01
Vdsat:     -1.72e-01   -1.70e-01  -1.70e-01   1.81e-01   1.82e-01
Gm:        1.02e-01   2.56e-04   2.55e-04   4.34e-04   4.46e-04
Gds:       2.54e-03   5.07e-06   5.07e-06   3.41e-06   2.03e-06
Gmb:       2.16e-02   5.40e-05   5.39e-05   1.04e-04   1.07e-04
Cbd:       1.28e-13   3.03e-16   3.03e-16   5.60e-16   4.96e-16
Cbs:       2.29e-13   5.71e-16   5.71e-16   1.00e-15   1.00e-15

Name:      m2      m1      m8
Model:     nmos      nmos      nmos
Id:        2.46e-05   2.47e-05   5.00e-05
Vgs:       6.02e-01   6.03e-01   6.44e-01
Vds:       3.66e-01   3.60e-01   6.44e-01
Vbs:       0.00e+00   0.00e+00   0.00e+00
Vth:       4.66e-01   4.66e-01   4.69e-01
Vdsat:     1.44e-01   1.44e-01   1.82e-01
Gm:        2.40e-04   2.41e-04   4.40e-04
Gds:       4.94e-06   5.03e-06   2.21e-06
Gmb:       5.55e-05   5.56e-05   1.05e-04
Cbd:       1.25e-16   1.25e-16   5.30e-16
Cbs:       2.22e-16   2.22e-16   1.00e-15

Total elapsed time: 0.077 seconds.

```

Figure 50: Output_{log} details

From the above file we can verify that all the devices are in saturation as follows:

Transistor Operating Regions Table

This document provides a table summarizing the operating regions of several transistors based on their parameters.

| Transistor | Type | V_{ds} (V) | V_{gs}/V_{sg} (V) | V_t (V) | $V_{gs}/V_{sg} - V_t$ (V) | Operating Region |
|------------|------|--------------|---------------------|-----------|---------------------------|------------------|
| M1 | NMOS | 0.360 | 0.603 | 0.466 | 0.137 | Saturation |
| M2 | NMOS | 0.366 | 0.602 | 0.466 | 0.136 | Saturation |
| M3 | NMOS | 0.397 | 0.644 | 0.469 | 0.175 | Saturation |
| M4 | PMOS | 0.637 | 0.637 | 0.484 | 0.153 | Saturation |
| M5 | PMOS | 0.643 | 0.637 | 0.484 | 0.153 | Saturation |
| MPass | PMOS | 0.387 | 0.643 | 0.487 | 0.156 | Saturation |
| M7 | NMOS | 1.01 | 0.644 | 0.469 | 0.173 | Saturation |
| M8 | NMOS | 0.644 | 0.644 | 0.469 | 0.175 | Saturation |

Table 14: Transistor Parameters and Operating Regions

Loop gain plots:-

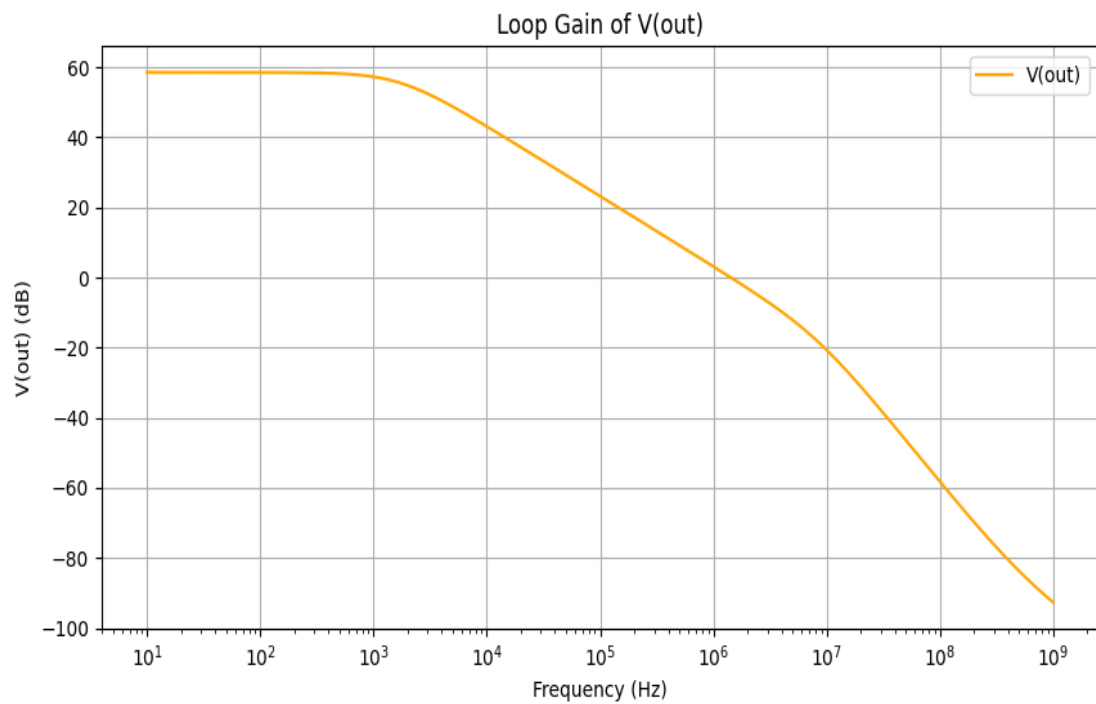


Figure 51: Loop gain of LDO

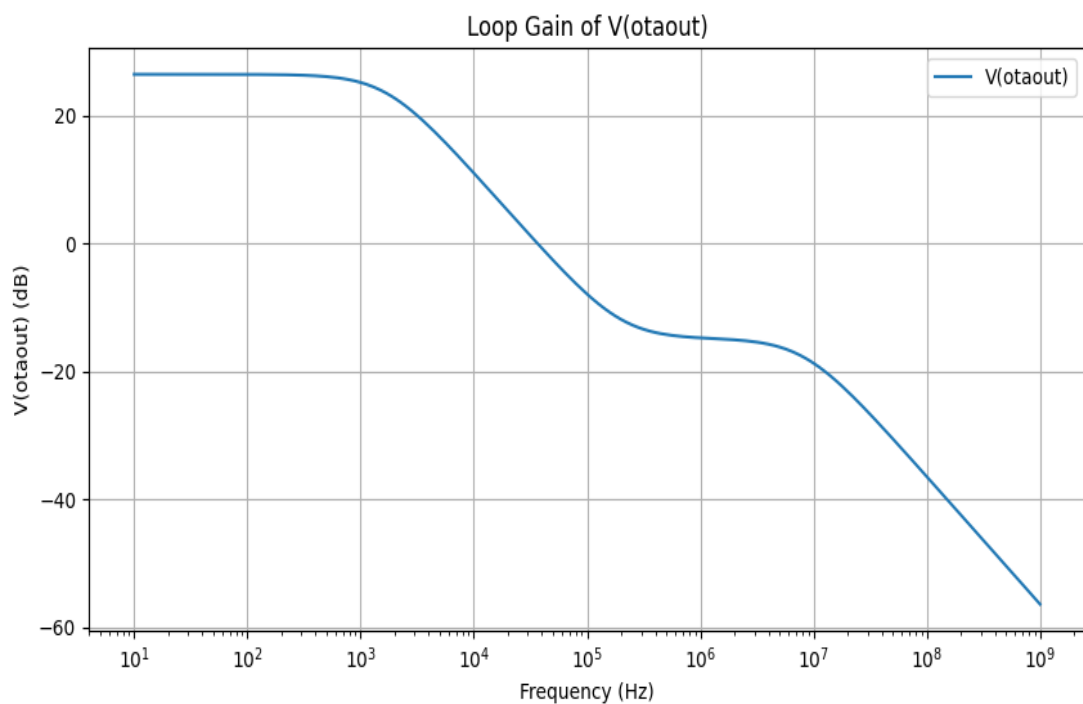


Figure 52: Loop gain of OTA

Phase margin

 


Figure 53: Phase Margin

Open loop psrr plots:-

 


Figure 55: Open Loop PSRR of LDO


 


Figure 56: Open Loop PSRR of OTA

Schematic

 

lose loop psrr plots:-

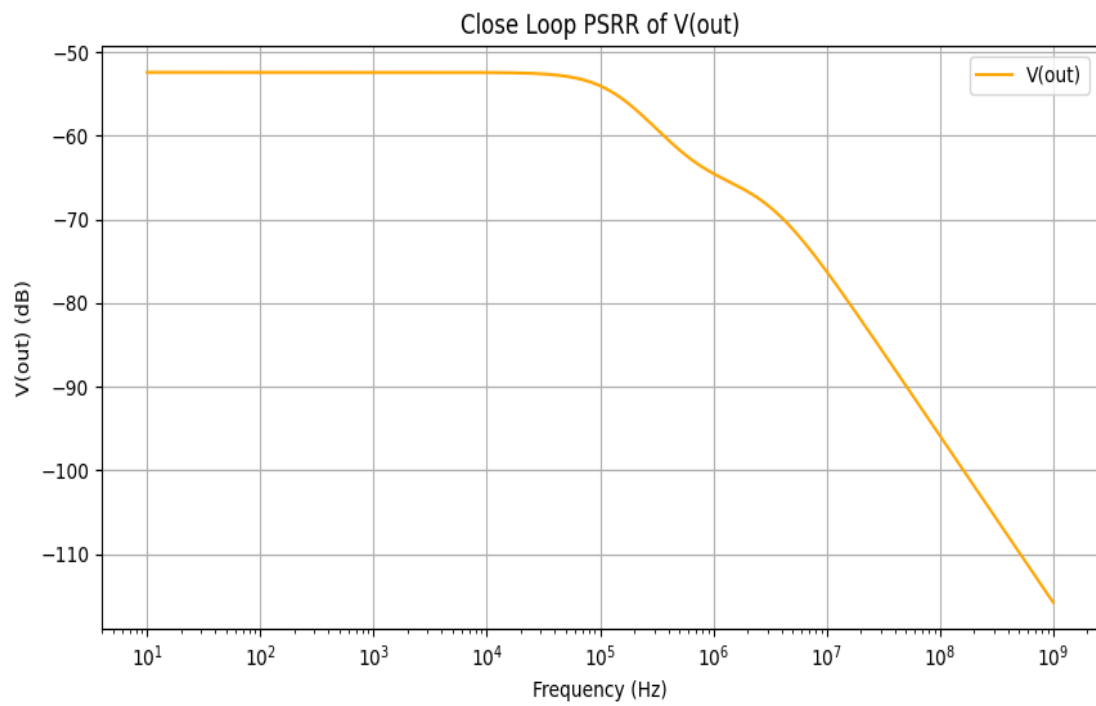


Figure 58: Close loop psrr of LDO

 


Figure 59: Close Loop PSRR of OTA

Transient Analysis

Schematic

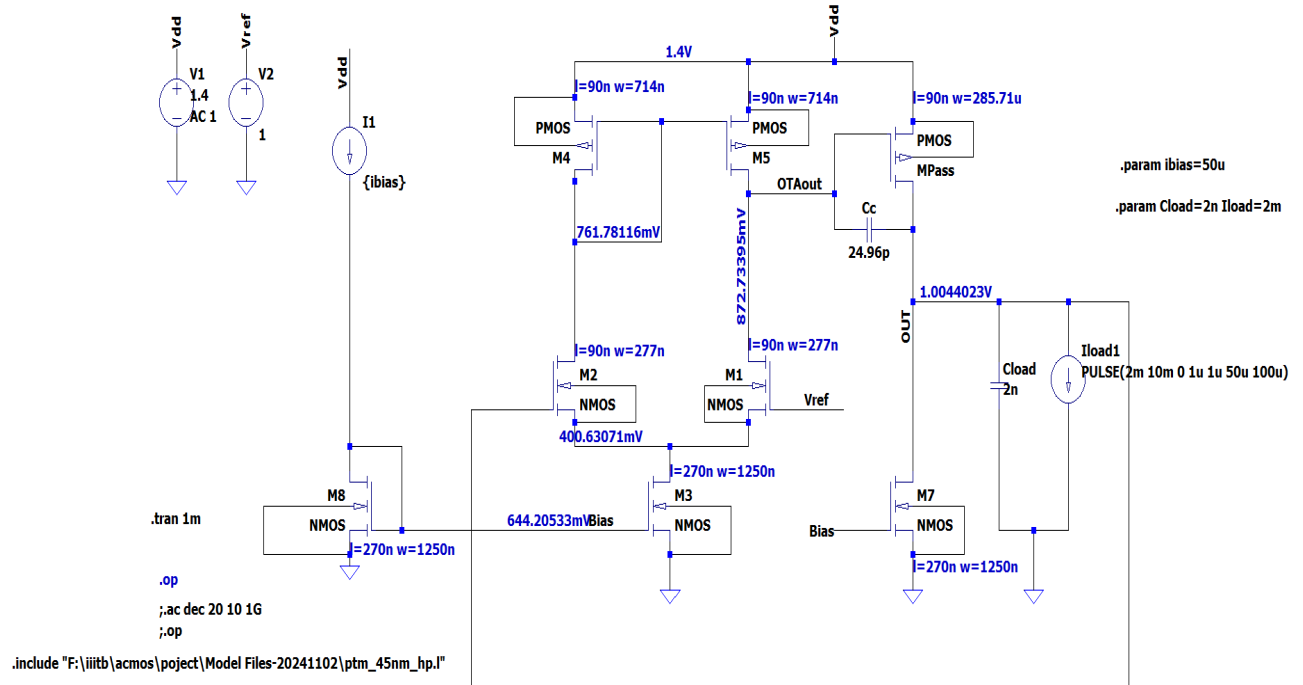


Figure 60: Schematic

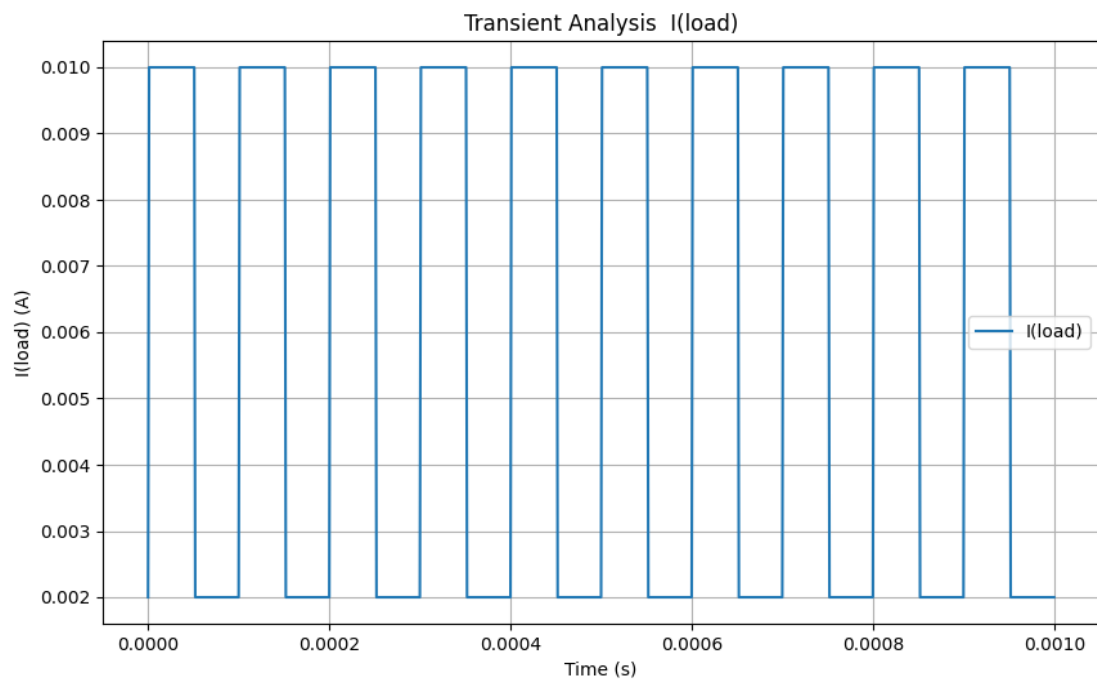
Iload Vs Time

Figure 61: Iload Vs Time

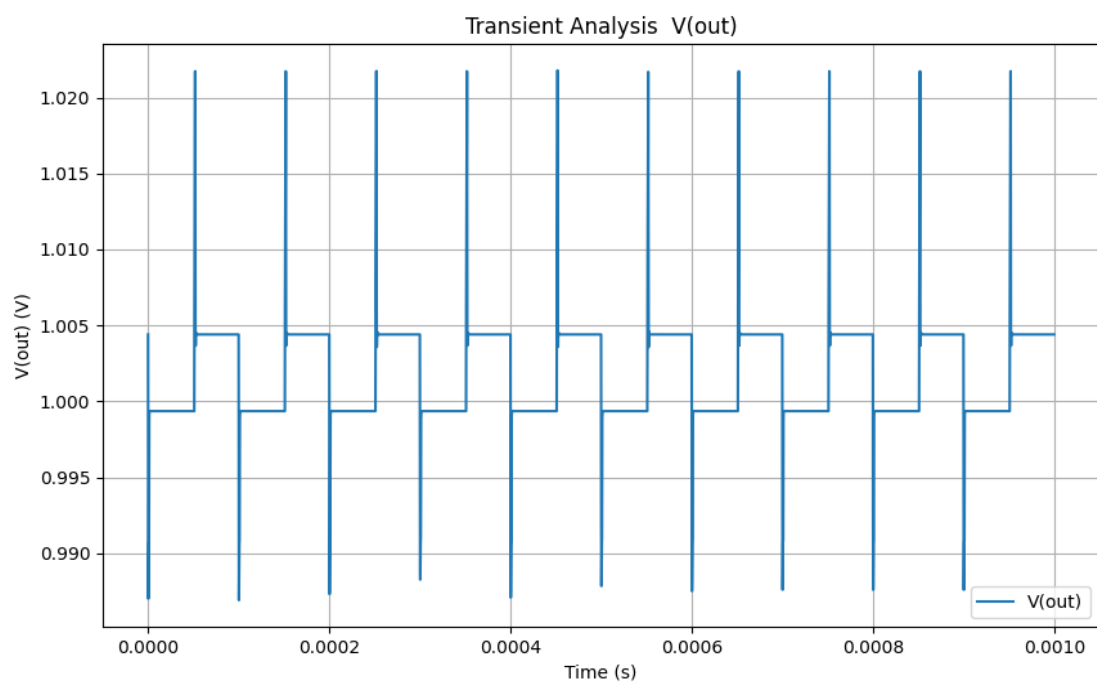
Vout Vs Time

Figure 62: Vout Vs Time

Simulation vs. Hand Calculations

For Passfet HEAVY LOAD

Hand Calculation

- $r_o = 500 \Omega$
- $g_m = 0.1 \text{ A/V}$
- W_{p1} (first pole location) = 9.94k
- $g_m r_o = 50$
- $C_{gg} = 0.569p$
- $C_l = 2n$
- $C_c = 24.96p$

Simulation Results from SPICE Error Log:

- $r_o = 1/g_{ds} = 393 \Omega$
- $g_m = 0.102 \text{ A/V}$
- W_{p1} (first pole location) = 10.04k
- $g_m r_o = 40.086$

Table 15: Hand Calculation vs Simulation Results

| Parameter | Hand Calculation | Simulation Result | % Difference |
|-------------------|------------------|-------------------|--------------|
| r_o (ohm) | 500.00 | 390 | 22.0% |
| g_m (A/V) | 0.1 | 0.102 | 1.9% |
| $g_m * r_o$ | 50 | 40.15 | 19.7% |
| W_{p1} (Hz) | 9.94k | 10.04k | 1.01% |
| W_{p2} (Hz) | 50M | 51M | 1.9% |
| W_{ugb} (Hz) | 9.94M | 10.04M | 1.01% |
| r_{odiff} (ohm) | 80k | 98.619k | 57.8% |
| g_{mdiff} (A/V) | 250u | 256u | 2.4% |

| max width= | | | | | | | | |
|--------------|-----------|-----------|-----------|----------|----------|----------|----------|----------|
| Name | mpass | m5 | m4 | m3 | m7 | m2 | m1 | m8 |
| Model | pmos | pmos | pmos | nmos | nmos | nmos | nmos | nmos |
| Id | -1.01E-02 | -2.46E-05 | -2.46E-05 | 4.94E-05 | 5.08E-05 | 2.46E-05 | 2.47E-05 | 5.00E-05 |
| Vgs | -6.43E-01 | -6.37E-01 | -6.37E-01 | 6.44E-01 | 6.44E-01 | 6.02E-01 | 6.03E-01 | 6.44E-01 |
| Vds | -3.87E-01 | -6.43E-01 | -6.37E-01 | 3.97E-01 | 1.01E+00 | 3.66E-01 | 3.60E-01 | 6.44E-01 |
| Vbs | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 |
| Vth | -4.87E-01 | -4.84E-01 | -4.84E-01 | 4.69E-01 | 4.69E-01 | 4.66E-01 | 4.66E-01 | 4.69E-01 |
| Vdsat | -1.72E-01 | -1.70E-01 | -1.70E-01 | 1.81E-01 | 1.82E-01 | 1.44E-01 | 1.44E-01 | 1.82E-01 |
| Gm | 1.02E-01 | 2.56E-04 | 2.55E-04 | 4.34E-04 | 4.46E-04 | 2.40E-04 | 2.41E-04 | 4.40E-04 |
| Gds | 2.54E-03 | 5.07E-06 | 5.07E-06 | 3.41E-06 | 2.03E-06 | 4.94E-06 | 5.03E-06 | 2.21E-06 |
| Gmb | 2.16E-02 | 5.40E-05 | 5.39E-05 | 1.04E-04 | 1.07E-04 | 5.55E-05 | 5.56E-05 | 1.05E-04 |
| Cbd | 1.28E-13 | 3.03E-16 | 3.03E-16 | 5.60E-16 | 4.96E-16 | 1.25E-16 | 1.25E-16 | 5.30E-16 |
| Cbs | 2.29E-13 | 5.71E-16 | 5.71E-16 | 1.00E-15 | 1.00E-15 | 2.22E-16 | 2.22E-16 | 1.00E-15 |
| ro | 3.94E+02 | 1.97E+05 | 1.97E+05 | 2.93E+05 | 4.93E+05 | 2.02E+05 | 1.99E+05 | 4.52E+05 |
| gm*ro | 4.02E+01 | 5.05E+01 | 5.03E+01 | 1.27E+02 | 2.20E+02 | 4.86E+01 | 4.79E+01 | 1.99E+02 |

Table 16: Transistor Parameter Table

For Passfet LIGHT LOAD

Hand Calculation

- $r_o = 2500 \Omega$
- $g_m = 0.02 \text{ A/V}$
- W_{p1} (first pole location) = 10k
- $g_m r_o = 50$
- $C_{gg} = 0.1136p$
- $C_l = 2n$
- $C_c = 24.96p$

Simulation Results from SPICE Error Log:

- $r_o = 1/g_{ds} = 1503.7 \Omega$
- $g_m = 0.0364 \text{ A/V}$
- W_{p1} (first pole location) = 7.01k
- $g_m r_o = 54.7$

Table 17: Hand Calculation vs Simulation Results

| Parameter | Hand Calculation | Simulation Result | % Difference |
|-------------------|------------------|-------------------|--------------|
| r_o (ohm) | 2500.00 | 1503.7 | 39.0% |
| g_m (A/V) | 0.02 | 0.0364 | 45% |
| $g_m * r_o$ | 50 | 54.7 | 8.5% |
| W_{p1} (Hz) | 10k | 7.70k | 23% |
| W_{p2} (Hz) | 10M | 18.2M | 45.05% |
| W_{ugb} (Hz) | 10M | 7.70M | 23 % |
| r_{odiff} (ohm) | 80k | 104.24k | 23.07% |
| g_{mdiff} (A/V) | 250u | 253u | 1.185% |

| max width= | | | | | | | | |
|--------------|-----------|-----------|-----------|----------|----------|----------|----------|----------|
| Name | mpass | m5 | m4 | m3 | m7 | m2 | m1 | m8 |
| Model | pmos | pmos | pmos | nmos | nmos | nmos | nmos | nmos |
| Id | -2.05E-03 | -2.44E-05 | -2.50E-05 | 4.94E-05 | 5.08E-05 | 2.50E-05 | 2.44E-05 | 5.00E-05 |
| Vgs | -5.28E-01 | -6.38E-01 | -6.38E-01 | 6.44E-01 | 6.44E-01 | 6.04E-01 | 5.99E-01 | 6.44E-01 |
| Vds | -3.82E-01 | -5.28E-01 | -6.38E-01 | 4.01E-01 | 1.02E+00 | 3.61E-01 | 4.72E-01 | 6.44E-01 |
| Vbs | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 | 0.00E+00 |
| Vth | -4.87E-01 | -4.86E-01 | -4.84E-01 | 4.69E-01 | 4.69E-01 | 4.66E-01 | 4.65E-01 | 4.69E-01 |
| Vdsat | -9.28E-02 | -1.70E-01 | -1.71E-01 | 1.81E-01 | 1.82E-01 | 1.45E-01 | 1.43E-01 | 1.82E-01 |
| Gm | 3.64E-02 | 2.53E-04 | 2.57E-04 | 4.34E-04 | 4.46E-04 | 2.42E-04 | 2.41E-04 | 4.40E-04 |
| Gds | 6.65E-04 | 5.30E-06 | 5.12E-06 | 3.36E-06 | 2.03E-06 | 5.06E-06 | 4.27E-06 | 2.21E-06 |
| Gmb | 7.50E-03 | 5.34E-05 | 5.43E-05 | 1.04E-04 | 1.07E-04 | 5.58E-05 | 5.56E-05 | 1.05E-04 |
| Cbd | 1.28E-13 | 3.10E-16 | 3.03E-16 | 5.59E-16 | 4.96E-16 | 1.25E-16 | 1.22E-16 | 5.30E-16 |
| Cbs | 2.29E-13 | 5.71E-16 | 5.71E-16 | 1.00E-15 | 1.00E-15 | 2.22E-16 | 2.22E-16 | 1.00E-15 |
| ro | 1.50E+03 | 1.89E+05 | 1.95E+05 | 2.98E+05 | 4.93E+05 | 1.98E+05 | 2.34E+05 | 4.52E+05 |
| gm*ro | 5.47E+01 | 4.77E+01 | 5.02E+01 | 1.29E+02 | 2.20E+02 | 4.78E+01 | 5.64E+01 | 1.99E+02 |

Table 18: Transistor Parameter Table

Stability Analysis

For Heavy load we get the following curve:

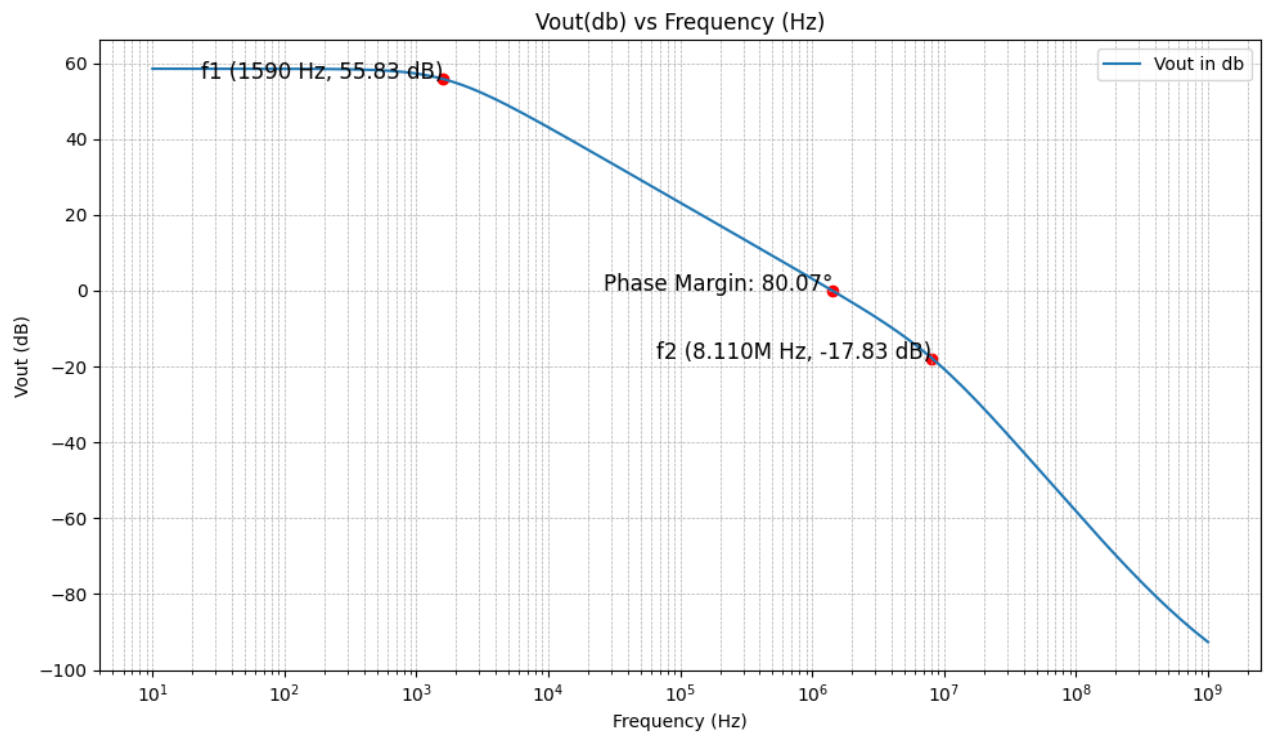


Figure 63: Pole representation

For Light load we get the following curve

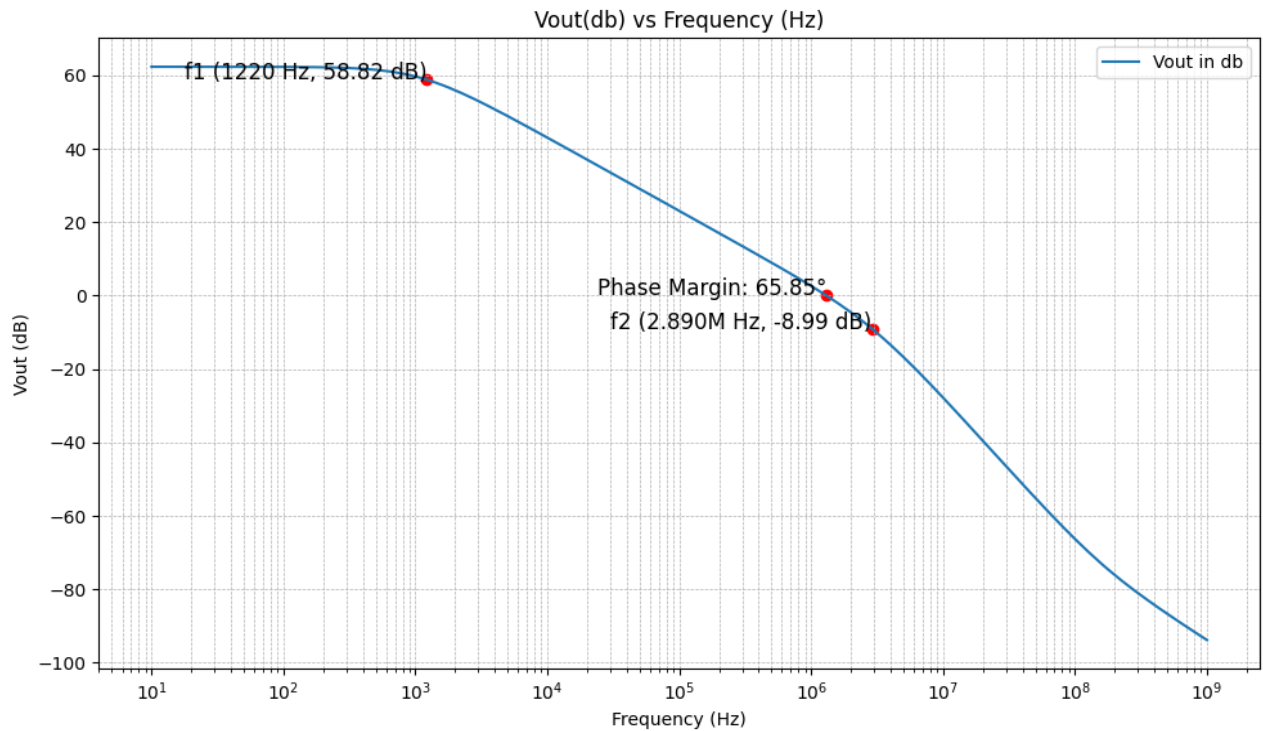


Figure 64: Pole representation

From the above analysis we can see that the unity gain bandwidth is closer to the second pole for the light load case than the heavy load case. From the phase margin also we observe a better phase margin of 80.07 degrees for the heavy load case. From this analysis, we can say that we get a more stable system when we apply heavy load.

Intersection of Subjects Studied This Semester

This semester, I had the opportunity to study subjects like ASIC, AC-MOS, DCMOS, Embedded Systems, and FPGA. Each of these fields has unique aspects, but they also overlap in concepts, techniques, and applications, particularly within the broader domains of semiconductor design, embedded hardware, and digital electronics. Below, I've outlined how these subjects intersect and complement one another:

Design and Synthesis Techniques

Subjects Involved: ASIC, FPGA

Intersection: Both ASIC and FPGA deal with hardware synthesis, where high-level designs are transformed into functional circuits. While ASIC focuses on tools and workflows like OpenLane and OpenRoad to create custom silicon designs, FPGA emphasizes the synthesis of designs that can be implemented on reconfigurable hardware.

Transistor-Level Circuit Design

Subjects Involved: ACMOS, DCMOS, ASIC

Intersection: The principles of MOSFET-based circuit design in ACMOS and the logic gate implementations in DCMOS form the basis for ASIC development. Understanding these transistor-level designs is essential for building efficient digital and analog circuits.

Communication and Interfacing

Subjects Involved: Embedded Systems, FPGA

Intersection: Both areas involve implementing communication protocols such as UART. In Embedded Systems, these protocols are typically realized on microcontrollers like the PSoC 5, while in FPGA, they are designed for high-speed and parallel data handling.

Analog and Mixed-Signal Design

Subjects Involved: ACMOS, ASIC

Intersection: Analog circuit elements, such as amplifiers and feedback mechanisms studied in ACMOS, play a critical role in mixed-signal ASIC designs. These designs combine both analog and digital functions to create versatile electronic systems.

System-Level Integration

Subjects Involved: ASIC, FPGA, Embedded Systems

Intersection: Whether integrating components on a silicon chip (ASIC), on programmable logic (FPGA), or within microcontroller-based systems (Embedded Systems), system-level integration focuses on achieving seamless hardware-software co-design and testing.

Conclusion

The subjects I studied this semester share a significant amount of overlap, especially in their emphasis on designing, analyzing, and implementing advanced electronic systems. Together, they have provided me with a strong foundation to tackle real-world challenges in semiconductor technology and embedded systems.