

# IIIT BANGALORE

VLS 502

Analog CMOS VLSI Design

---

## Project Report

---

Submitted By:-

Bibin B Jacob- MT2024513

Utkarsh Jain- MT2024538

Vaibhav Naresh Dachewar- MT2024539

Submitted To:-

**Prof. Sakshi Arora**

Assistant Professor,  
VLSI Lab,

International Institute of Information Technology - Bangalore

# Externally compensated LDO

## 1. Specifications

In this project we have designed an LDO subject to different conditions. For this design we are designing the LDO for both externally and internally compensated LDO. For the below figure we are considering 45nm technology node. Our aim is to design the LDO for a max and a min load condition.

Table 1: Specifications Summary

Parameter	Value
Vin	1.4V
Vout	1V
PSRR	60dB
Iload (min)	2mA
Iload (max)	10mA
Cload	1uF
Iquiescent	50uA
Transient duration	1u

## 2. Purpose of an LDO

Low Drop-Out (LDO) regulators are critical components in Very Large Scale Integration (VLSI) circuits, where the demand for stable power supply is paramount due to the increasing complexity and sensitivity of integrated circuits. In VLSI applications, LDOs help maintain consistent voltage levels, which is essential for the reliable operation of digital, analog, and mixed-signal components within a chip.

### Key Purposes of an LDO

- **Voltage Regulation:** Maintains a stable output voltage despite variations in input voltage or load current, ensuring consistent operation of sensitive electronic components.
- **Low Noise Power Supply:** Provides clean, low-ripple power, which is essential for noise-sensitive applications such as RF circuits, audio devices, and ADCs/DACs.
- **Load Current Stability:** Supports a range of load currents while maintaining stability, which is vital in circuits with dynamic power requirements.
- **Protection for Downstream Components:** Safeguards sensitive downstream components from voltage fluctuations and overvoltage conditions.
- **Power Efficiency at Low Dropout:** Operates efficiently when the difference between input and output voltage is minimal, reducing energy loss compared to traditional linear regulators.

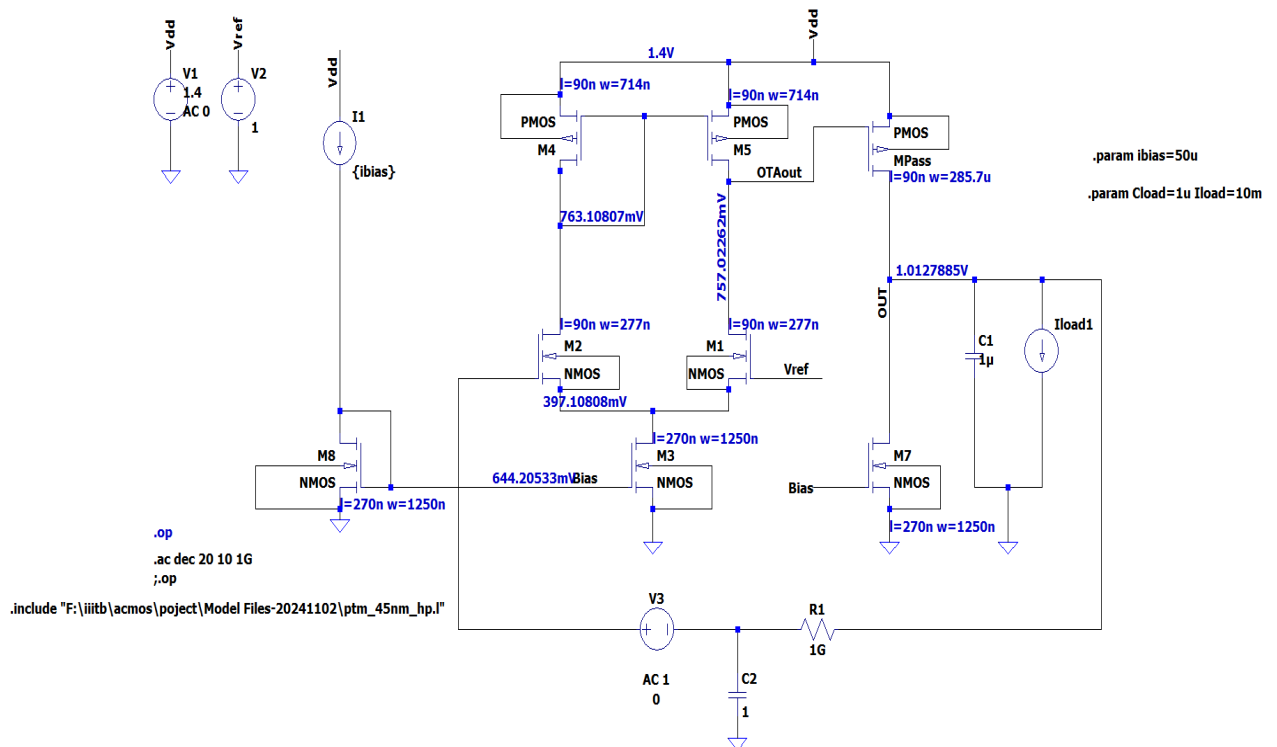


Figure 1: LDO schematic

### 3. Relevance of Techplots

We include all techplots generated.

- **Github Link:** <https://github.com/BibinBJacob/AnalogProject>  
Technology node : 45 nm
- $f_T$  improves with shorter channel lengths, making circuits faster with scaling.
- Compared to 180 nm the FOMs
- We chose the  $V_{ds}$  to be 0.4 mV, and we expect that to result in some error because the  $V_{ds}$  across every MOSFET might not be the same after sizing the circuit under a particular load. It is very possible that the  $V_{ds}$  across the MOSFETs can change under different values of load current. The above phenomenon can be understood from the output log files mentioned below.

### NMOS Techplots

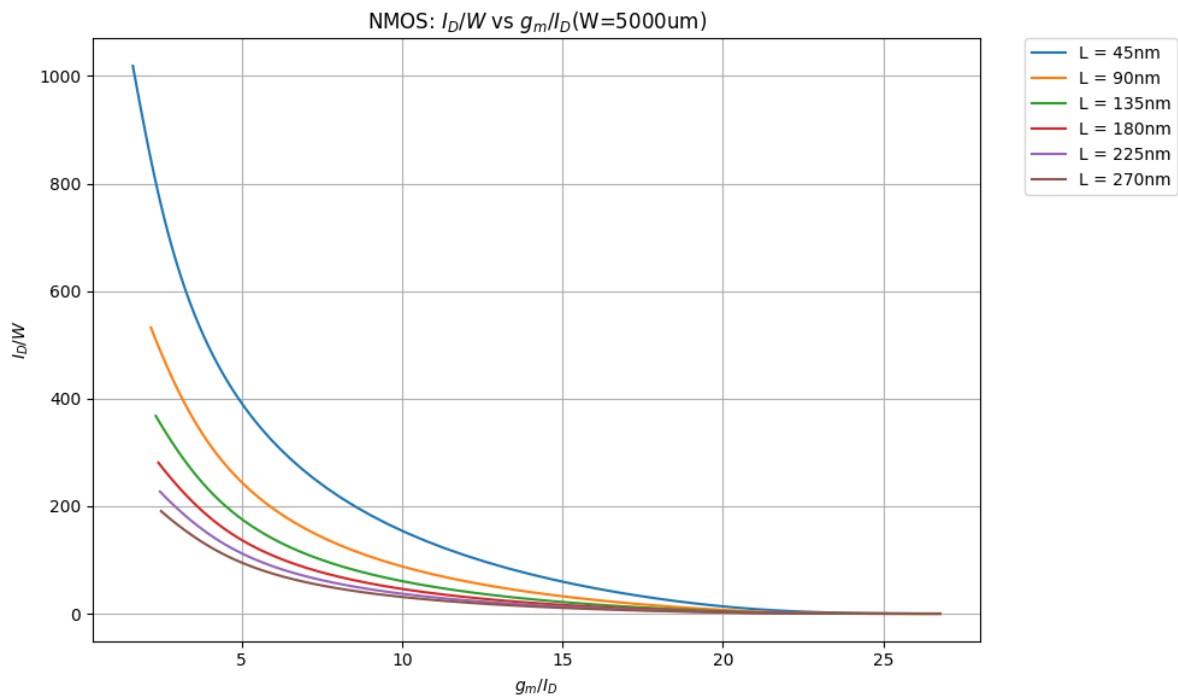
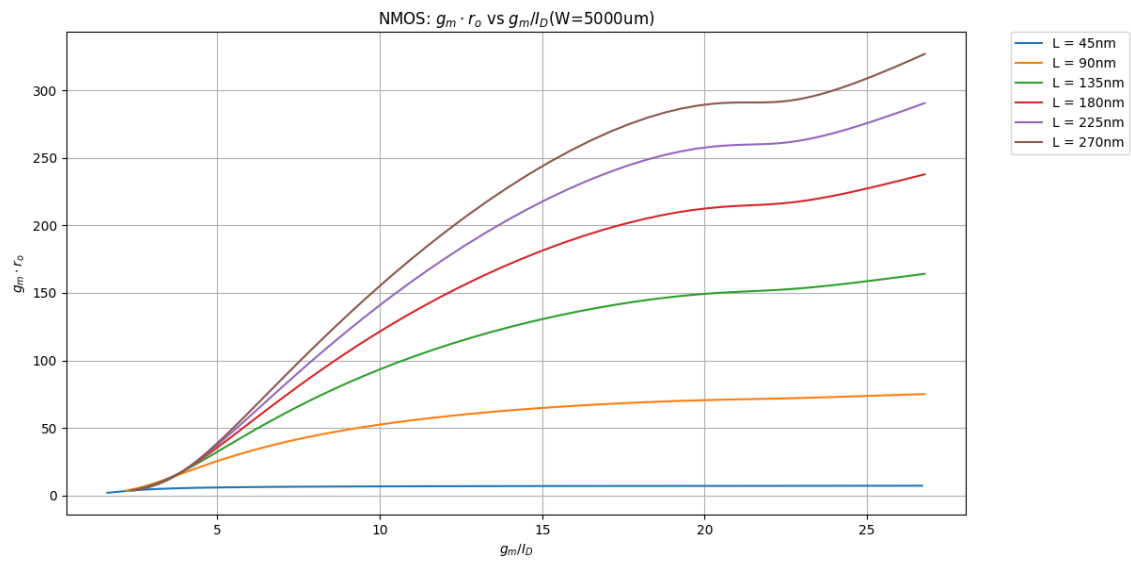
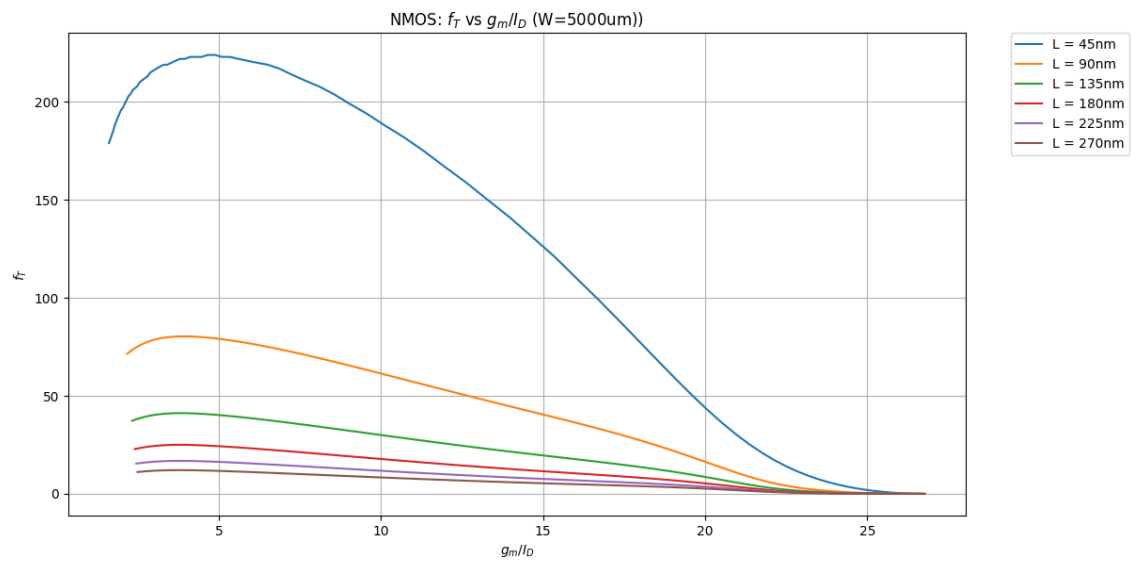


Figure 2:  $I_D/W$  vs  $g_m/I_D$

Figure 3:  $gmro$  vs  $gm/Id$ Figure 4:  $f_T$  vs  $gm/Id$

## PMOS Techplots

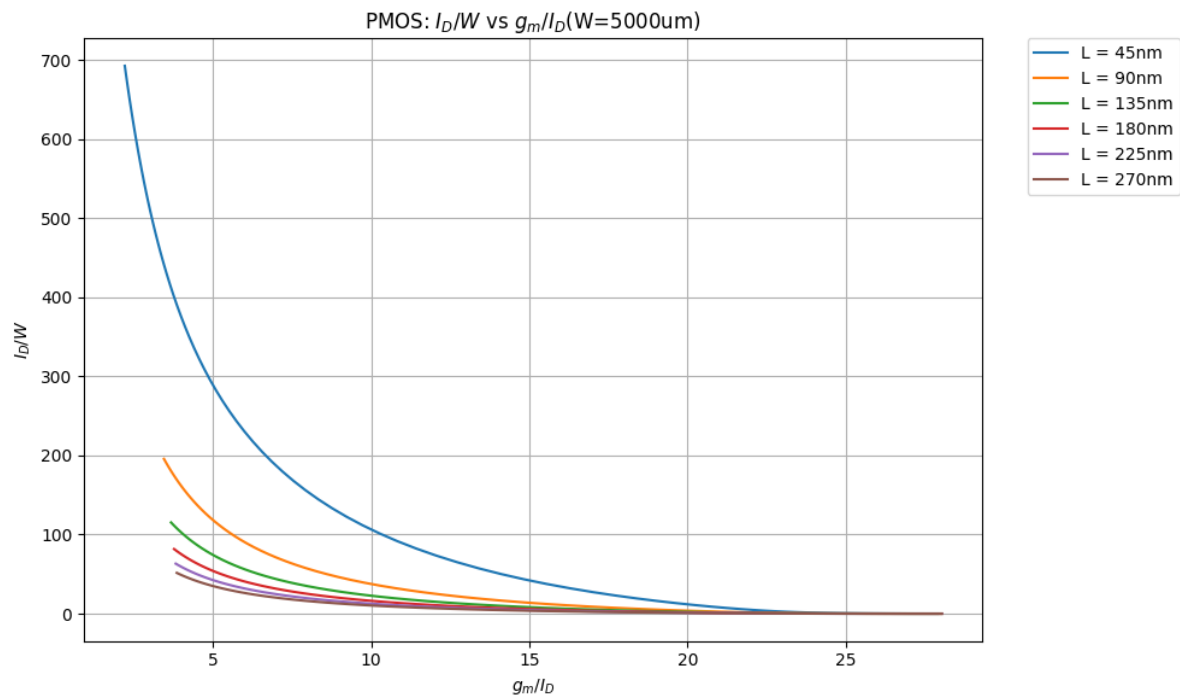


Figure 5:  $I_D/W$  vs  $g_m/I_D$

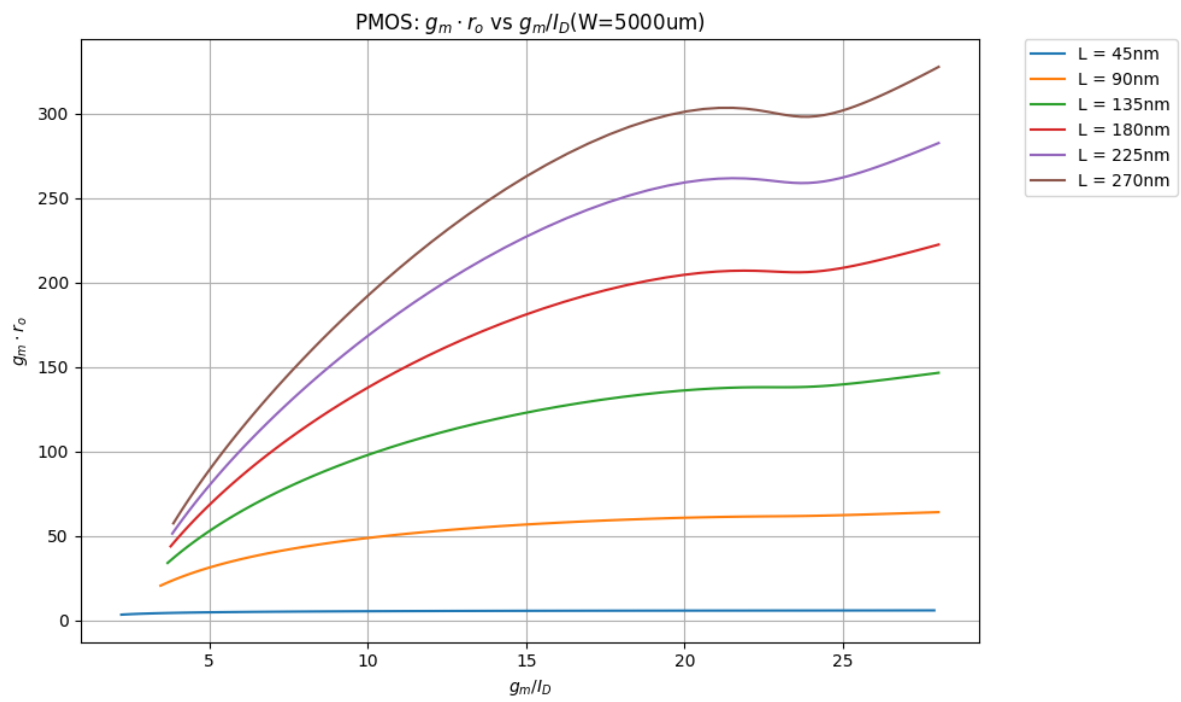


Figure 6: gmro vs gm/Id


Figure 7:  $f_T$  vs  $g_m/I_D$ 

Table 2: Key Differences Between 180nm and 45nm Technology Nodes for NMOS

Parameter	180nm Technology Node	45nm Technology Node
gmro	20	7
$I_d/W$ ( $\mu A/\mu m$ )	28	154
$f_T$ (Hz)	$1.6 \times 10^{10}$	$19 \times 10^{10}$

Table 3: Observations on Technology Scaling Effects

Parameter	Observation
gmro	As the channel length decreases, the output resistance ( $r_o$ ) decreases significantly, which dominates the intrinsic gain ( $gmro$ ). As a result, the overall value of $gmro$ decreases.
$I_d/W$	With reduced channel length, the drain current ( $I_d$ ) increases due to higher mobility and lower channel resistance. Consequently, $I_d/W$ increases, which is evident from the data.
$f_T$	A decrease in channel length increases the transconductance ( $g_m$ ), which directly leads to an increase in the unity-gain cutoff frequency ( $f_T$ ). This trend is observed in the values.

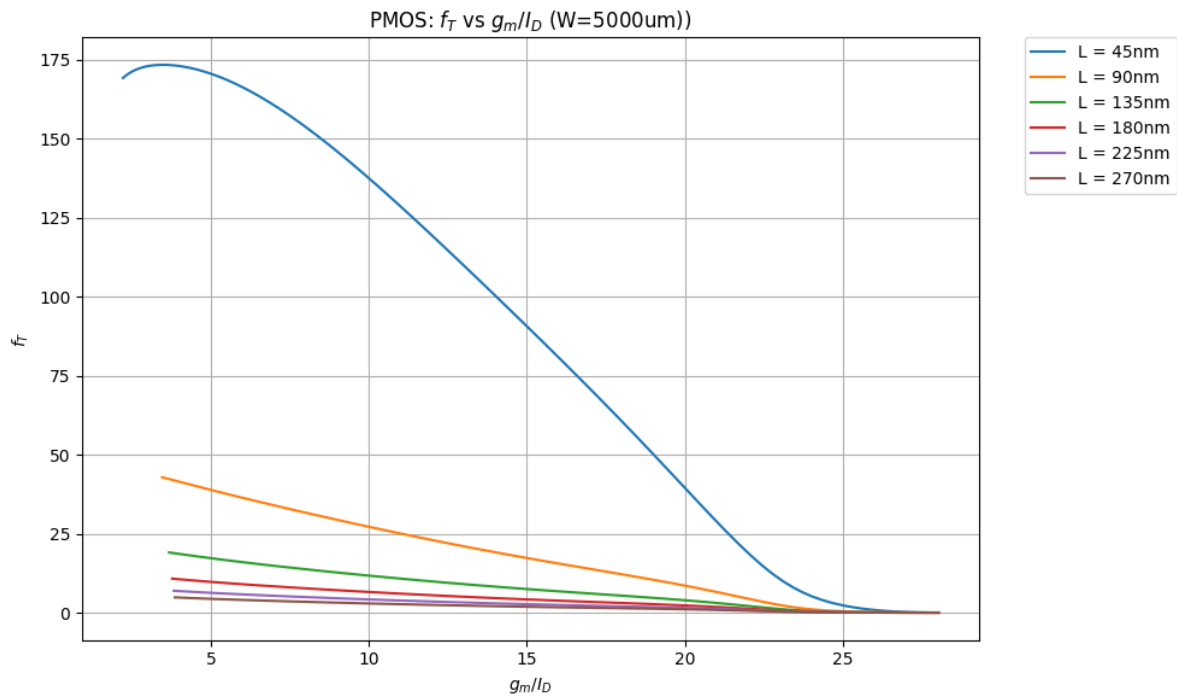

## 4. FET Sizes

We Provide the sizes of the passFET, differential amplifier, and mirror transistors. here we also Include small-signal parameters and figures of merit (FOMs). Discuss loop gain under heavy and light load conditions.

Table 4: FET Sizes and Parameters

Transistor	Size ( $W/L$ )	$g_m/I_d$	$g_m * r_o$	$I_d/W$	$f_t$
PassFET pmos	285.7u/90n	10	50	35	28 GHz
Diff-Amp pmos	714n/90n	10	40	35	28 GHz
Diff-Amp nmos	277.7n/90n	10	40	90	60 GHz
Current Mirror nmos	1250n/270n	10	154.1	40	10 GHz

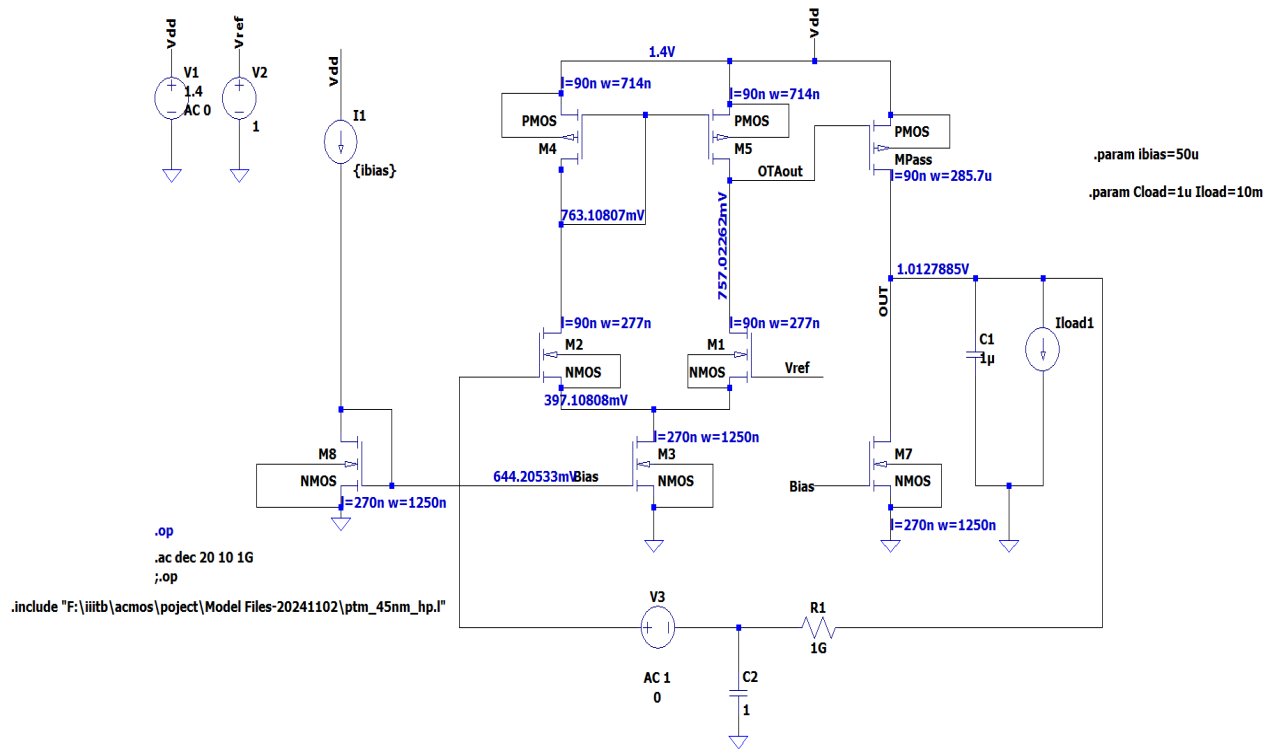


Figure 8: FET sizes and characteristics.

## 5. Stability Analysis

For Heavy load we get the following curve:

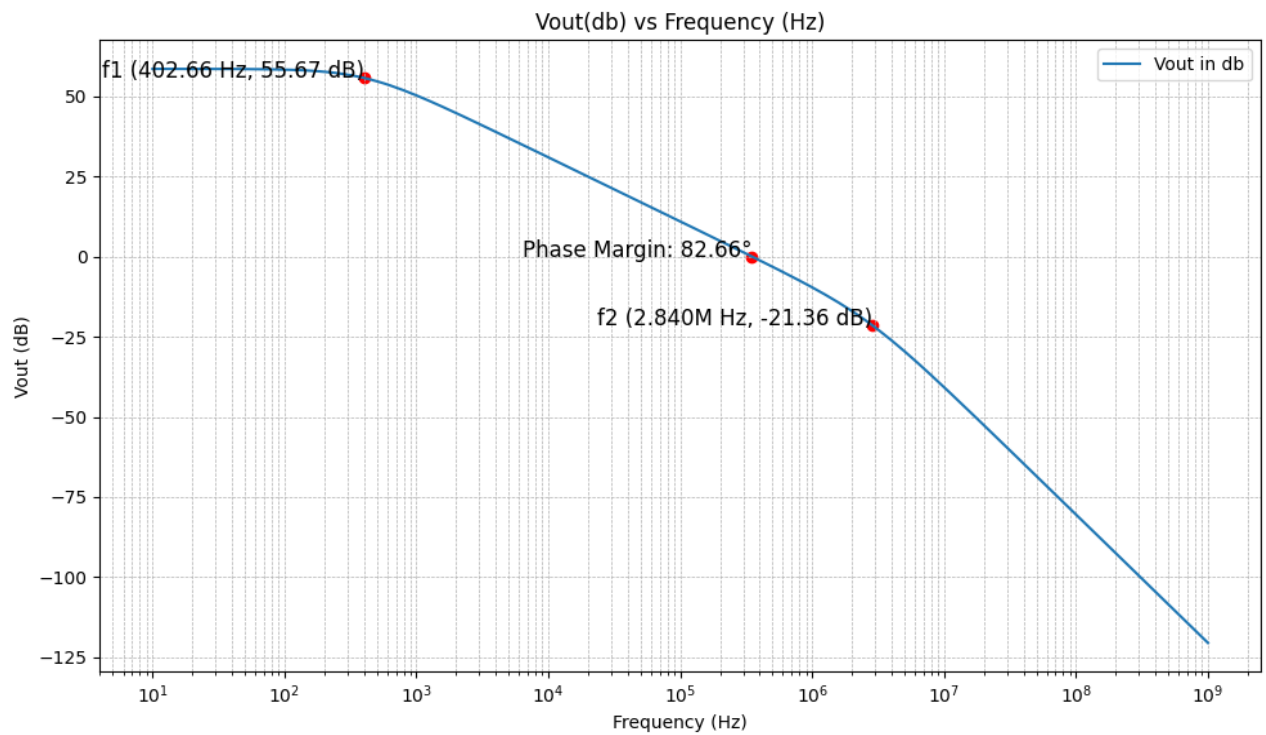


Figure 9: Pole location

For Light load we get the following curve

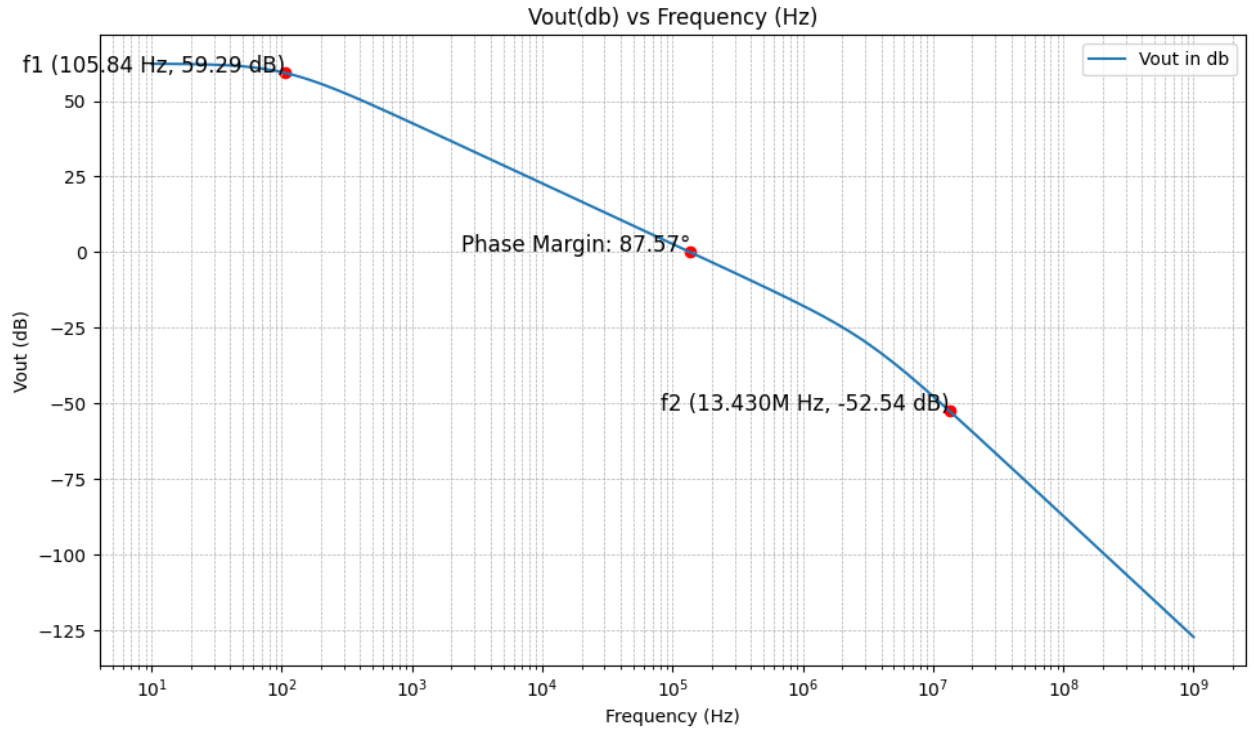


Figure 10: Pole location

From the above analysis we can see that the unity gain bandwidth is closer to the second pole for the heavy load case than the light load case. From the phase margin also we observe a smaller phase margin of 82.62 degrees for the heavy load case and 87.55 for light load case. From this analysis we can say that when we apply light load we get a more stable system.

Table 5: Key Metrics under Heavy and Light Load Conditions

Parameter	Heavy Load	Light Load
DC Loop Gain (dB)	58.52	62.30
Unity Gain Bandwidth (kHz)	402	105.8
Phase Margin (degrees)	82.62	87.55
Pole 1 (Hz)	402.6	105.8
Pole 2 (MHz)	2.84	13.43

## 6. PSRR Explanation

LDOs are essential components in the power supply of most ICs. They provide a ripple-free, stable fixed output voltage; isolating it from the input noise. An LDO has several important performance specifications and the power supply rejection ratio (PSRR) is one of them. PSRR is a quantitative measure of the attenuation of input ripples by the LDO at its output. These ripples can originate from various parts of the circuit, like DC/DC converters or shared power supplies of other circuit blocks. PSRR is expressed as  $PSRR = 20\log(v_{out}/v_{in})$ , where  $v_{out}$  and  $v_{in}$  refer to magnitudes of input and output ripples. In Figure 12, the PSRR of LDO is divided into two distinct regions (region 1 and region 2). Region 1 covers the low and mid frequency range till the regulator bandwidth frequency ( $\omega_{reg}$ ), where PSRR primarily depends on the loop gain (LG) of the regulator. Region 2 starts after  $\omega_{reg}$ , where PSRR is independent of LG and is dominated by output parasitics, PCB impedance, etc.

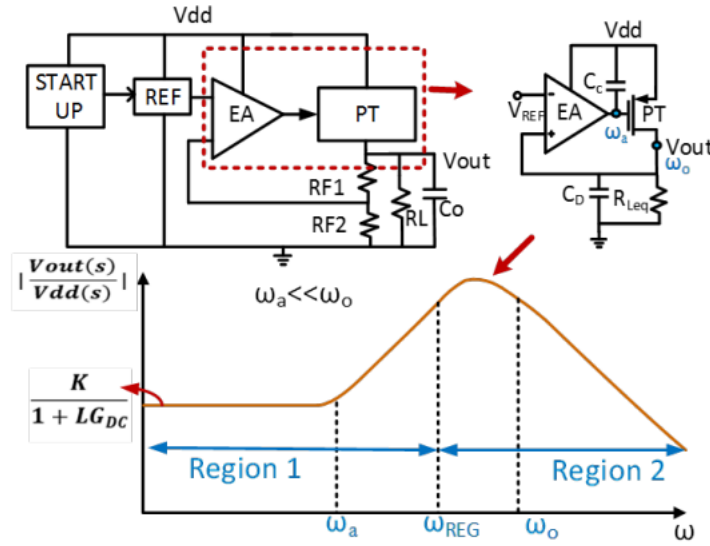


Figure 11: : Block diagram of a low drop-out (LDO) regulator and its associated PSRR curve (linear scale)

### 6 Power Supply Rejection Ratio (PSRR)

PSRR is a critical parameter in LDO design, dictating how well the regulator can suppress variations in the input supply voltage.

$$PSRR = \frac{PSRR_{OL}(s)}{1 + A_{lg}(s)} \quad (1)$$

where:

- $PSRR_{OL}(s)$  is the open-loop PSRR.
- $A_{lg}(s)$  is the loop gain of the system.

Figure 12: PSRR block diagram.

## 7. PSRR Simulation Results

we have made three schematics in LTSpice to calculate the three conditions. We have made a simulation artifact for the same.

Case 1 : Loop Gain Analysis

Case 2 : Open Loop PSRR Calculation

Case 3 : Closed Loop PSRR Calculation

### Heavy Load ( 10ma )

#### Schematic

Case 1:- Loop gain analysis:-


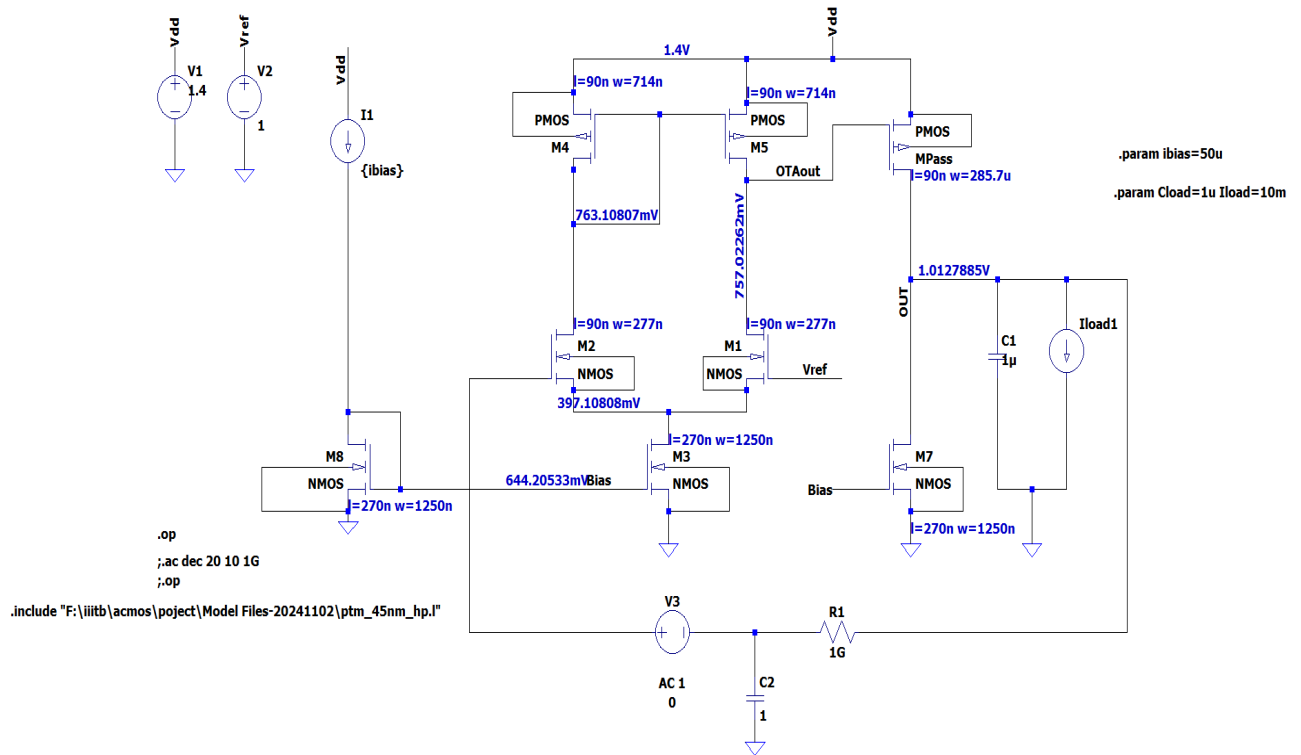


Figure 13: Schematic

#### Explanation of the artifact used:-

In order to calculate the loop gain we have given a RC circuit in the feedback loop alongwith a AC source with amplitude 1 ( as we want to maintain an AC voltage of 1V ) at the output. At the same time we also need to bias the circuit and provide a dc voltage to the gate of the nmos in the differential amplifier and for this we are giving the RC circuit which will prevent the flow of dc current to ground but will send any AC signal at the output to ground at high frequency. Also the drop across the resistor will be very less as we have given a very high resistance with very negligible current ( since current going into the gate of the mosfet is zero). Thus we will bias the circuit and also calculate the loop gain.

## Output Log File:-

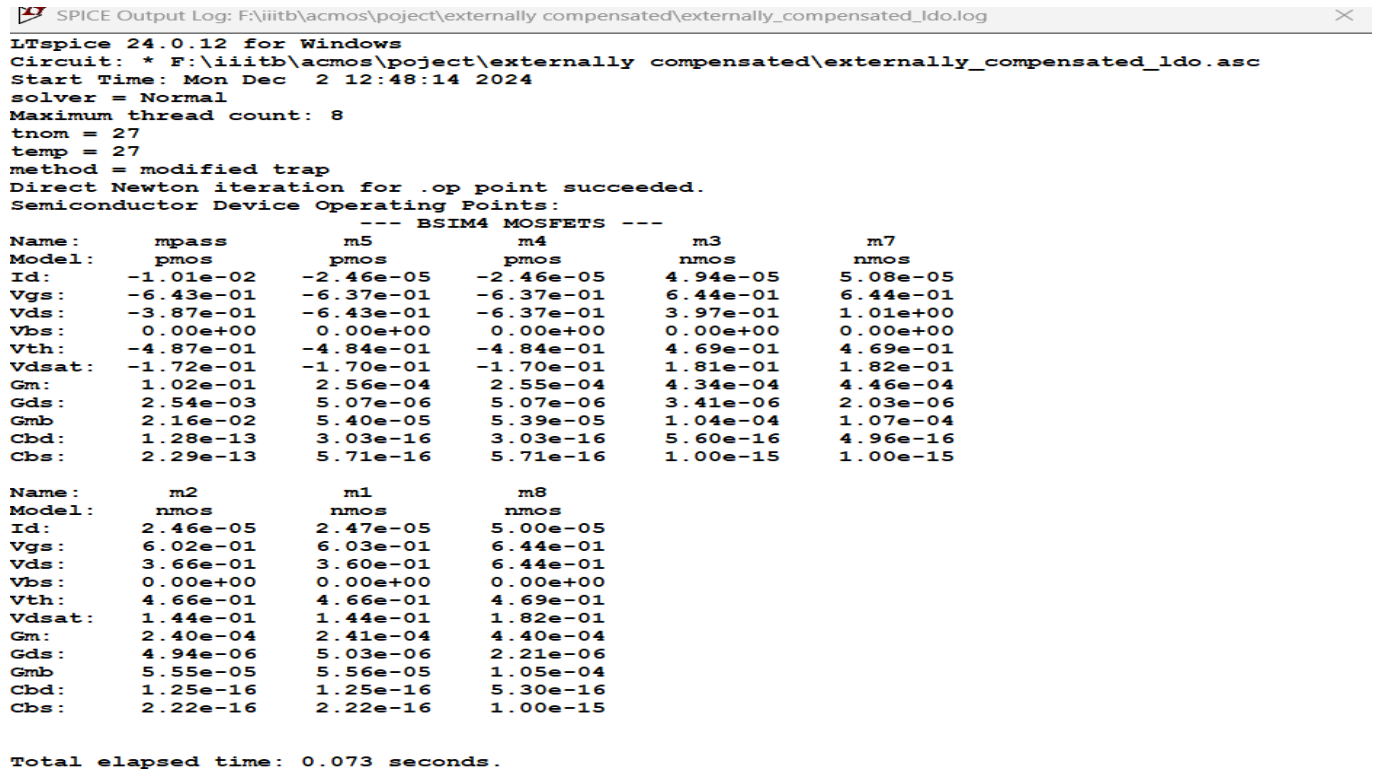

```

SPICE Output Log: F:\iiitb\acmos\project\externally compensated\externally_compensated_1do.log
LTspice 24.0.12 for Windows
Circuit: * F:\iiitb\acmos\project\externally compensated\externally_compensated_1do.asc
Start Time: Mon Dec 2 12:48:14 2024
solver = Normal
Maximum thread count: 8
tnom = 27
temp = 27
method = modified trap
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM4 MOSFETS ---
Name:      mpass      m5      m4      m3      m7
Model:      pmos      pmos      pmos      nmos      nmos
Id:         -1.01e-02  -2.46e-05  -2.46e-05  4.94e-05  5.08e-05
Vgs:        -6.43e-01  -6.37e-01  -6.37e-01  6.44e-01  6.44e-01
Vds:        -3.87e-01  -6.43e-01  -6.37e-01  3.97e-01  1.01e+00
Vbs:        0.00e+00  0.00e+00  0.00e+00  0.00e+00  0.00e+00
Vth:        -4.87e-01  -4.84e-01  -4.84e-01  4.69e-01  4.69e-01
Vdsat:      -1.72e-01  -1.70e-01  -1.70e-01  1.81e-01  1.82e-01
Gm:         1.02e-01  2.56e-04  2.55e-04  4.34e-04  4.46e-04
Gds:        2.54e-03  5.07e-06  5.07e-06  3.41e-06  2.03e-06
Gmb:        2.16e-02  5.40e-05  5.39e-05  1.04e-04  1.07e-04
Cbd:        1.28e-13  3.03e-16  3.03e-16  5.60e-16  4.96e-16
Cbs:        2.29e-13  5.71e-16  5.71e-16  1.00e-15  1.00e-15

Name:      m2      m1      m8
Model:      nmos      nmos      nmos
Id:         2.46e-05  2.47e-05  5.00e-05
Vgs:        6.02e-01  6.03e-01  6.44e-01
Vds:        3.66e-01  3.60e-01  6.44e-01
Vbs:        0.00e+00  0.00e+00  0.00e+00
Vth:        4.66e-01  4.66e-01  4.69e-01
Vdsat:      1.44e-01  1.44e-01  1.82e-01
Gm:         2.40e-04  2.41e-04  4.40e-04
Gds:        4.94e-06  5.03e-06  2.21e-06
Gmb:        5.55e-05  5.56e-05  1.05e-04
Cbd:        1.25e-16  1.25e-16  5.30e-16
Cbs:        2.22e-16  2.22e-16  1.00e-15

Total elapsed time: 0.073 seconds.

```

Figure 14: Output Log Details

From the above file we can verify that all the devices are in saturation as follows:

## Transistor Operating Regions Table

This document provides a table summarizing the operating regions of several transistors based on their parameters.

Transistor	Type	$V_{ds}$ (V)	$V_{gs}/V_{sg}$ (V)	$V_t$ (V)	$V_{gs}/V_{sg} - V_t$ (V)	Operating Region
M1	NMOS	0.36	0.602	0.466	0.136	Saturation
M2	NMOS	0.366	0.602	0.466	0.163	Saturation
M3	NMOS	0.397	0.644	0.469	0.334	Saturation
M4	PMOS	0.637	0.637	0.469	0.168	Saturation
M5	PMOS	0.643	0.637	0.484	0.159	Saturation
Mpass	PMOS	0.387	0.643	0.487	0.156	Saturation
M7	NMOS	1.01	0.644	0.469	0.541	Saturation
M8	NMOS	0.644	0.644	0.489	0.155	Saturation

Table 6: Transistor Parameters and Operating Regions

Output loop gain:-

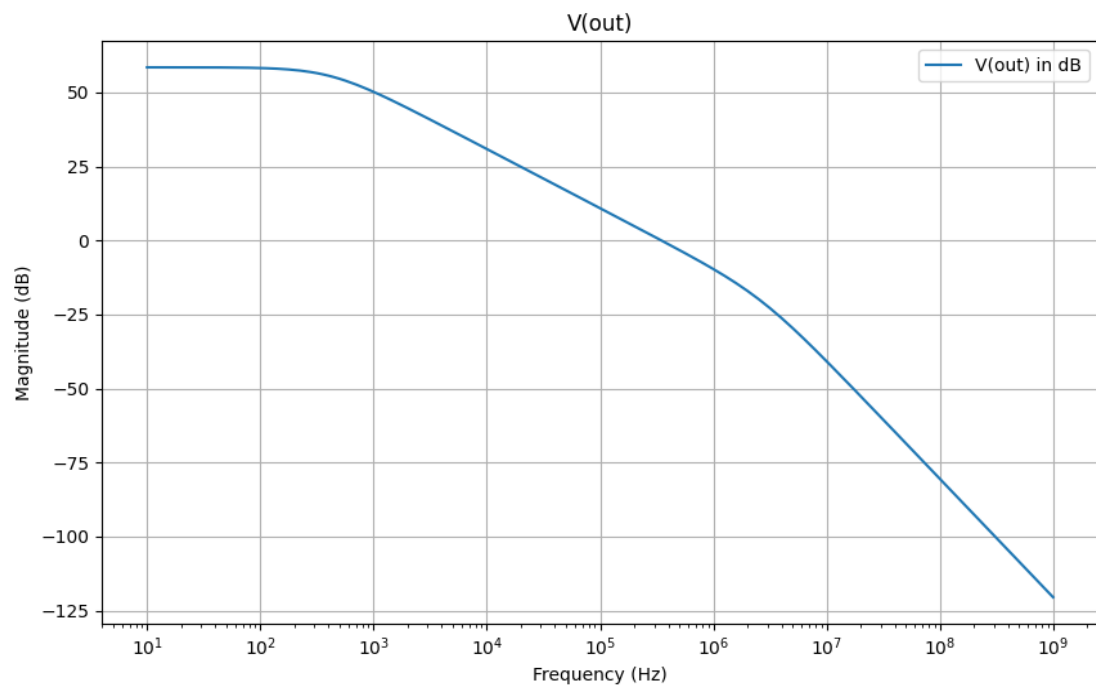


Figure 15: Output loop gain

OTA loop gain:-

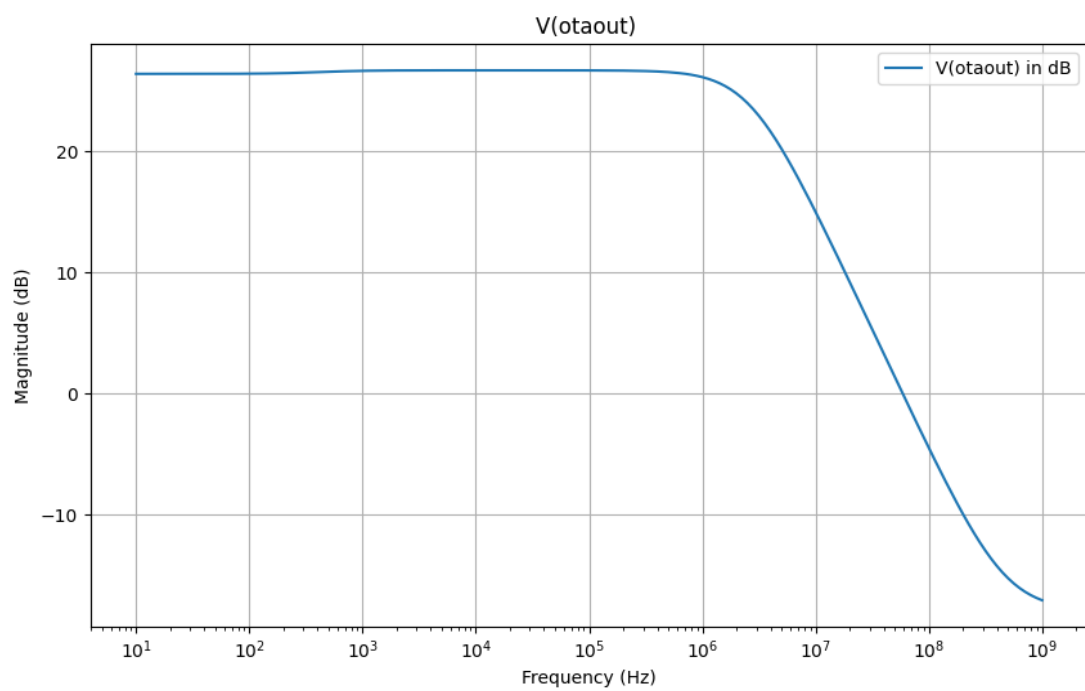


Figure 16: OTA loop gain

## Phase margin

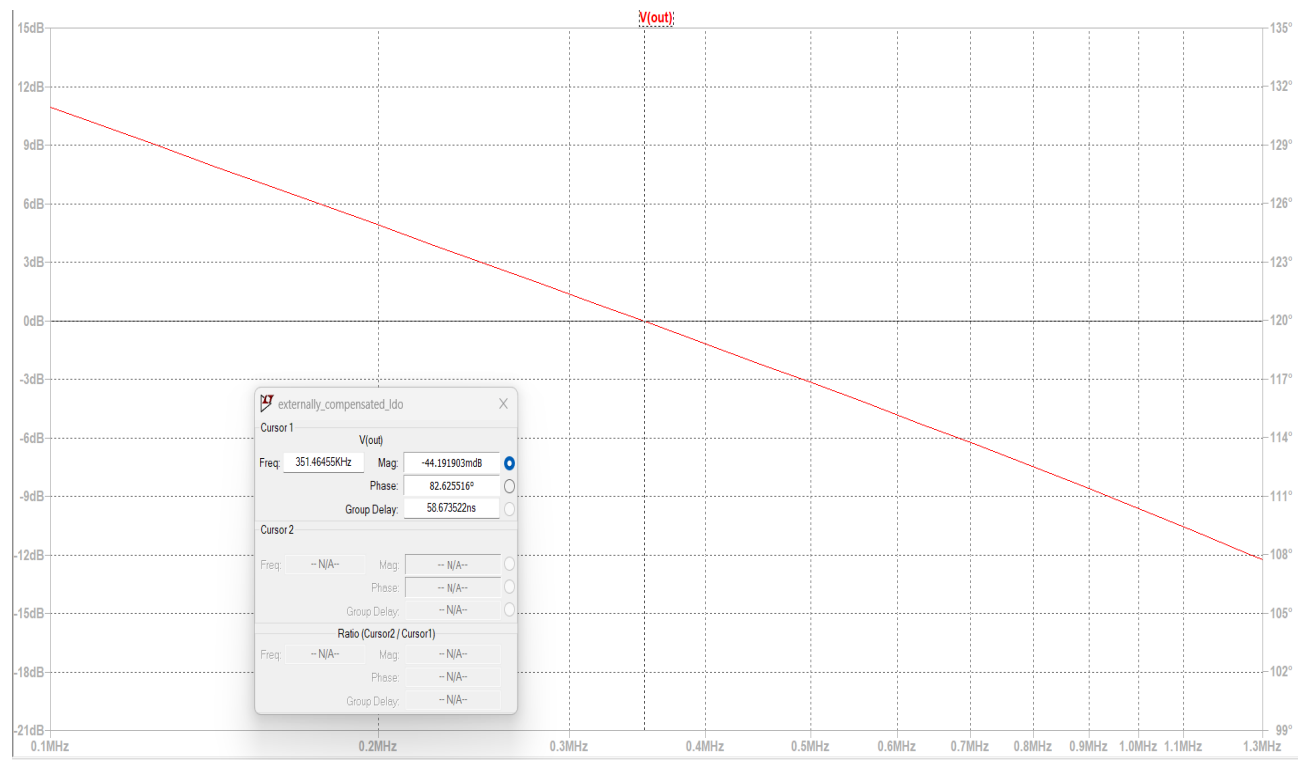


Figure 17: Phase Margin

The phase margin is 82.62

The output voltage ( Loop gain ) comes out to be close to 58.52db . The formula for loop gain is  $A_{diff} \cdot A_{pass}$  where  $A_{diff}$  is differential amplifier gain and  $A_{pass}$  is the passfet gain.



## Case 2:- Open Loop PSRR calculation

### Schematic

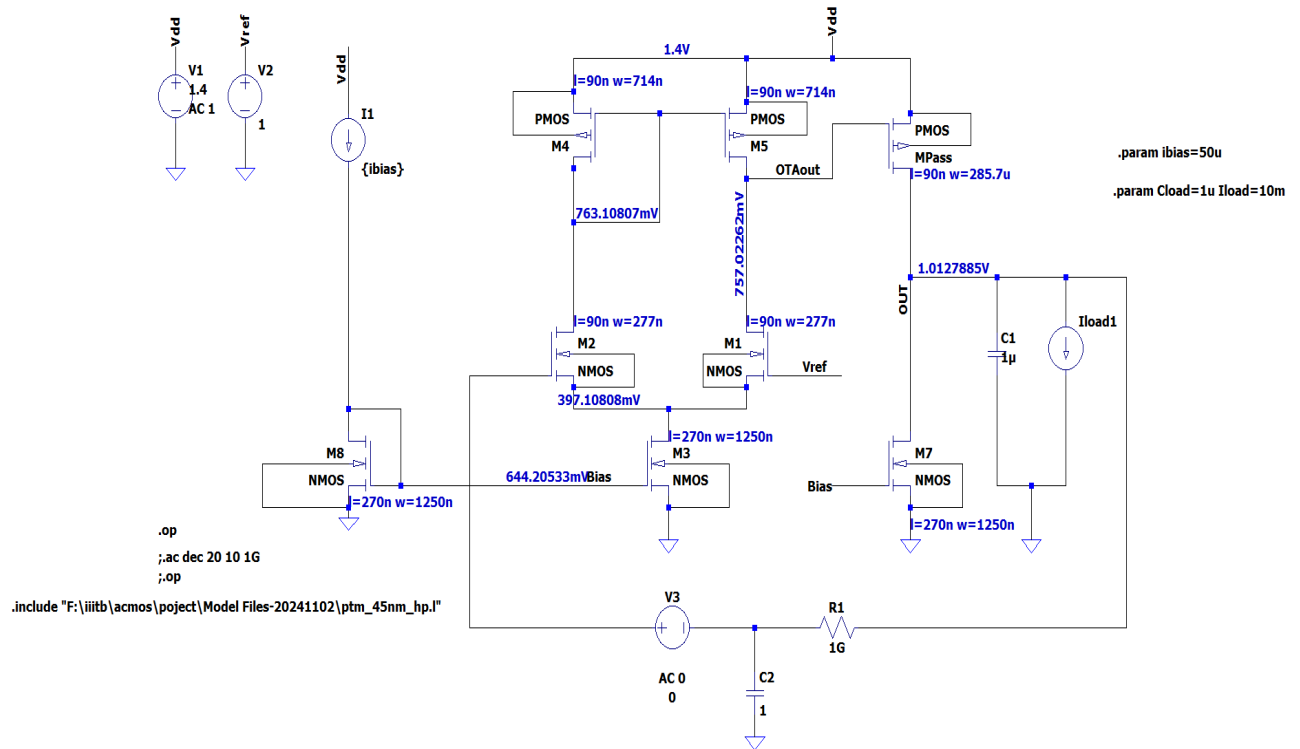


Figure 18: Schematic

### Explanation of the artifact used:-

In order to calculate the open loop PSRR we need to send an AC signal from the source which in our case is VDD. Here we are giving an AC 1 signal in the source. This signal is given to the source of the passfet and the source of pmos in the diffamp. We will ideally want very bad PSRR in the diffamp as we want the OTA output to have all the AC noise such that  $V_{sg}$  of pmos = 0 ( small signal analysis ). Thus all the noise will get rejected and we will get a noise free dc voltage at the output of the LDO. Here in order to calculate the open loop PSRR we have a RC circuit to bias the differential amplifier. You can see AC 0 in the circuit indicating that there is an open loop in the circuit . From here we have calculated the open loop PSRR in the circuit. Since there is no feedback in the circuit we can thus say that there will be noise at the output and thus the rejection will be very poor.

Open loop psrr plots:-

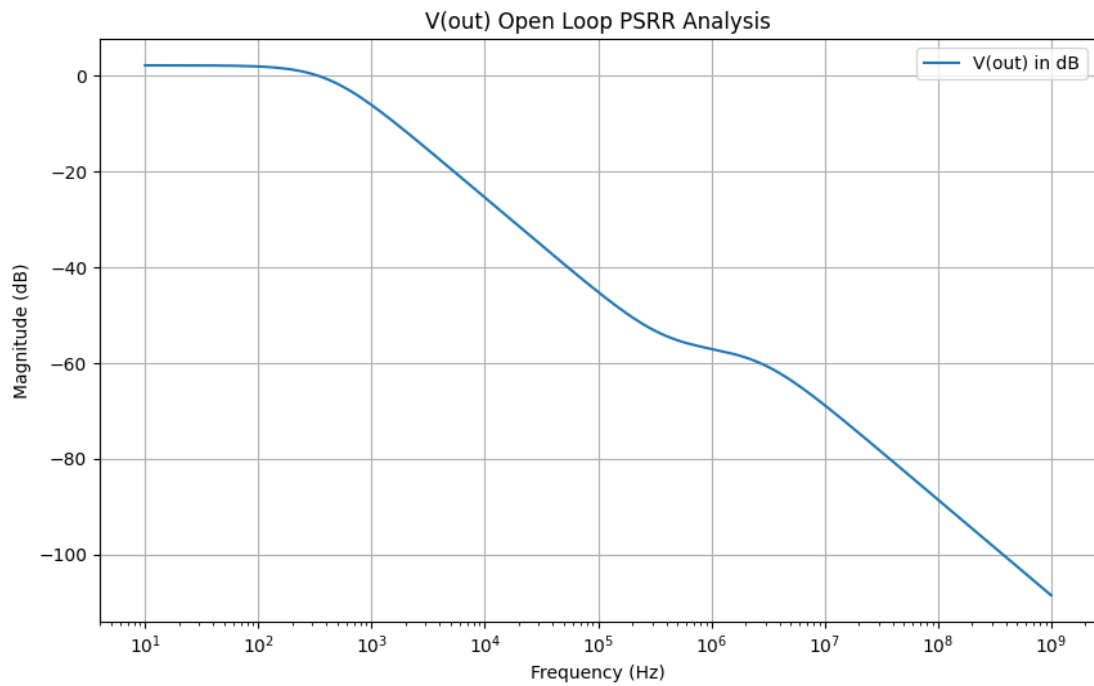


Figure 19: Open loop psrr for Output

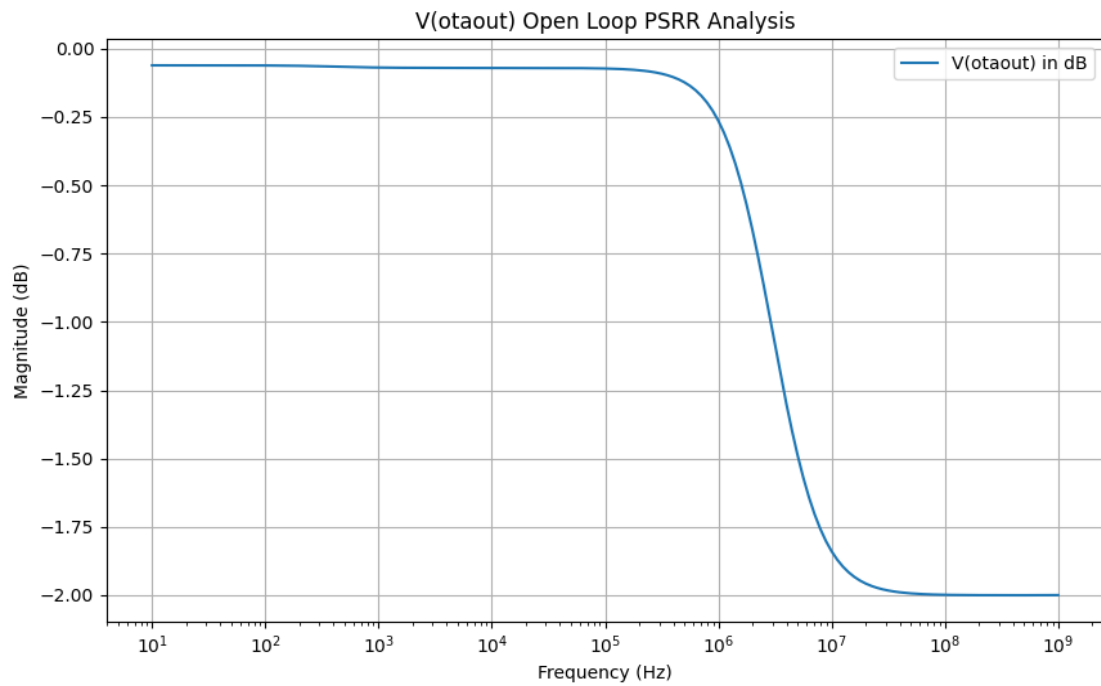


Figure 20: open loop psrr for OTA

### Case 3:- Closed Loop PSRR Calculation

The circuit schematic shows a 1.4V CMOS OTA. The PMOS current mirror consists of M4 and M5, with a tail current source I1. The NMOS current mirror consists of M2 and M1, with a tail current source I1. The output node OUT is connected to a load capacitor C1 and a load current source Iload1. The circuit is simulated with a 1.4V supply and a 10mV input signal.

Simulation results are shown in the table below:

Node	Voltage (mV)
Vdd	1.4
Vref	1.4
I1	763.10402
M4	763.10402
M5	757.35182
M2	397.11902
M1	397.11902
M8	644.20533
M3	644.20533
OUT	999.35549

Simulation parameters:

```

.param ibias=50u
.param Cload=1u Iload=10m
.op
;ac dec 20 10 1G
;op

```

Include file: "F:\iitb\acmos\project\Model Files-20241102\ptm\_45nm\_hp.l"

Explanation of the artifact used:-

19

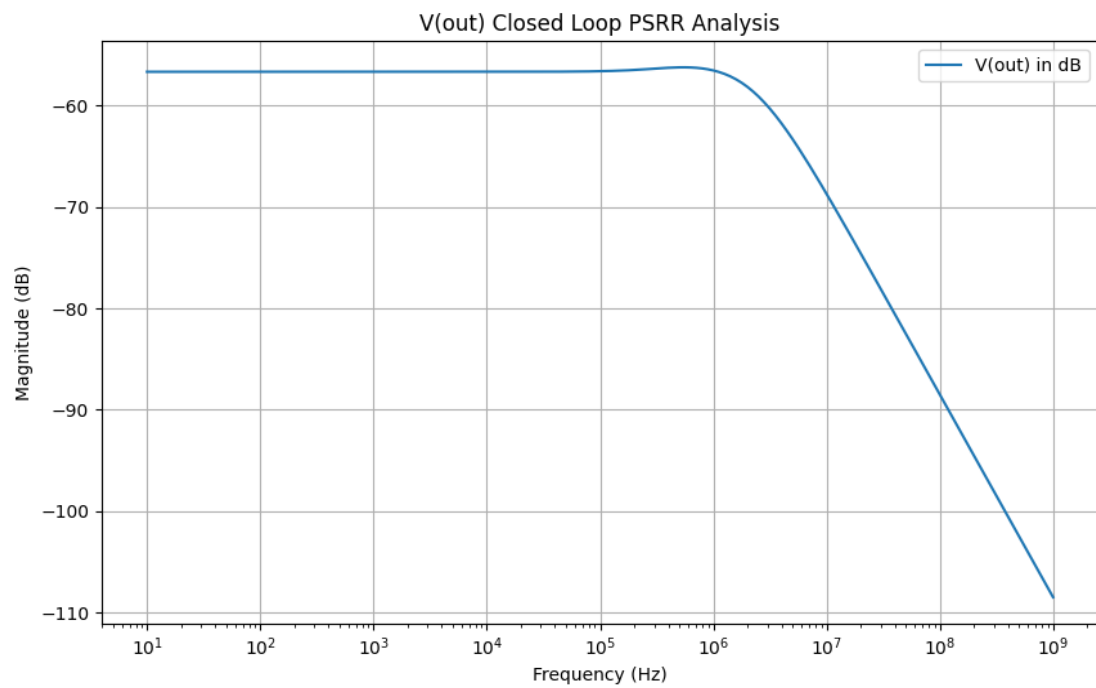
**Close loop PSRR:-**

Figure 22: close loop psrr for output

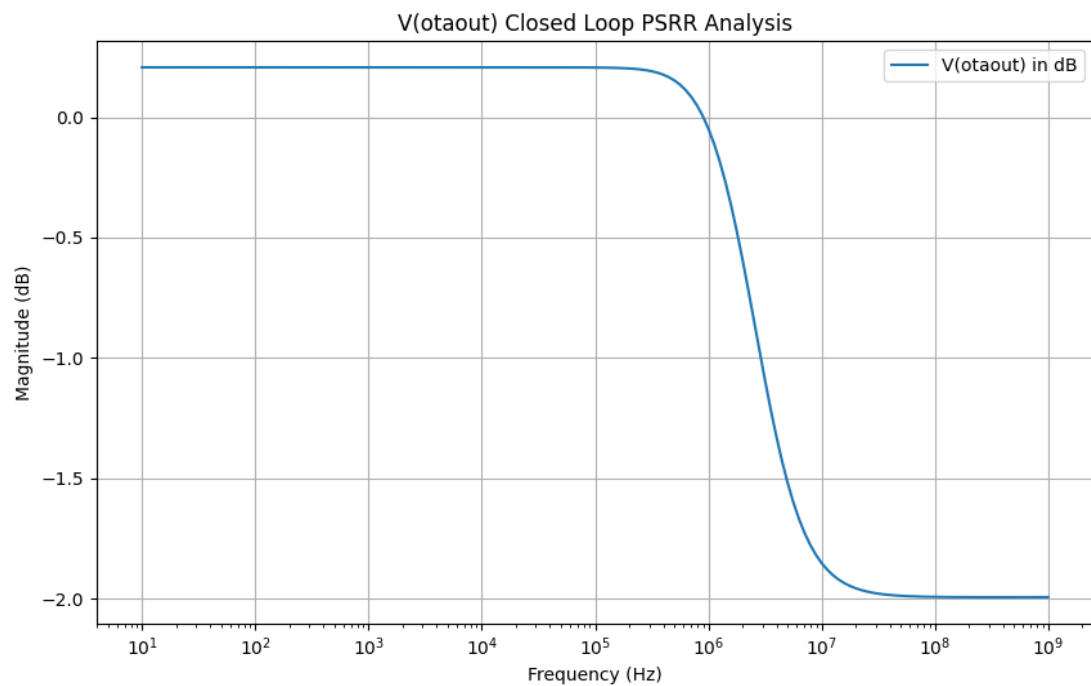


Figure 23: close loop psrr for OTA

Light Load ( 2ma )

### Case 1:- Loop gain analysis

## Schematic


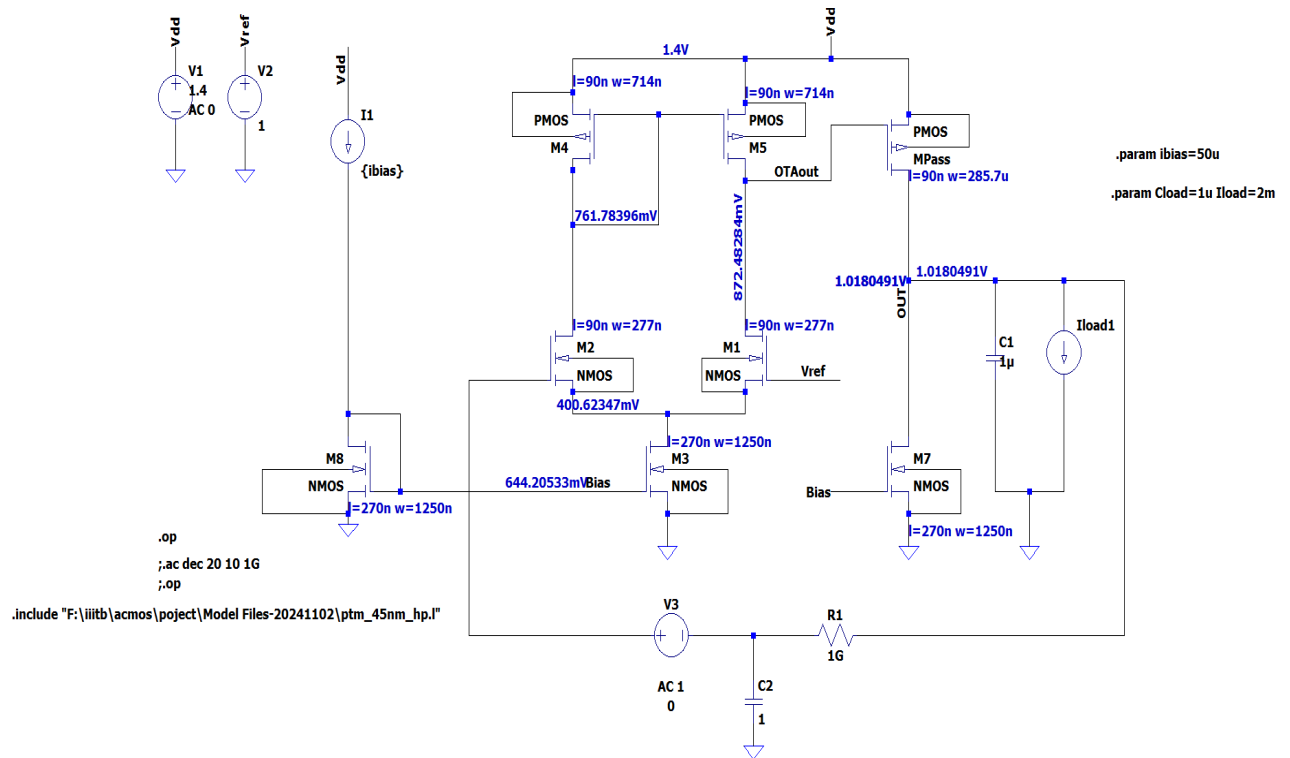


Figure 24: Schematic

## Output Log File:-

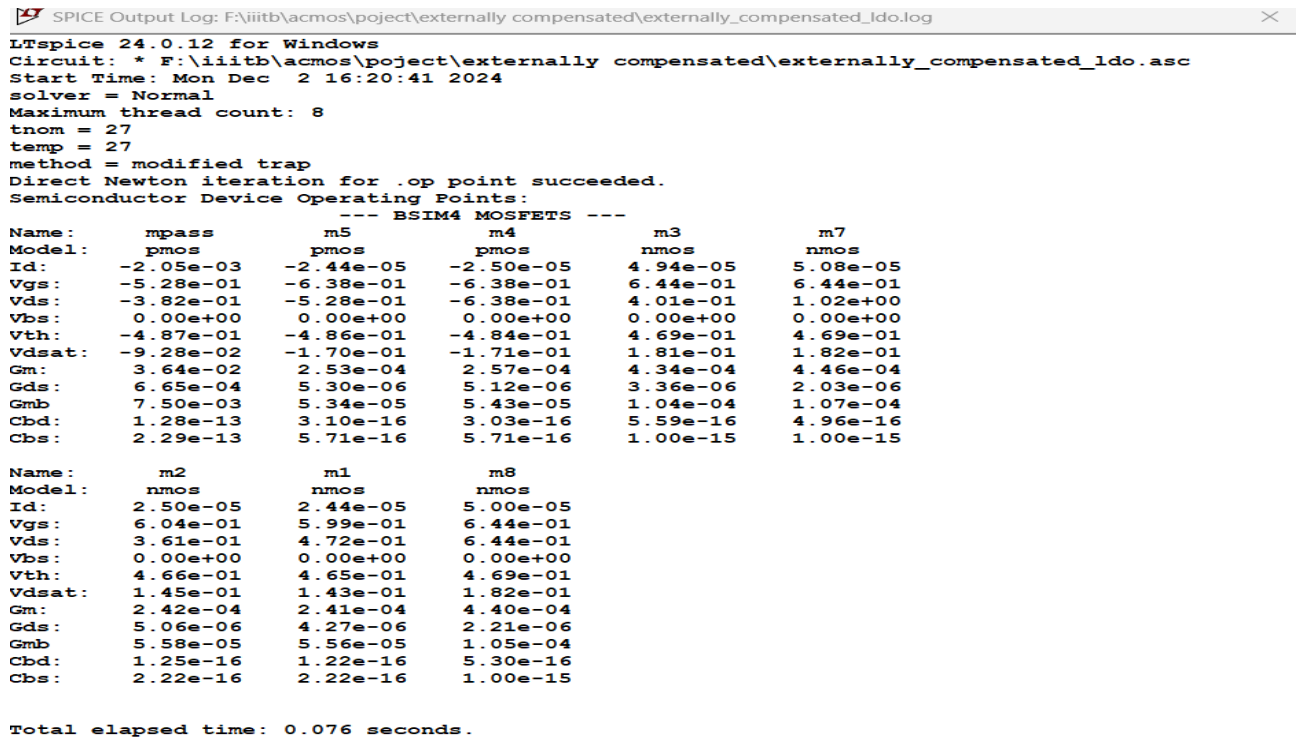

```

SPICE Output Log: F:\iiitb\acmos\project\externally compensated\externally_compensated_ido.log
LTspice 24.0.12 for Windows
Circuit: * F:\iiitb\acmos\project\externally compensated\externally_compensated_ido.asc
Start Time: Mon Dec 2 16:20:41 2024
solver = Normal
Maximum thread count: 8
tnom = 27
temp = 27
method = modified trap
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM4 MOSFETS ---
Name:      mpass      m5      m4      m3      m7
Model:      pmos      pmos      pmos      nmos      nmos
Id:         -2.05e-03  -2.44e-05  -2.50e-05  4.94e-05  5.08e-05
Vgs:        -5.28e-01  -6.38e-01  -6.38e-01  6.44e-01  6.44e-01
Vds:        -3.82e-01  -5.28e-01  -6.38e-01  4.01e-01  1.02e+00
Vbs:         0.00e+00  0.00e+00  0.00e+00  0.00e+00  0.00e+00
Vth:        -4.87e-01  -4.86e-01  -4.84e-01  4.69e-01  4.69e-01
Vdsat:      -9.28e-02  -1.70e-01  -1.71e-01  1.81e-01  1.82e-01
Gm:         3.64e-02  2.53e-04  2.57e-04  4.34e-04  4.46e-04
Gds:         6.65e-04  5.30e-06  5.12e-06  3.36e-06  2.03e-06
Gmb:         7.50e-03  5.34e-05  5.43e-05  1.04e-04  1.07e-04
Cbd:         1.28e-13  3.10e-16  3.03e-16  5.59e-16  4.96e-16
Cbs:         2.29e-13  5.71e-16  5.71e-16  1.00e-15  1.00e-15

Name:      m2      m1      m8
Model:      nmos      nmos      nmos
Id:         2.50e-05  2.44e-05  5.00e-05
Vgs:         6.04e-01  5.99e-01  6.44e-01
Vds:         3.61e-01  4.72e-01  6.44e-01
Vbs:         0.00e+00  0.00e+00  0.00e+00
Vth:         4.66e-01  4.65e-01  4.69e-01
Vdsat:       1.45e-01  1.43e-01  1.82e-01
Gm:         2.42e-04  2.41e-04  4.40e-04
Gds:         5.06e-06  4.27e-06  2.21e-06
Gmb:         5.58e-05  5.56e-05  1.05e-04
Cbd:         1.25e-16  1.22e-16  5.30e-16
Cbs:         2.22e-16  2.22e-16  1.00e-15

Total elapsed time: 0.076 seconds.

```

Figure 25: Output Log Details

## Transistor Operating Regions Table

This document provides a table summarizing the operating regions of several transistors based on their parameters.

Transistor	Type	$V_{ds}$ (V)	$V_{gs}/V_{sg}$ (V)	$V_t$ (V)	$V_{gs}/V_{sg} - V_t$ (V)	Operating Region
M1	NMOS	0.47	0.59	0.46	0.13	Saturation
M2	NMOS	0.36	0.64	0.46	0.18	Saturation
M3	NMOS	0.40	0.64	0.46	0.18	Saturation
M4	PMOS	0.63	0.63	0.48	0.15	Saturation
M5	PMOS	0.52	0.63	0.48	0.15	Saturation
Mpass	PMOS	0.38	0.52	0.48	0.41	Saturation
M7	NMOS	1.02	0.64	0.468	0.15	Saturation
M8	NMOS	0.64	0.64	0.46	0.18	Saturation

Table 7: Transistor Data Table

Loop gain plot:-

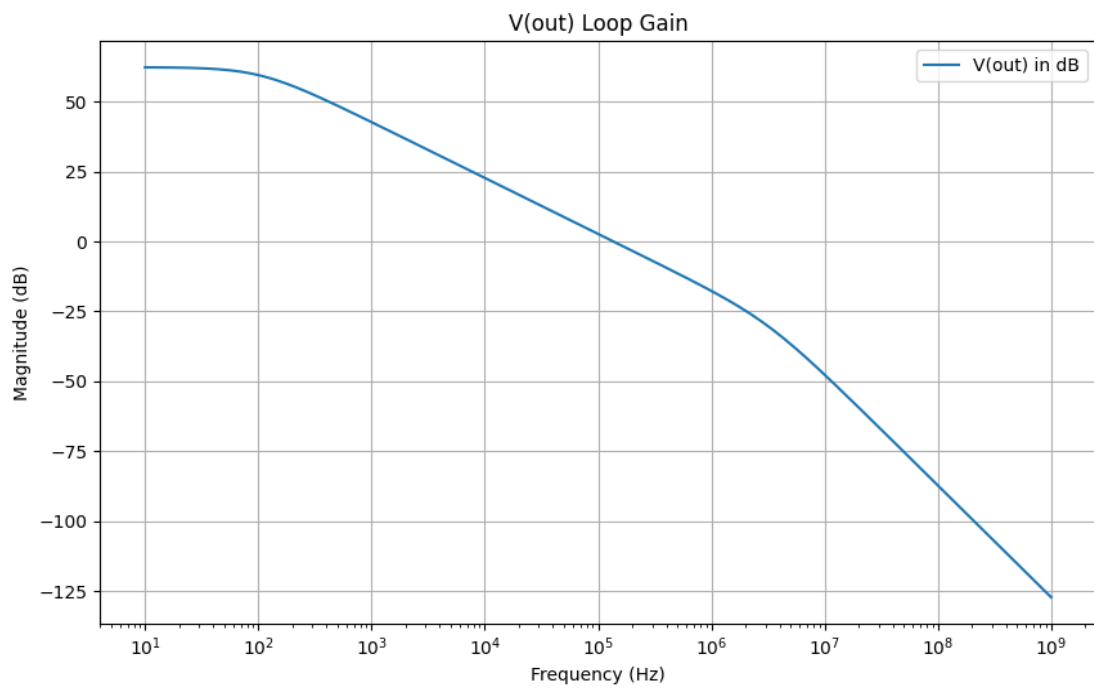


Figure 26: loop gain of output

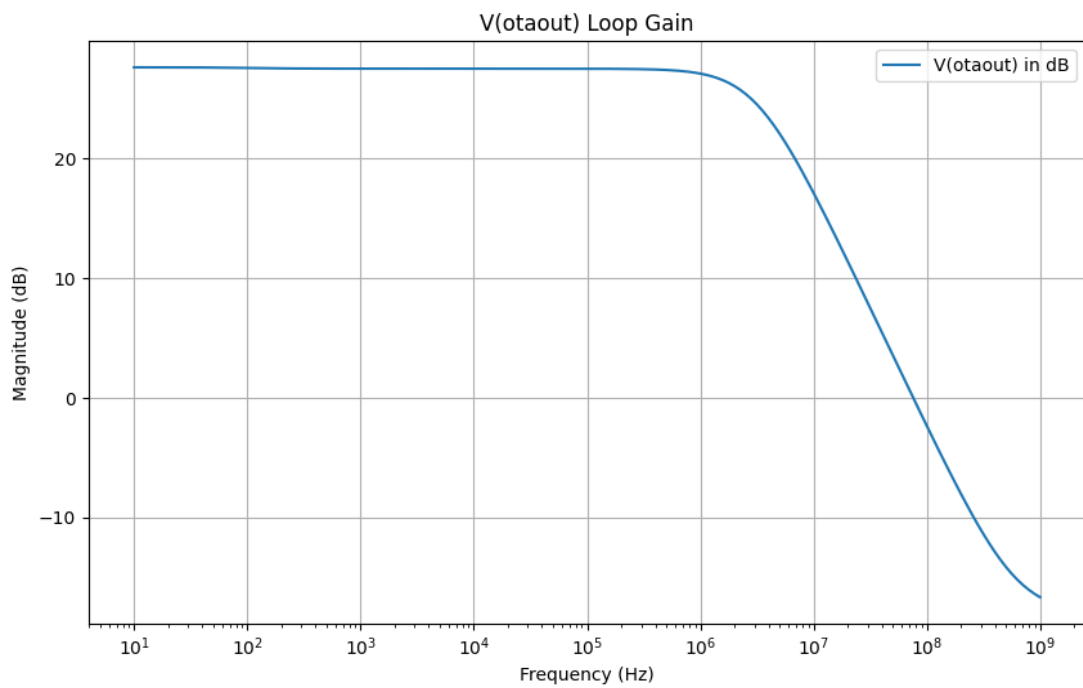


Figure 27: loop gain of OTA

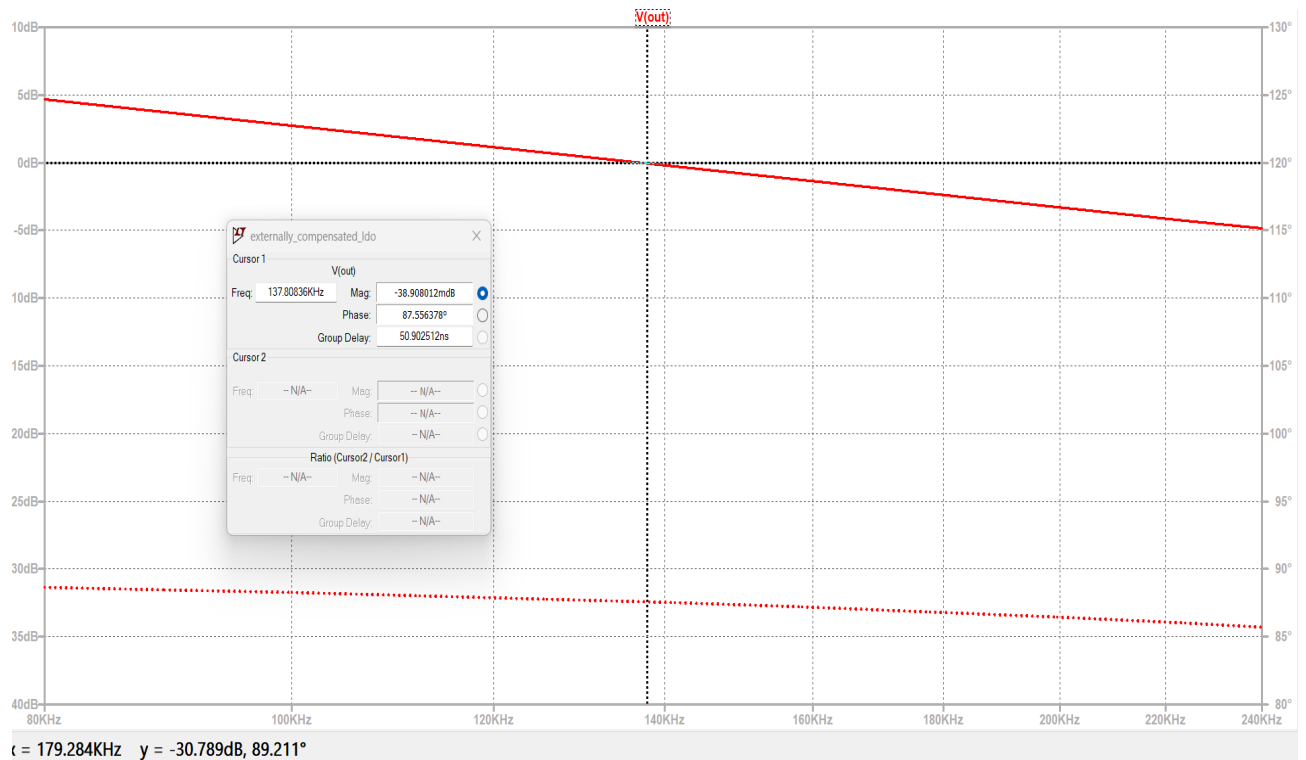


Figure 28: Phase Margin

The phase margin obtained is 87.55 degrees. This value is more than that of the value obtained for heavy load. Thus proving the point that for light load we get a better phase margin as the 1st pole and the 2nd pole are far apart.



## Case 2:- Open Loop PSRR calculation

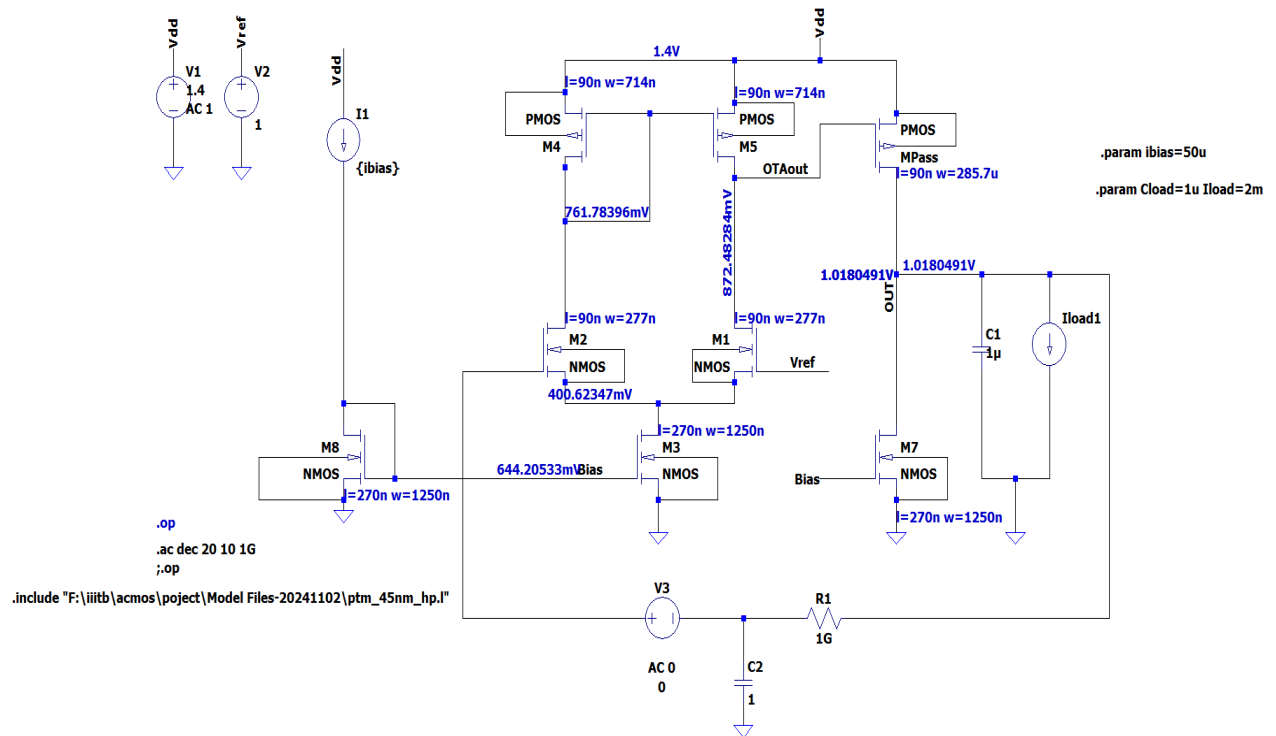


Figure 29: Schematic

## Open loop PSRR plots:-

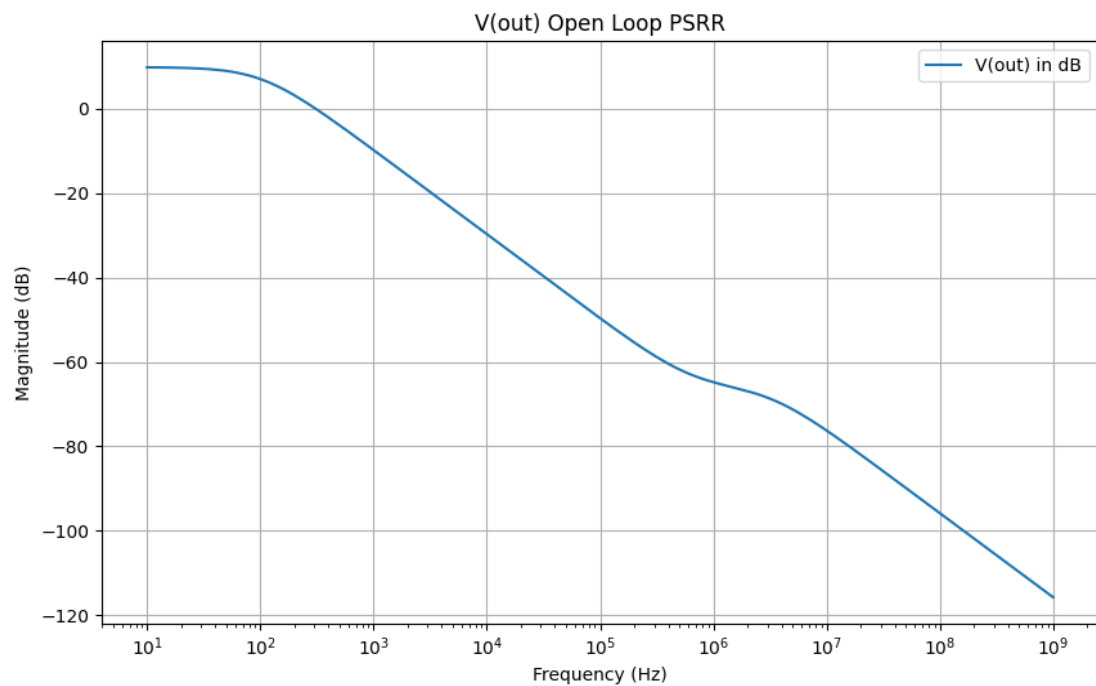


Figure 30: Open loop psrr of output

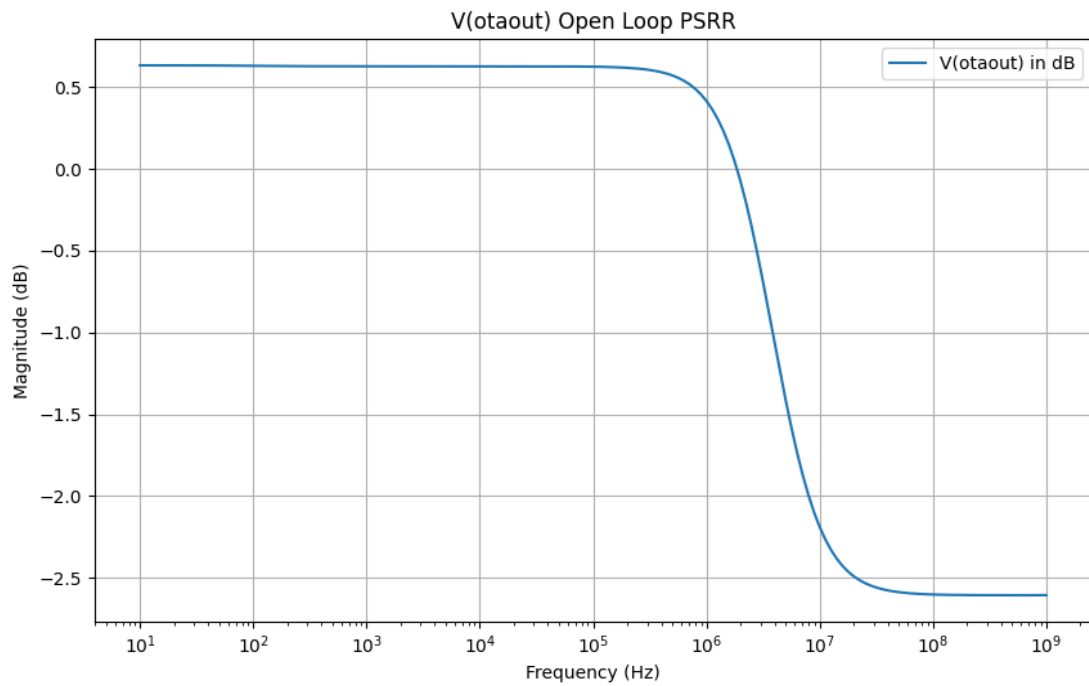


Figure 31: Open loop psrr of OTA

### Case 3:- Closed loop PSRR calculation

#### Schematic

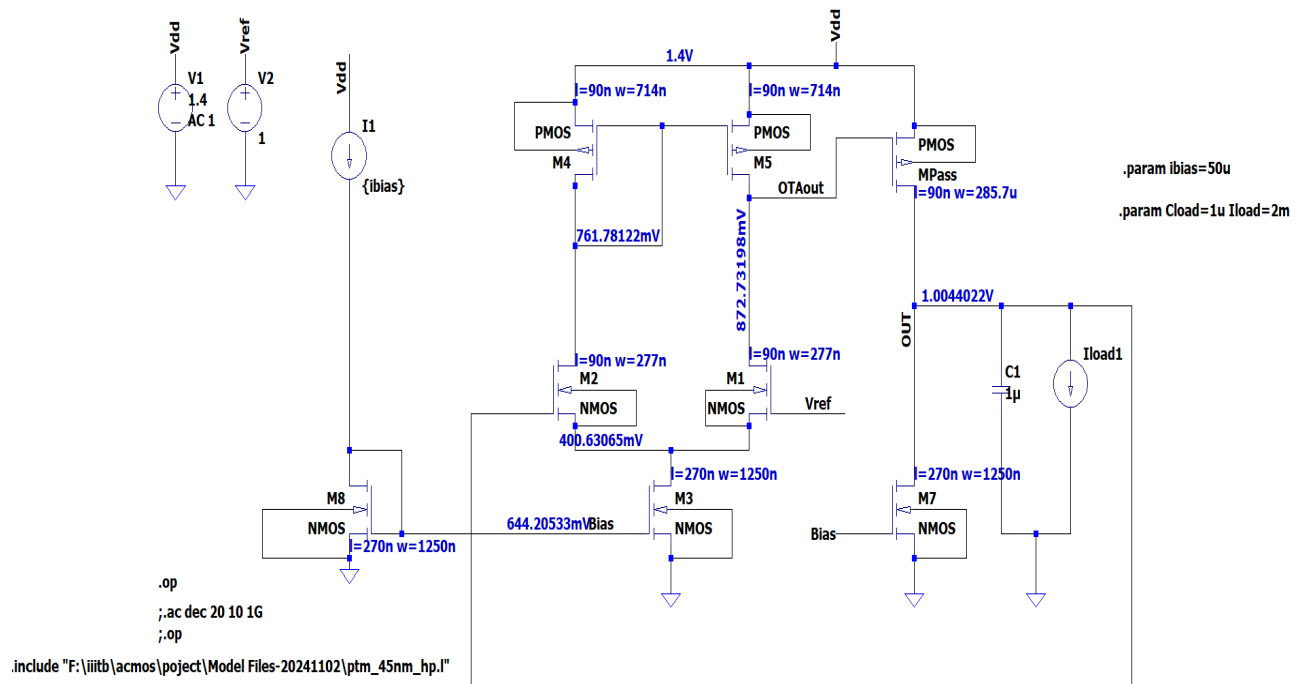


Figure 32: Schematic

Close loop PSRR plots:-

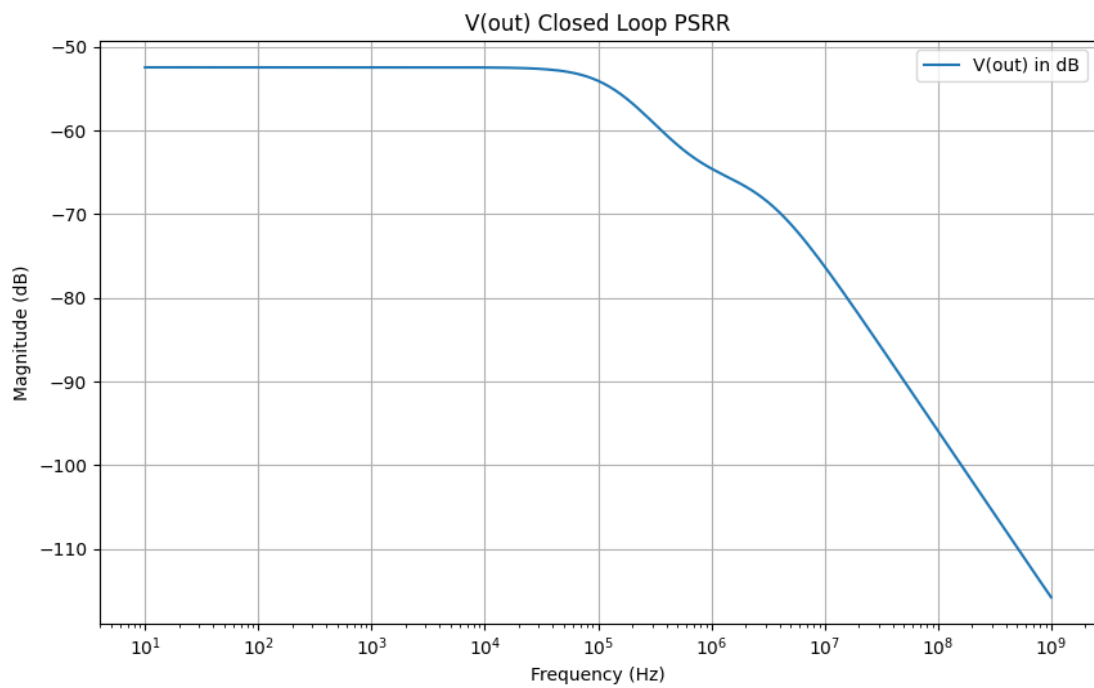


Figure 33: close loop psrr of output

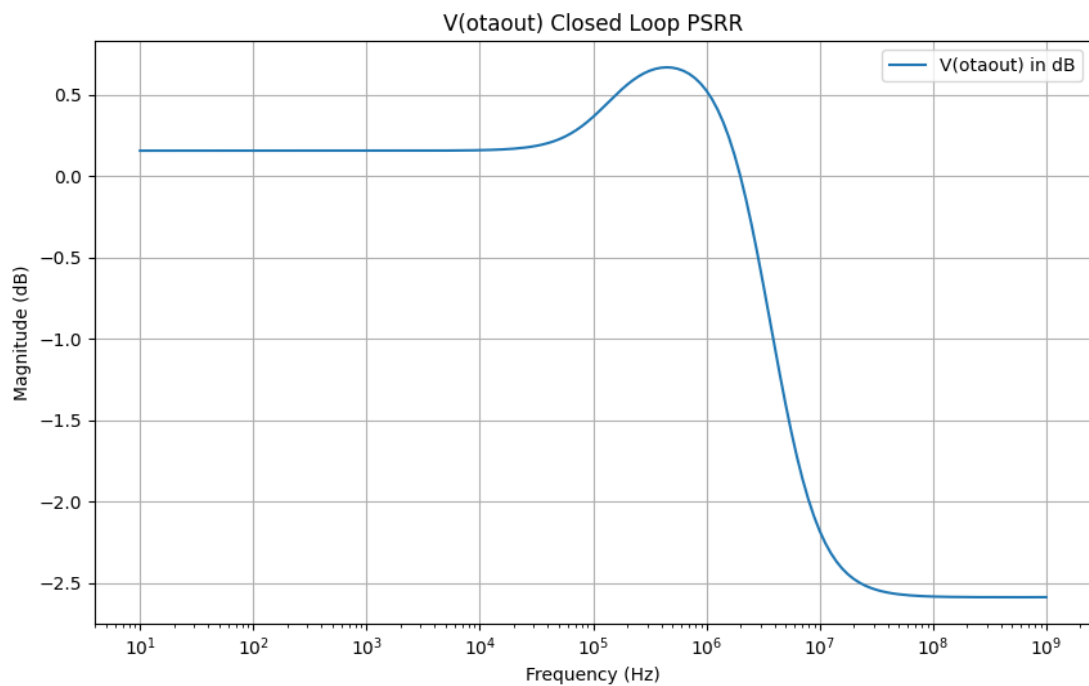


Figure 34: close loop psrr of OTA

## 8. Transient Simulation Results

We have given a pulse at the load with a rise time and fall time of 1u. Also the period of the pulse is 10m with a 50% duty cycle. From the below figure we can understand that the output is able to settle within the specified range of time. We are not able to observe any overshoot or undershoot in the output.

Schematic:-

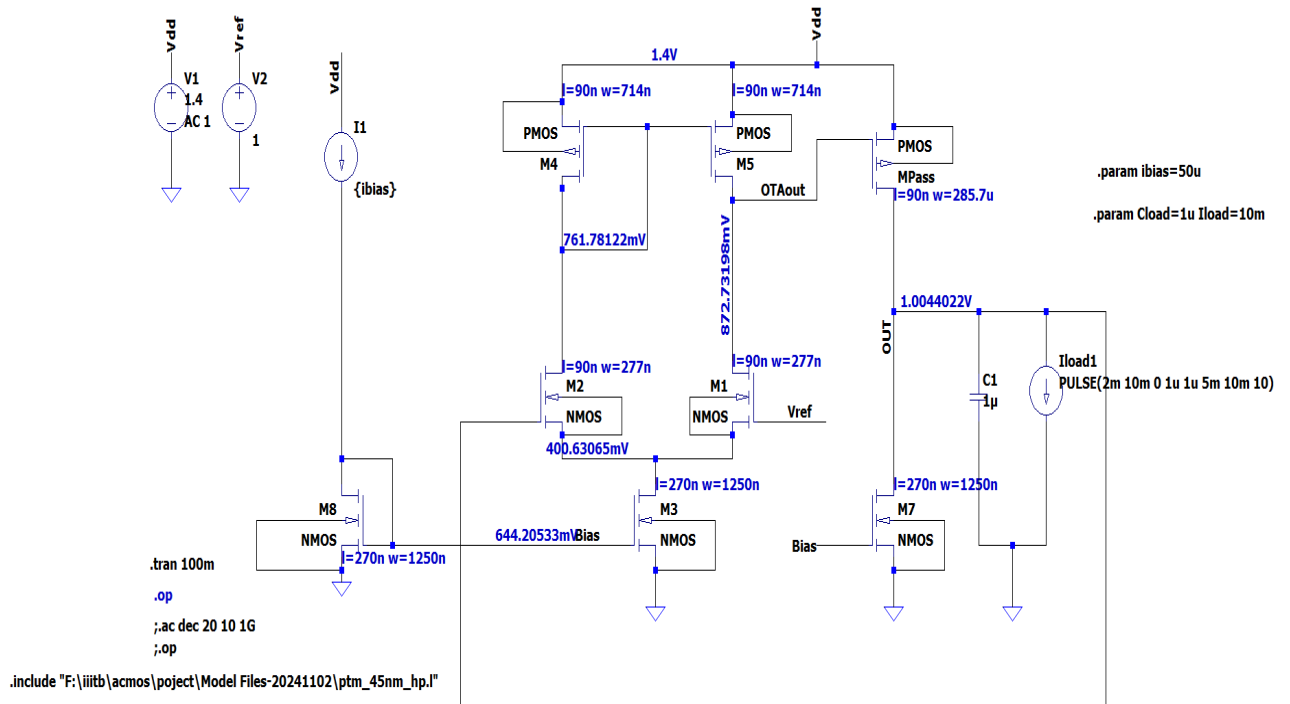


Figure 35: Schematic

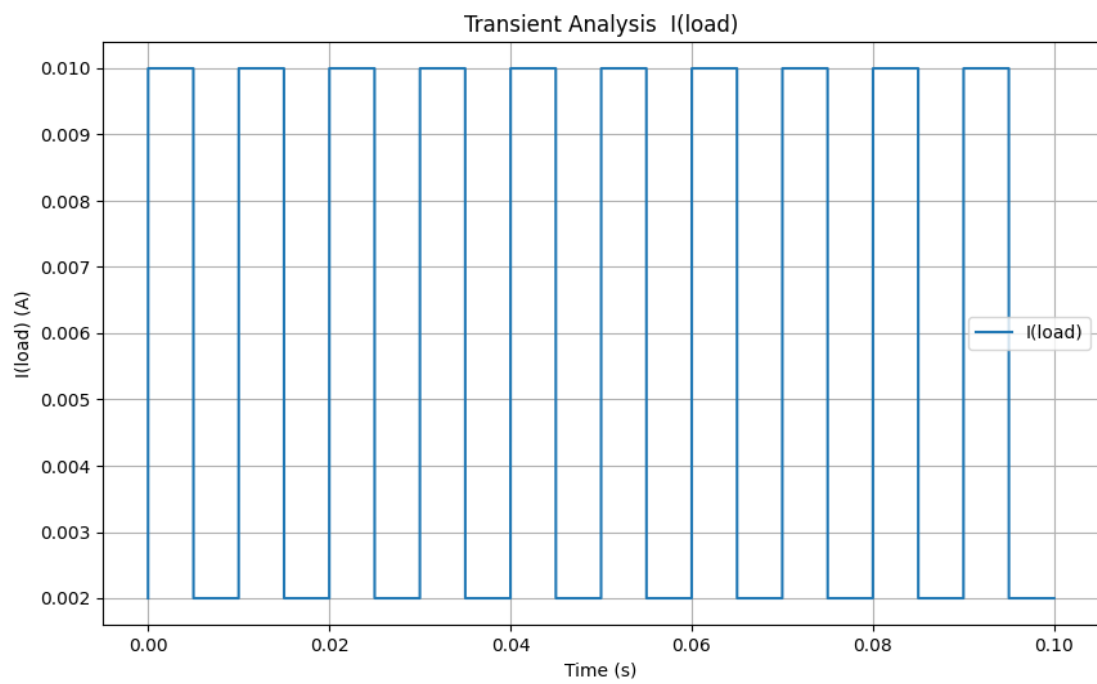
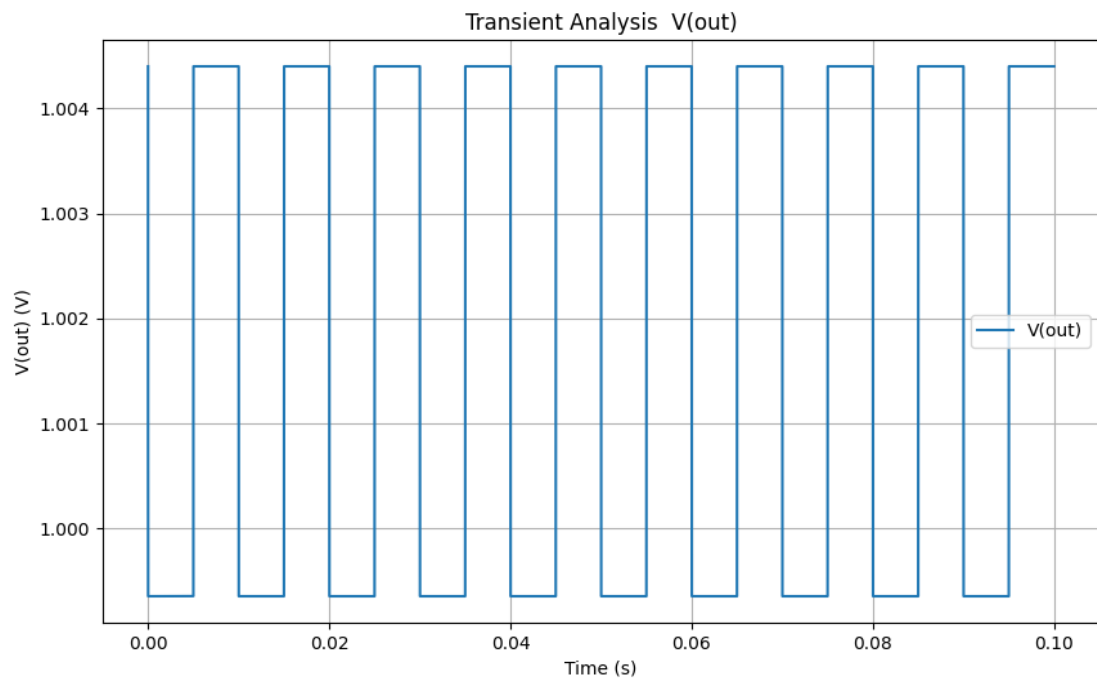
**Plots:-**Figure 36:  $I_{load}$ 

Figure 37: output voltage

## 9. Simulation vs. Hand Calculations

### For Passfet HEAVY LOAD

#### Hand Calculation

- $r_o = 500 \Omega$
- $g_m = 0.1 \text{ A/V}$
- $W_{p1}$  (first pole location) = 2k
- $g_m r_o = 50$
- $C_L = 1u$
- $C_g g = 0.568p$

#### Simulation Results from SPICE Error Log:

- $r_o = 1/g_{ds} = 393 \Omega$
- $g_m = 0.102 \text{ A/V}$
- $W_{p1}$  (first pole location) = 2.54k
- $g_m r_o = 40.086$

Table 8: Hand Calculation vs Simulation Results

Parameter	Hand Calculation	Simulation Result	% Difference
$r_o$ (ohm)	500.00	395.25	21.0%
$g_m$ (A/V)	0.1	0.102	1.9%
$g_m * r_o$	50	40.316	19.36%
$W_{p1}$ (Hz)	2k	2.53k	20.94%
$W_{p2}$ (Hz)	22M	17.85M	18.86%
$W_{ugb}$ (Hz)	2M	2.53M	20.94%
$r_{odiff}$ (ohm)	80k	98.619k	18.87%
$g_{mdiff}$ (A/V)	250u	255u	1.96%

max width=								
Name	mpass	m5	m4	m3	m7	m2	m1	m8
Model	pmos	pmos	pmos	nmos	nmos	nmos	nmos	nmos
<b>Id</b>	-1.01E-02	-2.46E-05	-2.46E-05	4.94E-05	5.08E-05	2.46E-05	2.47E-05	5.00E-05
<b>Vgs</b>	-6.43E-01	-6.37E-01	-6.37E-01	6.44E-01	6.44E-01	6.02E-01	6.03E-01	6.44E-01
<b>Vds</b>	-3.87E-01	-6.43E-01	-6.37E-01	3.97E-01	1.01E+00	3.66E-01	3.60E-01	6.44E-01
<b>Vbs</b>	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
<b>Vth</b>	-4.87E-01	-4.84E-01	-4.84E-01	4.69E-01	4.69E-01	4.66E-01	4.66E-01	4.69E-01
<b>Vdsat</b>	-1.72E-01	-1.70E-01	-1.70E-01	1.81E-01	1.82E-01	1.44E-01	1.44E-01	1.82E-01
<b>Gm</b>	1.02E-01	2.56E-04	2.55E-04	4.34E-04	4.46E-04	2.40E-04	2.41E-04	4.40E-04
<b>Gds</b>	2.54E-03	5.07E-06	5.07E-06	3.41E-06	2.03E-06	4.94E-06	5.03E-06	2.21E-06
<b>Gmb</b>	2.16E-02	5.40E-05	5.39E-05	1.04E-04	1.07E-04	5.55E-05	5.56E-05	1.05E-04
<b>Cbd</b>	1.28E-13	3.03E-16	3.03E-16	5.60E-16	4.96E-16	1.25E-16	1.25E-16	5.30E-16
<b>Cbs</b>	2.29E-13	5.71E-16	5.71E-16	1.00E-15	1.00E-15	2.22E-16	2.22E-16	1.00E-15
<b>ro</b>	3.94E+02	1.97E+05	1.97E+05	2.93E+05	4.93E+05	2.02E+05	1.99E+05	4.52E+05
<b>gm*ro</b>	4.02E+01	5.05E+01	5.03E+01	1.27E+02	2.20E+02	4.86E+01	4.79E+01	1.99E+02

Table 9: Updated Transistor Parameter Table

## For Passfet LIGHT LOAD

### Hand Calculation

- $r_o = 2500 \Omega$
- $g_m = 0.02 \text{ A/V}$
- $W_{p1}$  (first pole location) = 400
- $g_m r_o = 50$
- $C_L = 1u$
- $C_{gg} = 0.1136p$

### Simulation Results from SPICE Error Log:

- $r_o = 1/g_{ds} = 1503.7 \Omega$
- $g_m = 0.0364 \text{ A/V}$
- $W_{p1}$  (first pole location) = 665.02
- $g_m r_o = 54.7$

Table 10: Hand Calculation vs Simulation Results

Parameter	Hand Calculation	Simulation Result	% Difference
$r_o$ (ohm)	2500.00	1503.7	39.0%
$g_m$ (A/V)	0.02	0.0364	45%
$g_m * r_o$	50	54.7	8.5%
$W_{p1}$ (Hz)	400	665.02	39.8%
$W_{p2}$ (Hz)	110M	84.4M	23.2%
$W_{ugb}$ (Hz)	400k	665.02k	39.8%
$r_{odiff}$ (ohm)	80k	104.2k	23.07%
$g_{mdiff}$ (A/V)	250u	253u	1.185%



max width=								
Name	mpass	m5	m4	m3	m7	m2	m1	m8
Model	pmos	pmos	pmos	nmos	nmos	nmos	nmos	nmos
<b>Id</b>	-2.05E-03	-2.44E-05	-2.50E-05	4.94E-05	5.08E-05	2.50E-05	2.44E-05	5.00E-05
<b>Vgs</b>	-5.28E-01	-6.38E-01	-6.38E-01	6.44E-01	6.44E-01	6.04E-01	5.99E-01	6.44E-01
<b>Vds</b>	-3.82E-01	-5.28E-01	-6.38E-01	4.01E-01	1.02E+00	3.61E-01	4.72E-01	6.44E-01
<b>Vbs</b>	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
<b>Vth</b>	-4.87E-01	-4.86E-01	-4.84E-01	4.69E-01	4.69E-01	4.66E-01	4.65E-01	4.69E-01
<b>Vdsat</b>	-9.28E-02	-1.70E-01	-1.71E-01	1.81E-01	1.82E-01	1.45E-01	1.43E-01	1.82E-01
<b>Gm</b>	3.64E-02	2.53E-04	2.57E-04	4.34E-04	4.46E-04	2.42E-04	2.41E-04	4.40E-04
<b>Gds</b>	6.65E-04	5.30E-06	5.12E-06	3.36E-06	2.03E-06	5.06E-06	4.27E-06	2.21E-06
<b>Gmb</b>	7.50E-03	5.34E-05	5.43E-05	1.04E-04	1.07E-04	5.58E-05	5.56E-05	1.05E-04
<b>Cbd</b>	1.28E-13	3.10E-16	3.03E-16	5.59E-16	4.96E-16	1.25E-16	1.22E-16	5.30E-16
<b>Cbs</b>	2.29E-13	5.71E-16	5.71E-16	1.00E-15	1.00E-15	2.22E-16	2.22E-16	1.00E-15
<b>ro</b>	1.50E+03	1.89E+05	1.95E+05	2.98E+05	4.93E+05	1.98E+05	2.34E+05	4.52E+05
<b>gm*ro</b>	5.47E+01	4.77E+01	5.02E+01	1.29E+02	2.20E+02	4.78E+01	5.64E+01	1.99E+02

Table 11: Transistor Parameter Table

# Internally Compensated LDO

## 1. Specifications

Table 12: Specifications Summary

Parameter	Value
Vin	1.4V
Vout	1V
PSRR	60dB
Iload (min)	2mA
Iload (max)	10mA
Cload	2nF
Iquiescent	50uA
Transient duration	1u

we have made three schematics in LTSpice to calculate the three conditions. We have made a simulation artifact for the same.

Case 1 : Loop Gain Analysis

Case 2 : Open Loop PSRR Calculation

Case 3 : Closed Loop PSRR Calculation

## Light Load ( 2mA )

### Schematic

#### Case 1:- Loop gain analysis:-


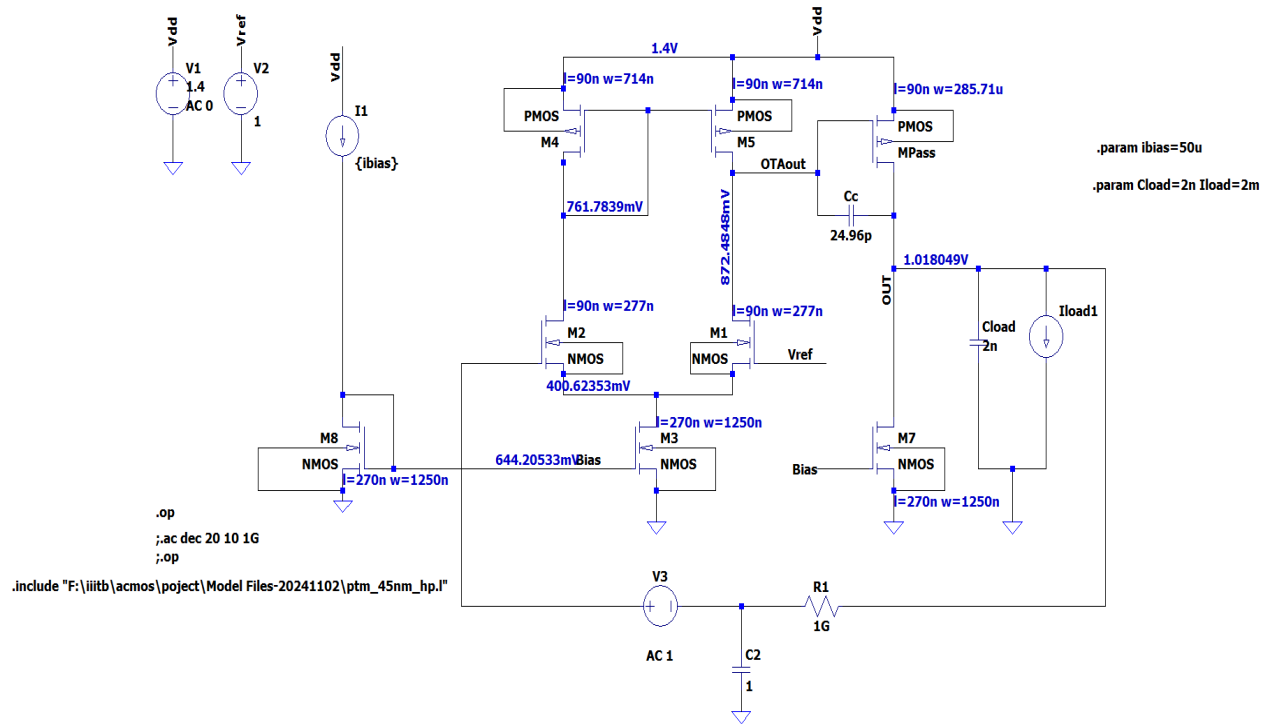


Figure 38: Schematic

Explanation of the artifact used:-

Output Log File:-

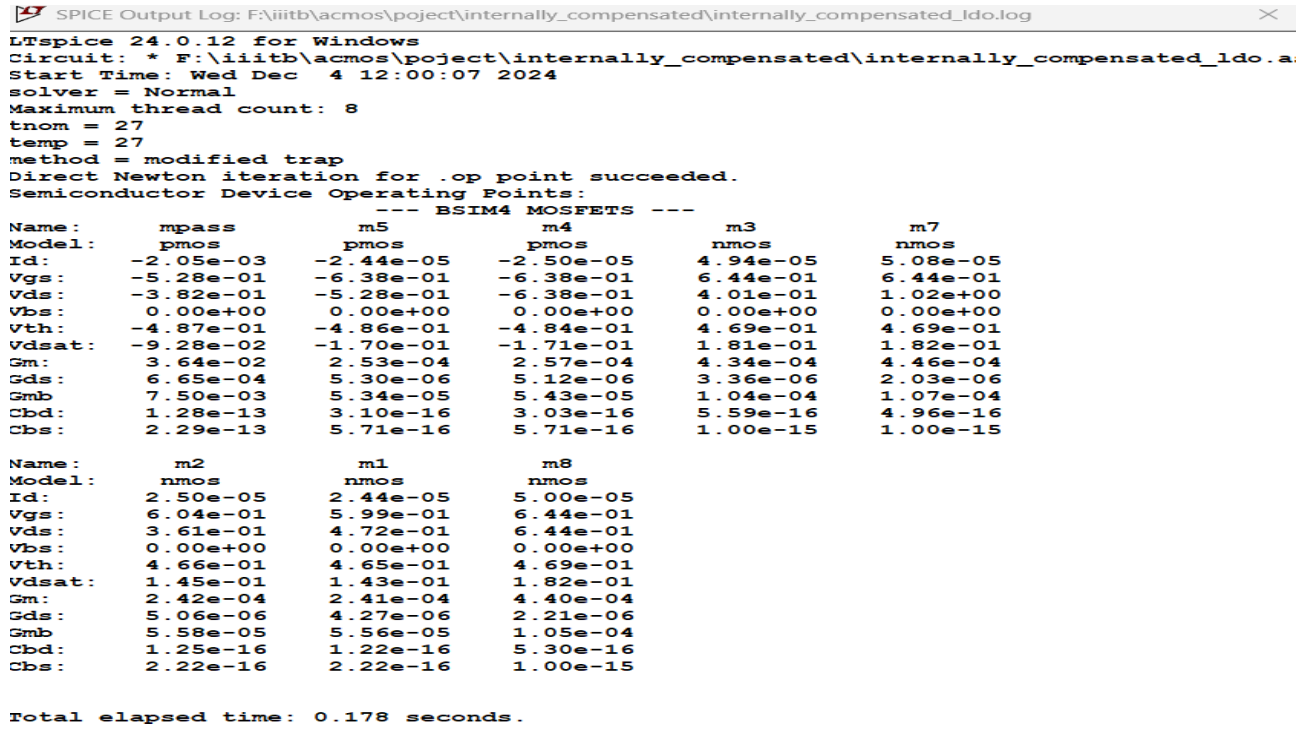

```

SPICE Output Log: F:\iiitb\acmos\project\internally_compensated\internally_compensated_ido.log
LTspice 24.0.12 for Windows
Circuit: * F:\iiitb\acmos\project\internally_compensated\internally_compensated_ido.a
Start Time: Wed Dec 4 12:00:07 2024
solver = Normal
Maximum thread count: 8
tnom = 27
temp = 27
method = modified trap
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM4 MOSFETS ---
Name:      mpass      m5      m4      m3      m7
Model:     pmos      pmos      pmos      nmos      nmos
Id:        -2.05e-03   -2.44e-05  -2.50e-05  4.94e-05  5.08e-05
Vgs:       -5.28e-01   -6.38e-01  -6.38e-01  6.44e-01  6.44e-01
Vds:       -3.82e-01   -5.28e-01  -6.38e-01  4.01e-01  1.02e+00
Vbs:       0.00e+00    0.00e+00   0.00e+00   0.00e+00  0.00e+00
Vth:       -4.87e-01   -4.86e-01  -4.84e-01  4.69e-01  4.69e-01
Vdsat:     -9.28e-02   -1.70e-01  -1.71e-01  1.81e-01  1.82e-01
Gm:        3.64e-02    2.53e-04   2.57e-04   4.34e-04  4.46e-04
Gds:       6.65e-04    5.30e-06   5.12e-06   3.36e-06  2.03e-06
Gmb:       7.50e-03    5.34e-05   5.43e-05   1.04e-04  1.07e-04
Cbd:       1.28e-13    3.10e-16   3.03e-16   5.59e-16  4.96e-16
Cbs:       2.29e-13    5.71e-16   5.71e-16   1.00e-15  1.00e-15

Name:      m2      m1      m8
Model:     nmos      nmos      nmos
Id:        2.50e-05   2.44e-05   5.00e-05
Vgs:       6.04e-01   5.99e-01   6.44e-01
Vds:       3.61e-01   4.72e-01   6.44e-01
Vbs:       0.00e+00   0.00e+00   0.00e+00
Vth:       4.66e-01   4.65e-01   4.69e-01
Vdsat:     1.45e-01   1.43e-01   1.82e-01
Gm:        2.42e-04   2.41e-04   4.40e-04
Gds:       5.06e-06   4.27e-06   2.21e-06
Gmb:       5.58e-05   5.56e-05   1.05e-04
Cbd:       1.25e-16   1.22e-16   5.30e-16
Cbs:       2.22e-16   2.22e-16   1.00e-15

Total elapsed time: 0.178 seconds.

```

Figure 39: Output Log Detail

From the above file we can verify that all the devices are in saturation as follows:

## Transistor Operating Regions Table

This document provides a table summarizing the operating regions of several transistors based on their parameters.

Transistor	Type	$V_{ds}$ (V)	$V_{gs}/V_{sg}$ (V)	$V_t$ (V)	$V_{gs}/V_{sg} - V_t$ (V)	Operating Region
M1	NMOS	0.472	0.599	0.465	0.134	Saturation
M2	NMOS	0.361	0.604	0.466	0.138	Saturation
M3	NMOS	0.401	0.644	0.469	0.175	Saturation
M4	PMOS	0.638	0.638	0.484	0.267	Saturation
M5	PMOS	0.528	0.638	0.487	0.151	Saturation
Mpass	PMOS	0.382	0.528	0.487	0.041	Saturation
M7	NMOS	1.02	0.644	0.469	0.175	Saturation
M8	NMOS	0.644	0.644	0.469	0.1.75	Saturation

Table 13: Transistor Parameters and Operating Regions

Loop gain plots:-

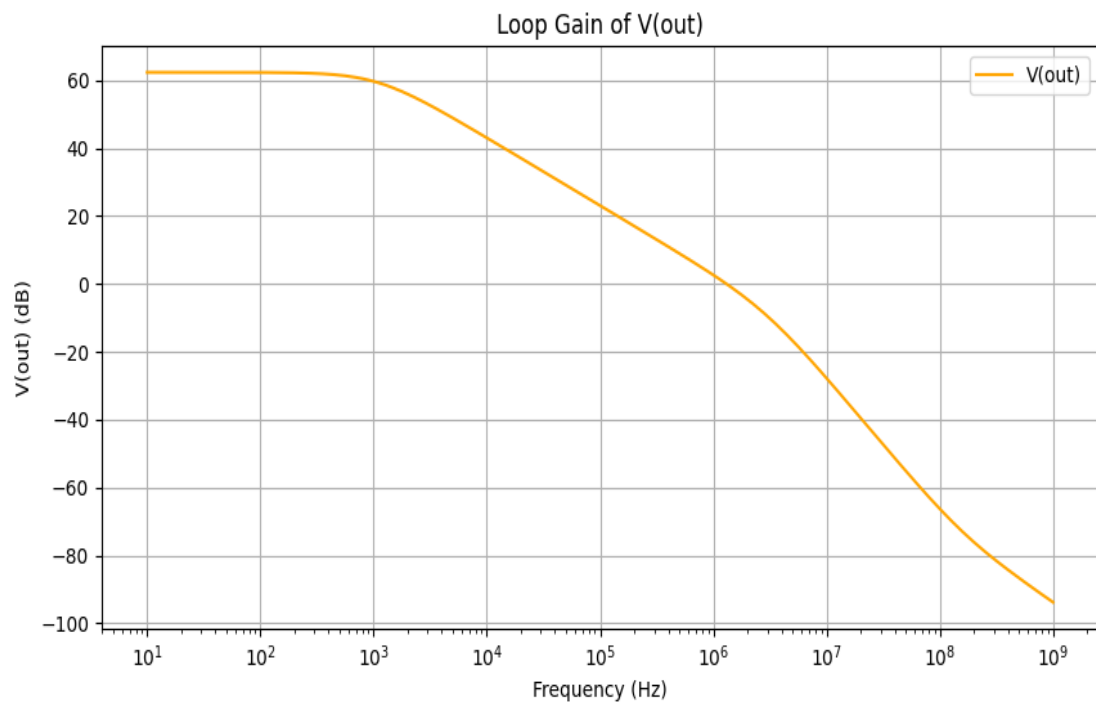


Figure 40: Loop gain of LDO

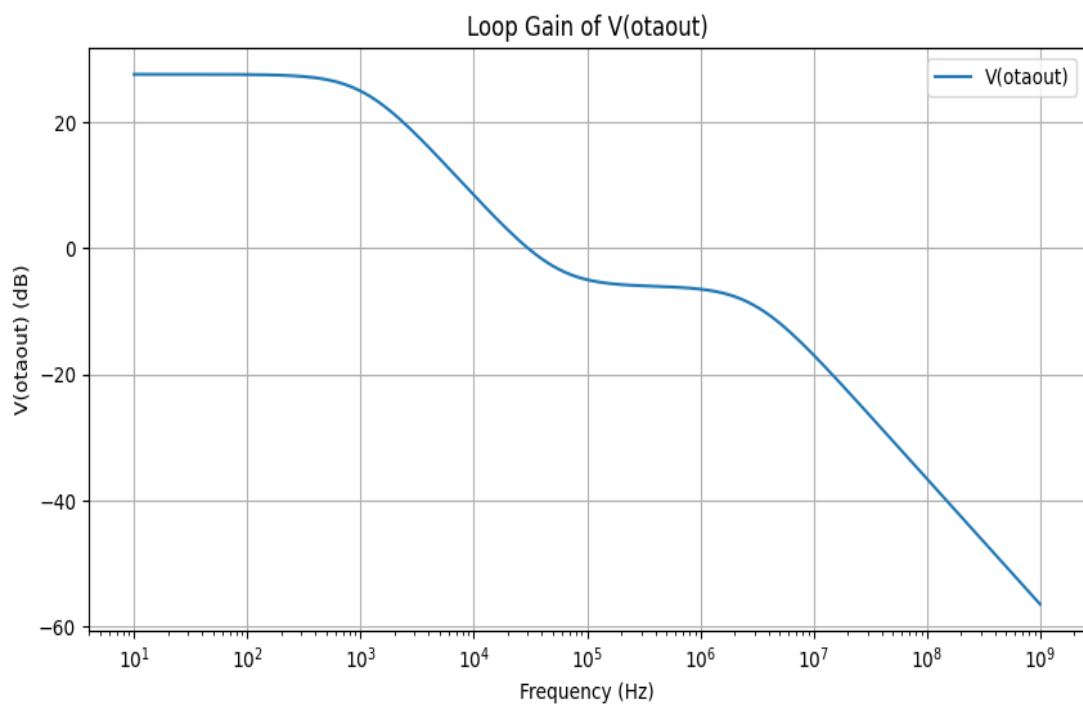


Figure 41: Loop gain of OTA

## Phase margin

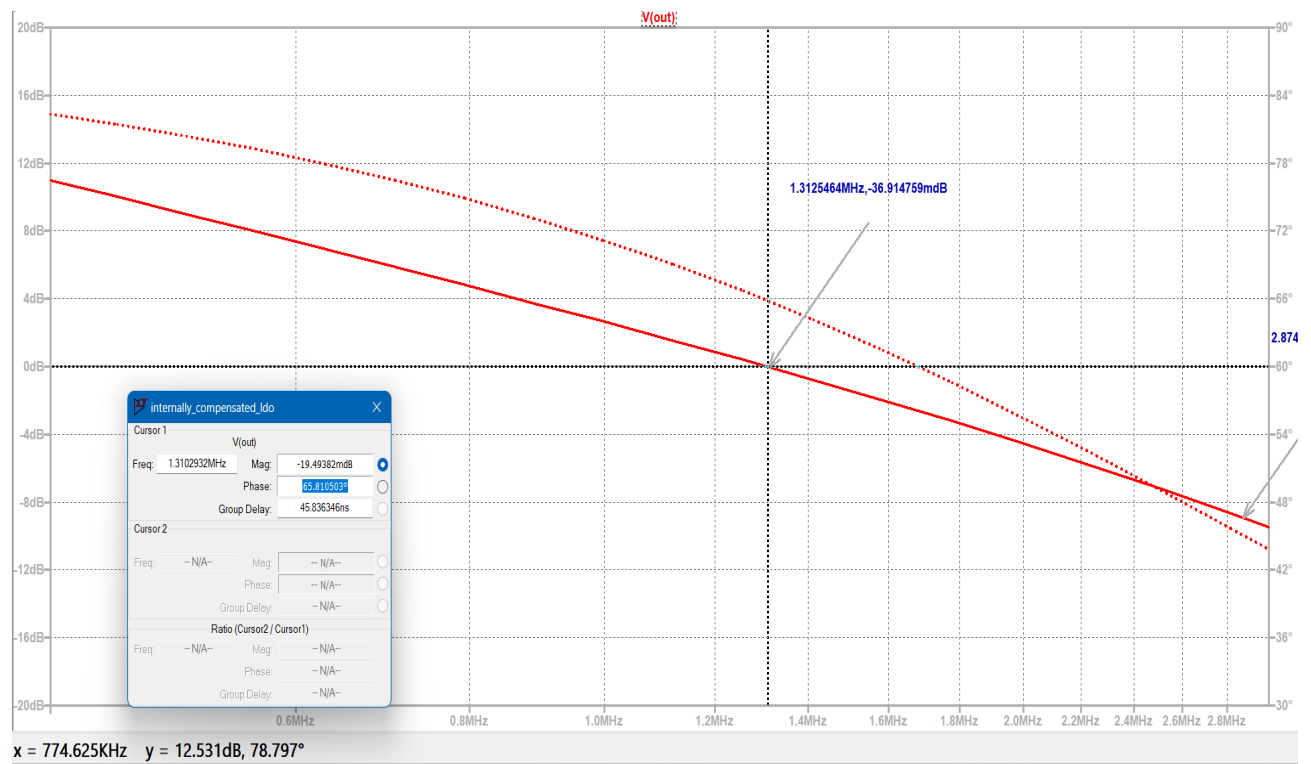


Figure 42: Phase Margin

## Case 2:- Open Loop PSRR calculation

### Schematic

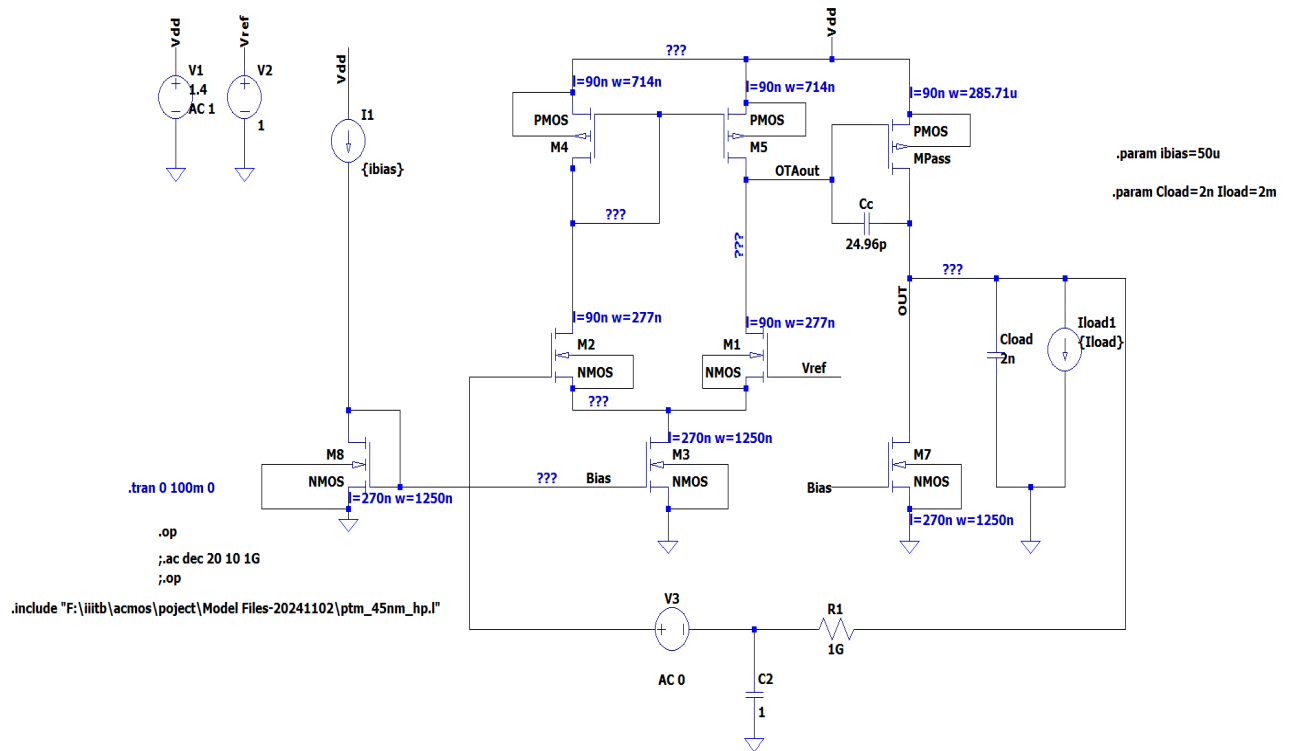


Figure 43: Schematic

Open loop PSRR plots:-

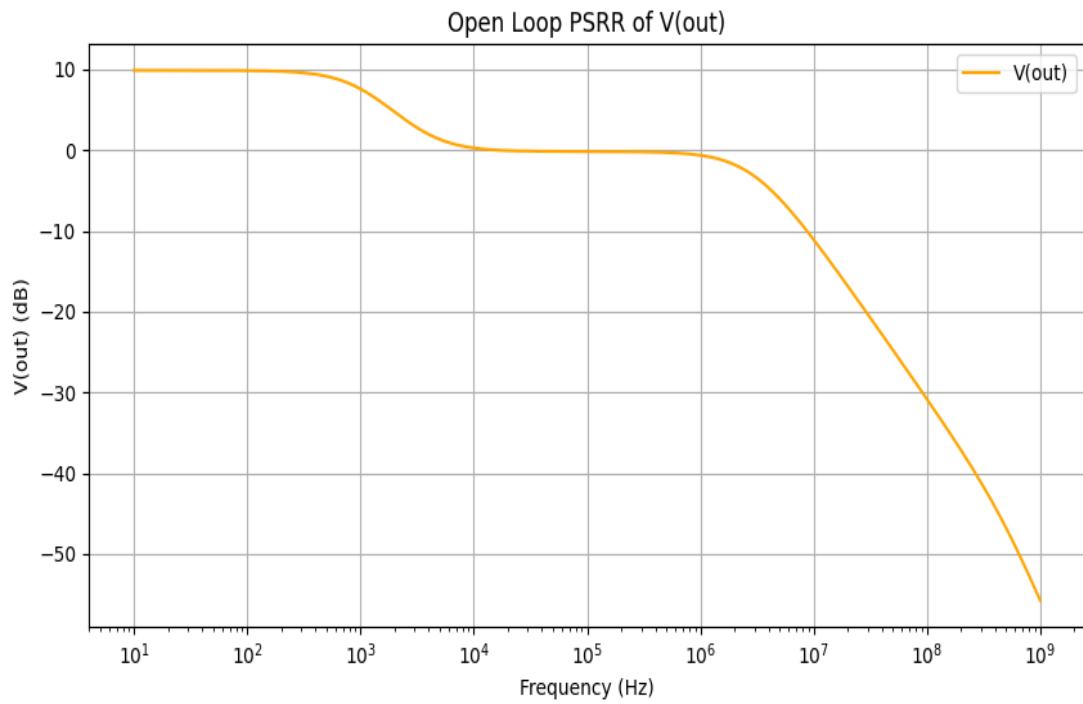


Figure 44: Open loop psrr of LDO

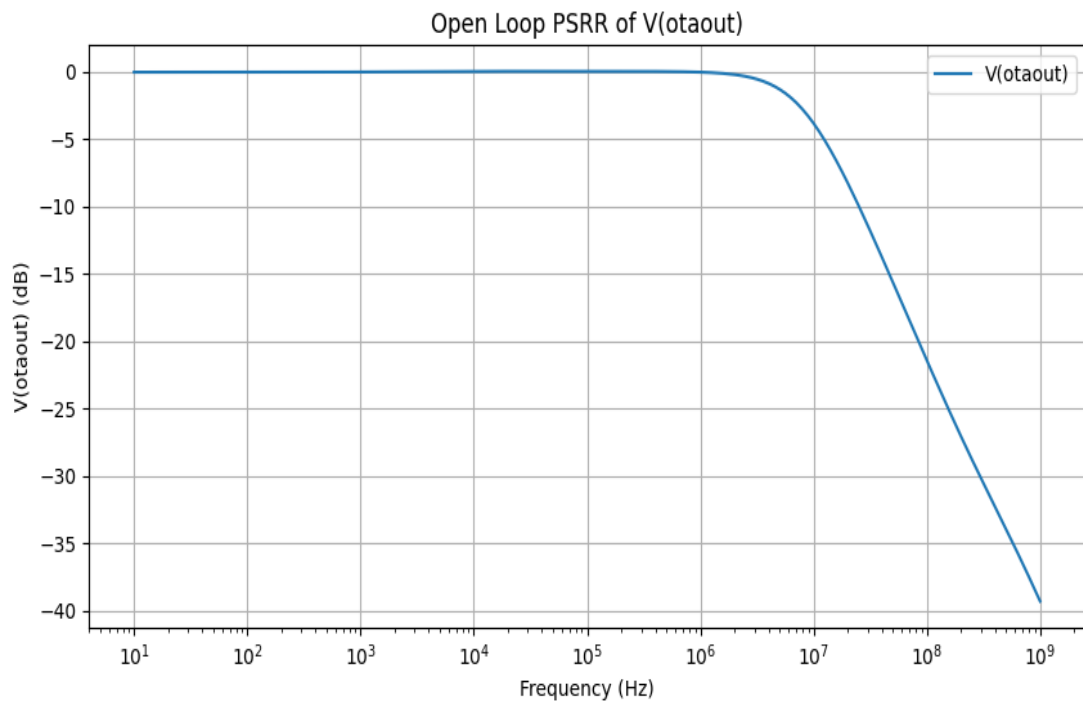


Figure 45: Open loop psrr of OTA



### Case 3:- Closed loop PSRR calculation

#### Schematic

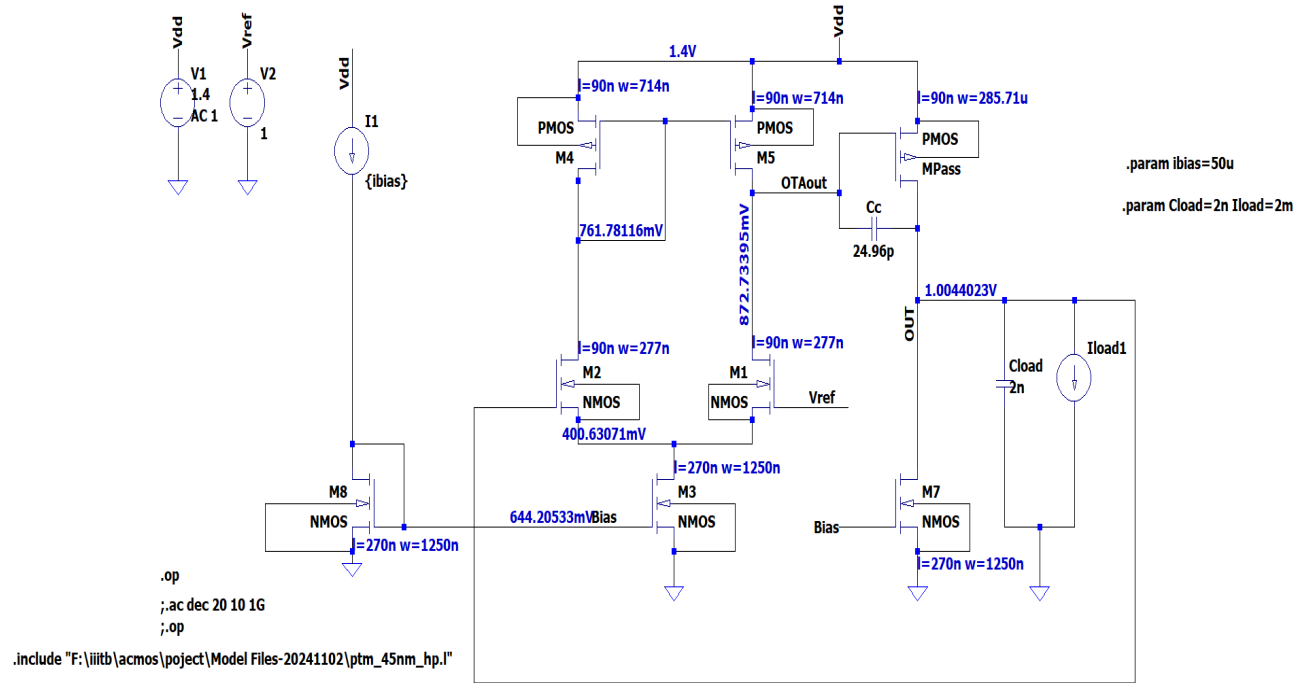


Figure 46: Schematic

Close loop psrr plots:-

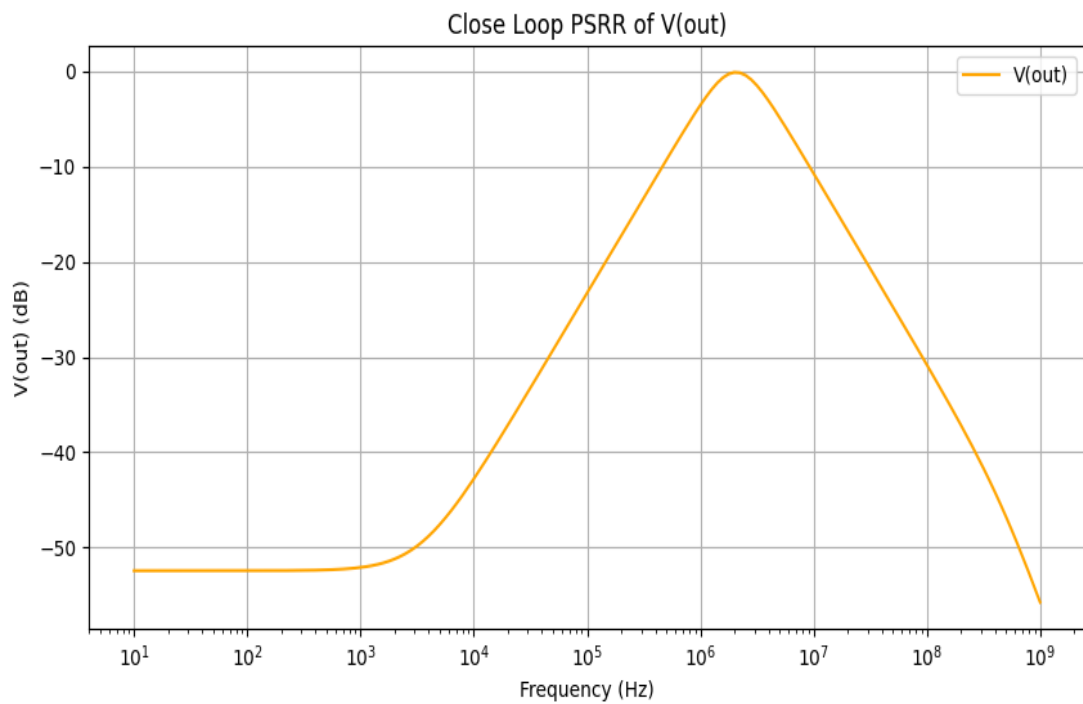


Figure 47: Close loop psrr of LDO

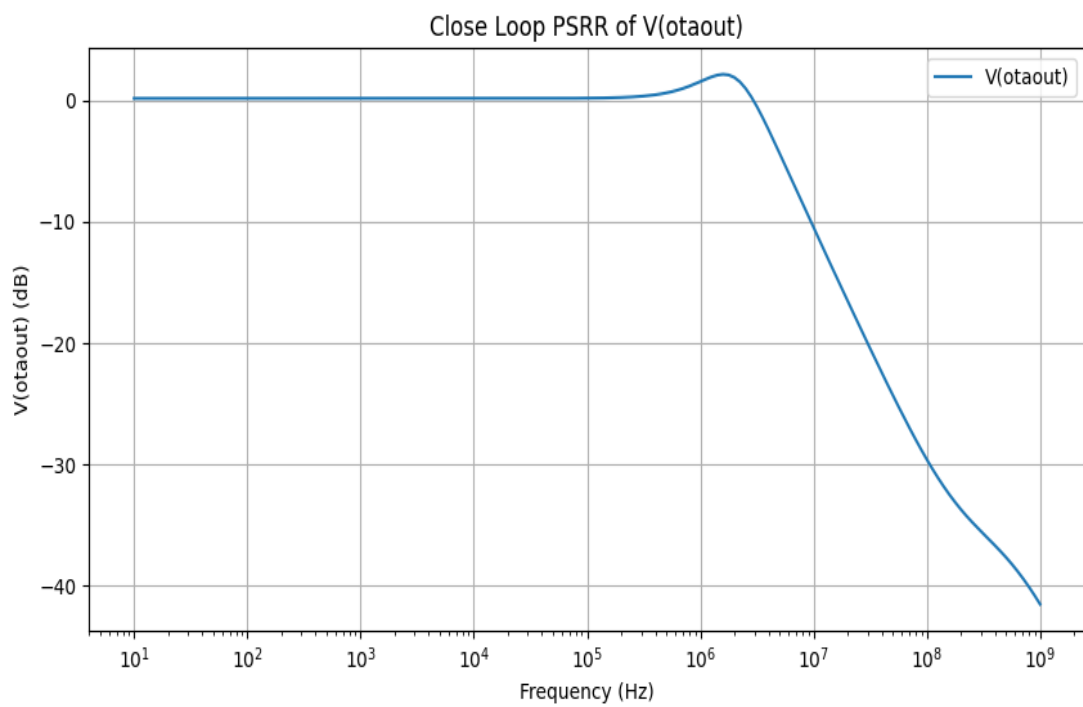


Figure 48: Close loop psrr of OTA

## Heavy Load ( 10mA )

### Schematic

#### Case 1:- Loop gain analysis:-

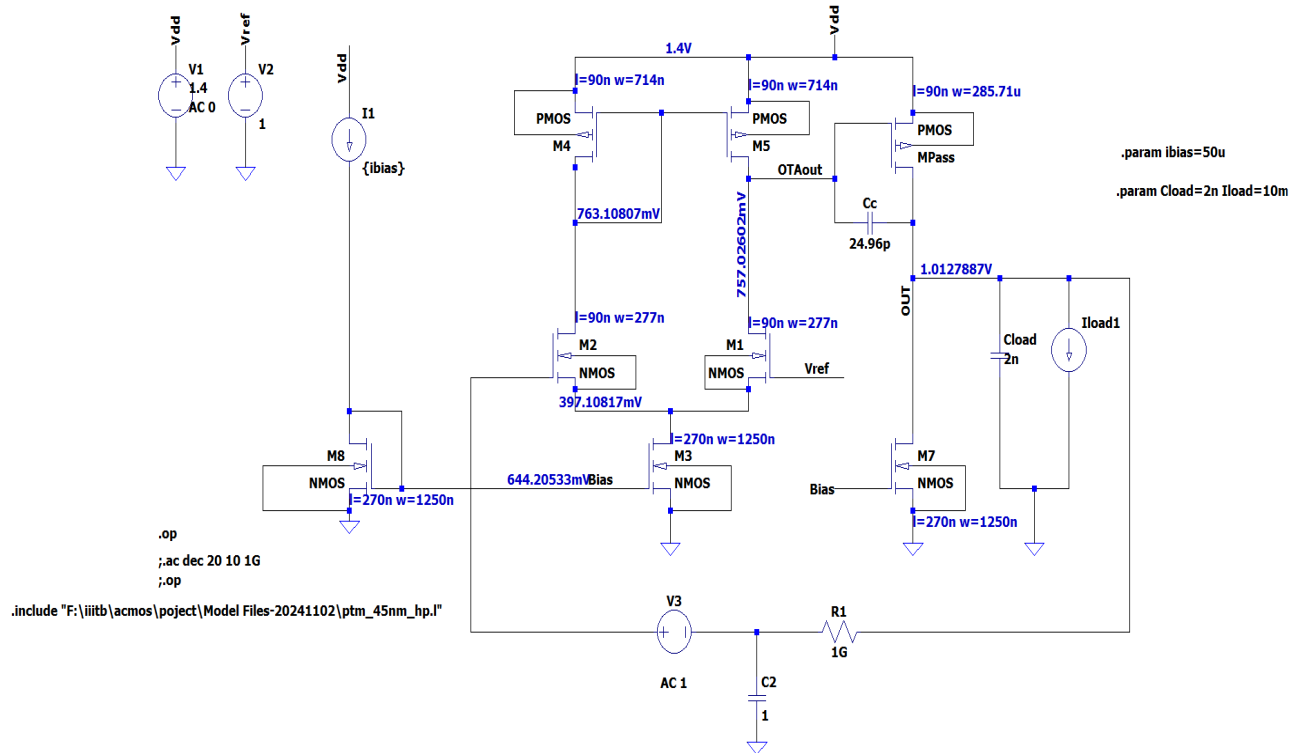


Figure 49: Schematic

Explanation of the artifact used:-

Output Log File:-

```

LTspice 24.0.12 for Windows
Circuit: * F:\iiiitb\acmos\project\internally_compensated\internally_compensated_1do.a
Start Time: Wed Dec 4 11:22:29 2024
solver = Normal
Maximum thread count: 8
tnom = 27
temp = 27
method = modified trap
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM4 MOSFETS ---
Name:      mpass      m5      m4      m3      m7
Model:      pmos      pmos      pmos      nmos      nmos
Id:         -1.01e-02  -2.46e-05  -2.46e-05  4.94e-05  5.08e-05
Vgs:        -6.43e-01  -6.37e-01  -6.37e-01  6.44e-01  6.44e-01
Vds:        -3.87e-01  -6.43e-01  -6.37e-01  3.97e-01  1.01e+00
Vbs:         0.00e+00  0.00e+00  0.00e+00  0.00e+00  0.00e+00
Vth:        -4.87e-01  -4.84e-01  -4.84e-01  4.69e-01  4.69e-01
Vdsat:      -1.72e-01  -1.70e-01  -1.70e-01  1.81e-01  1.82e-01
Gm:          1.02e-01  2.56e-04  2.55e-04  4.34e-04  4.46e-04
Gds:         2.54e-03  5.07e-06  5.07e-06  3.41e-06  2.03e-06
Gmb:         2.16e-02  5.40e-05  5.39e-05  1.04e-04  1.07e-04
Cbd:         1.28e-13  3.03e-16  3.03e-16  5.60e-16  4.96e-16
Cbs:         2.29e-13  5.71e-16  5.71e-16  1.00e-15  1.00e-15

Name:      m2      m1      m8
Model:      nmos      nmos      nmos
Id:          2.46e-05  2.47e-05  5.00e-05
Vgs:          6.02e-01  6.03e-01  6.44e-01
Vds:          3.66e-01  3.60e-01  6.44e-01
Vbs:           0.00e+00  0.00e+00  0.00e+00
Vth:          4.66e-01  4.66e-01  4.69e-01
Vdsat:        1.44e-01  1.44e-01  1.82e-01
Gm:           2.40e-04  2.41e-04  4.40e-04
Gds:          4.94e-06  5.03e-06  2.21e-06
Gmb:          5.55e-05  5.56e-05  1.05e-04
Cbd:          1.25e-16  1.25e-16  5.30e-16
Cbs:          2.22e-16  2.22e-16  1.00e-15

Total elapsed time: 0.077 seconds.

```

Figure 50: Output<sub>log</sub> details

From the above file we can verify that all the devices are in saturation as follows:

## Transistor Operating Regions Table

This document provides a table summarizing the operating regions of several transistors based on their parameters.

Transistor	Type	$V_{ds}$ (V)	$V_{gs}/V_{sg}$ (V)	$V_t$ (V)	$V_{gs}/V_{sg} - V_t$ (V)	Operating Region
M1	NMOS	0.360	0.603	0.466	0.137	Saturation
M2	NMOS	0.366	0.602	0.466	0.136	Saturation
M3	NMOS	0.397	0.644	0.469	0.175	Saturation
M4	PMOS	0.637	0.637	0.484	0.153	Saturation
M5	PMOS	0.643	0.637	0.484	0.153	Saturation
MPass	PMOS	0.387	0.643	0.487	0.156	Saturation
M7	NMOS	1.01	0.644	0.469	0.173	Saturation
M8	NMOS	0.644	0.644	0.469	0.175	Saturation

Table 14: Transistor Parameters and Operating Regions

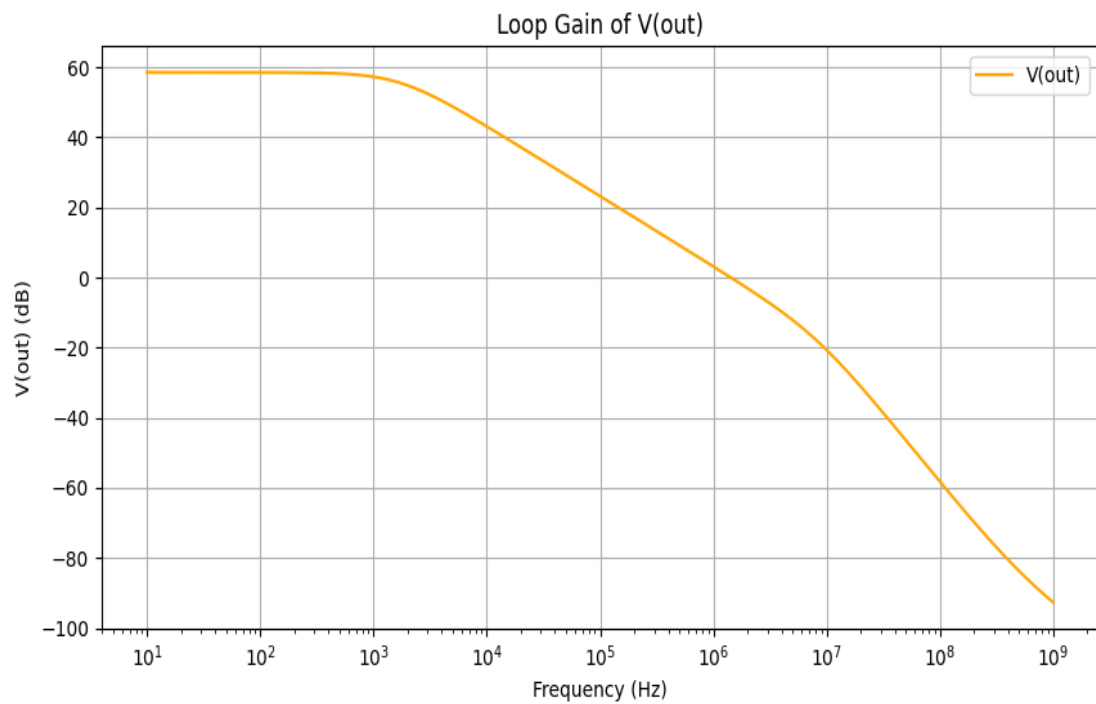
**Loop gain plots:-**

Figure 51: Loop gain of LDO

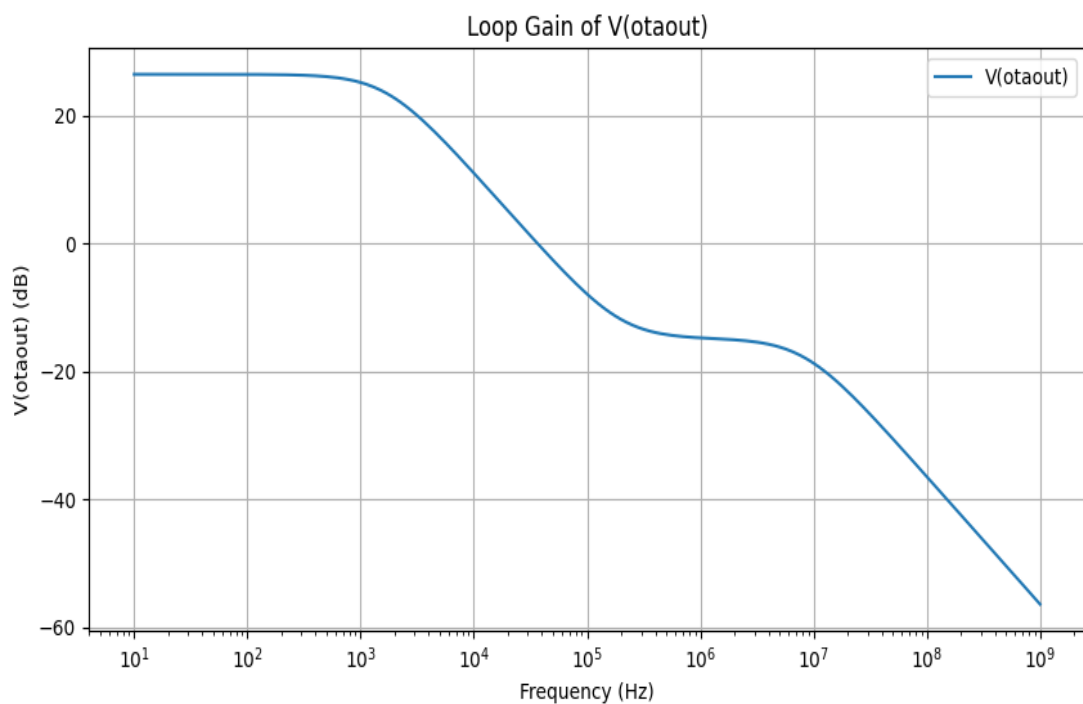


Figure 52: Loop gain of OTA

## Phase margin

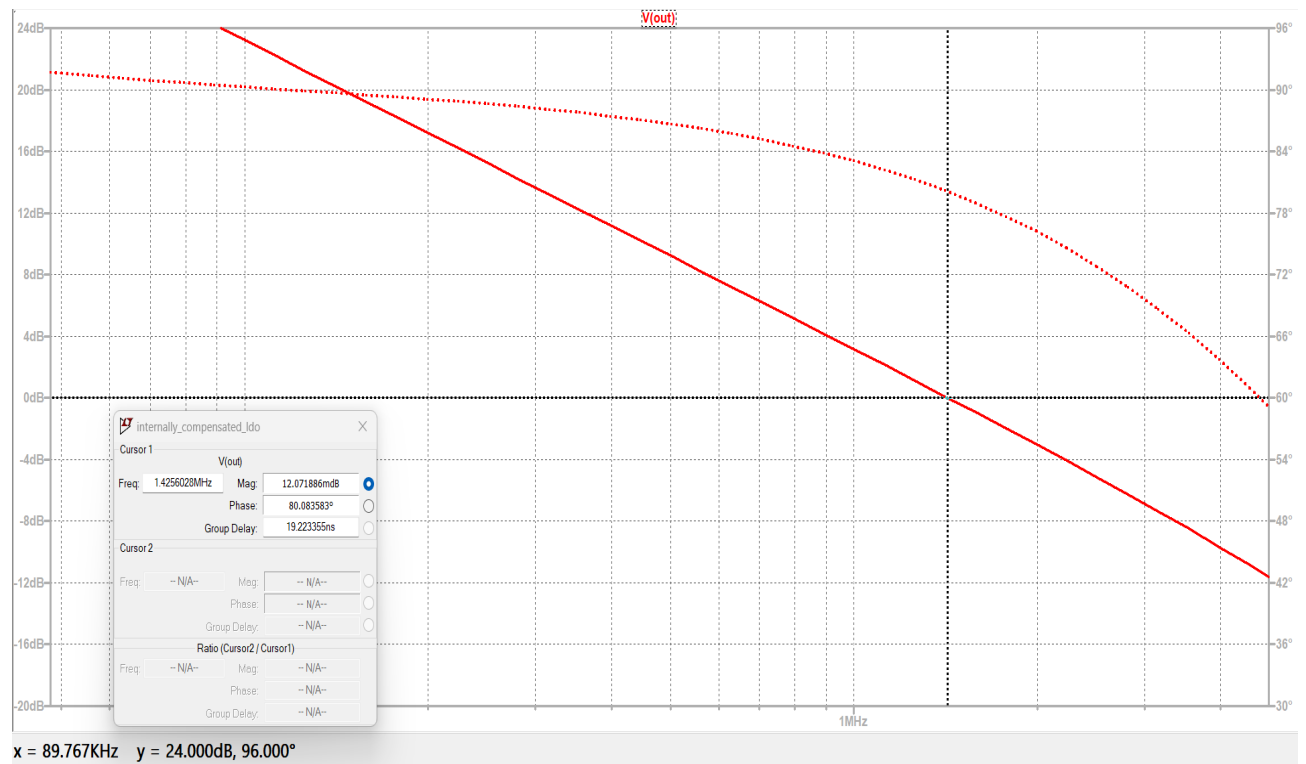


Figure 53: Phase Margin

### Case 2:- Open Loop PSRR calculation

## Schematic

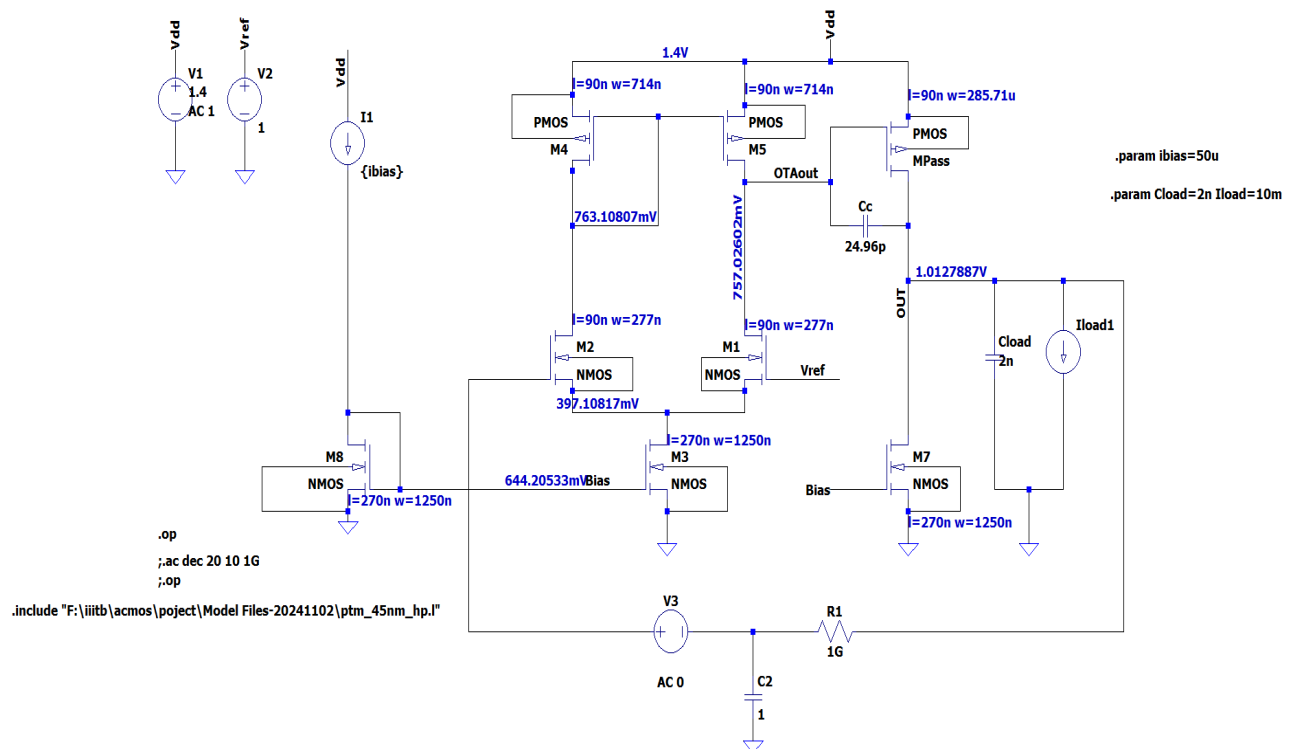


Figure 54: Schematic

Open loop psrr plots:-

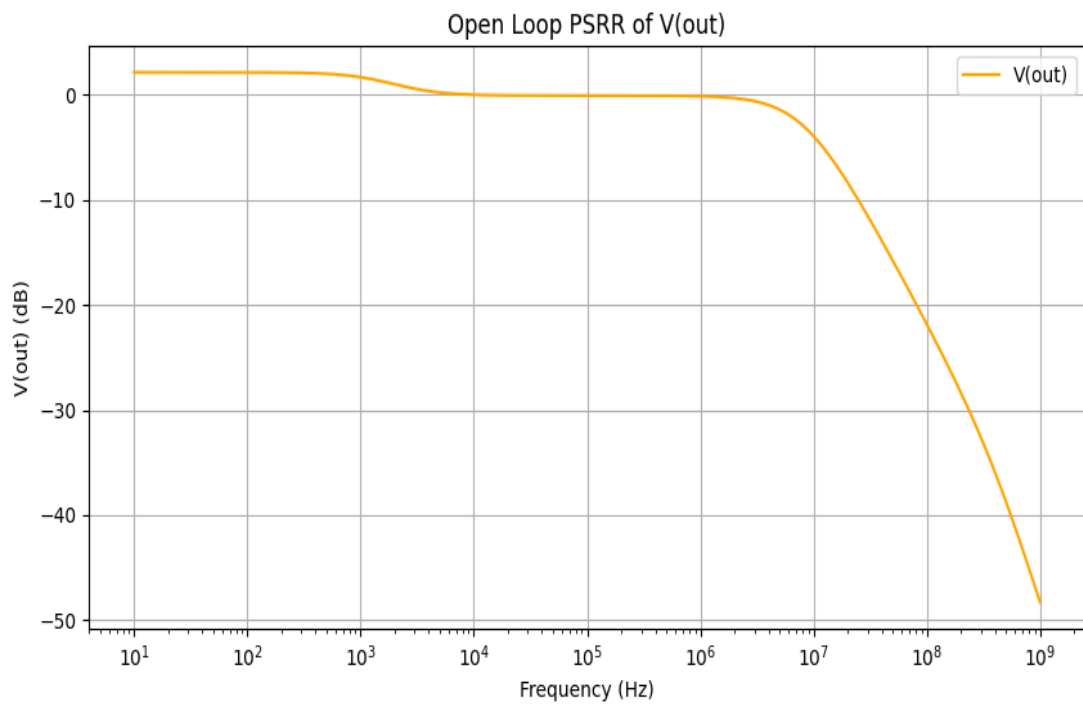


Figure 55: Open Loop PSRR of LDO

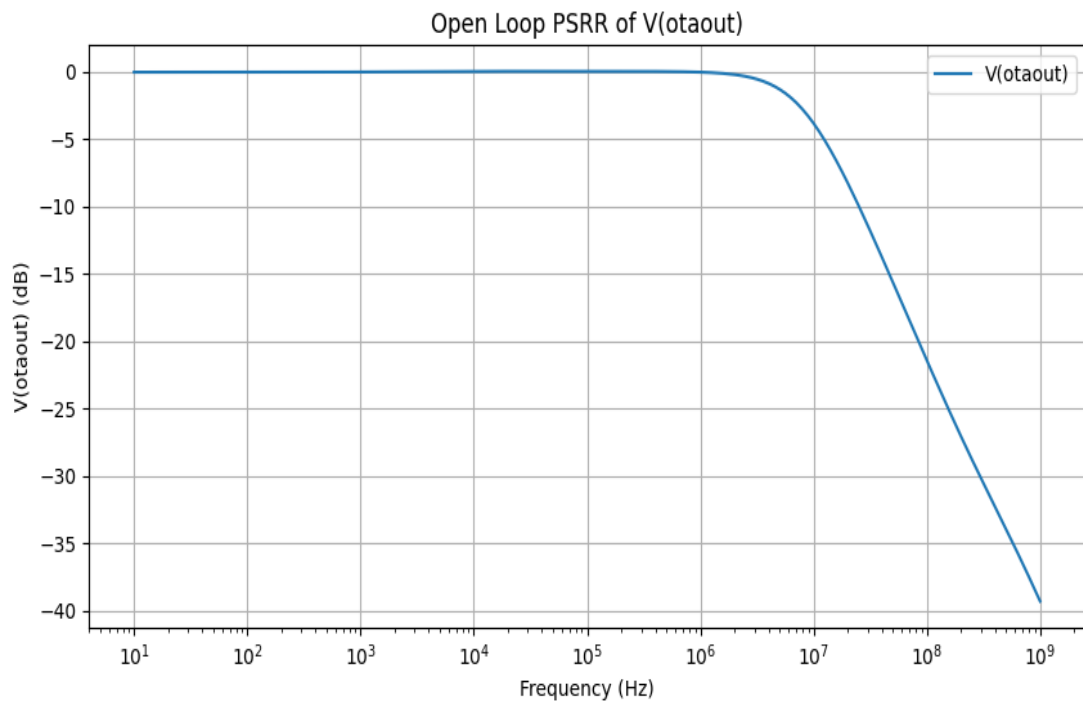


Figure 56: Open Loop PSRR of OTA



### Case 3:- Closed loop PSRR calculation

#### Schematic

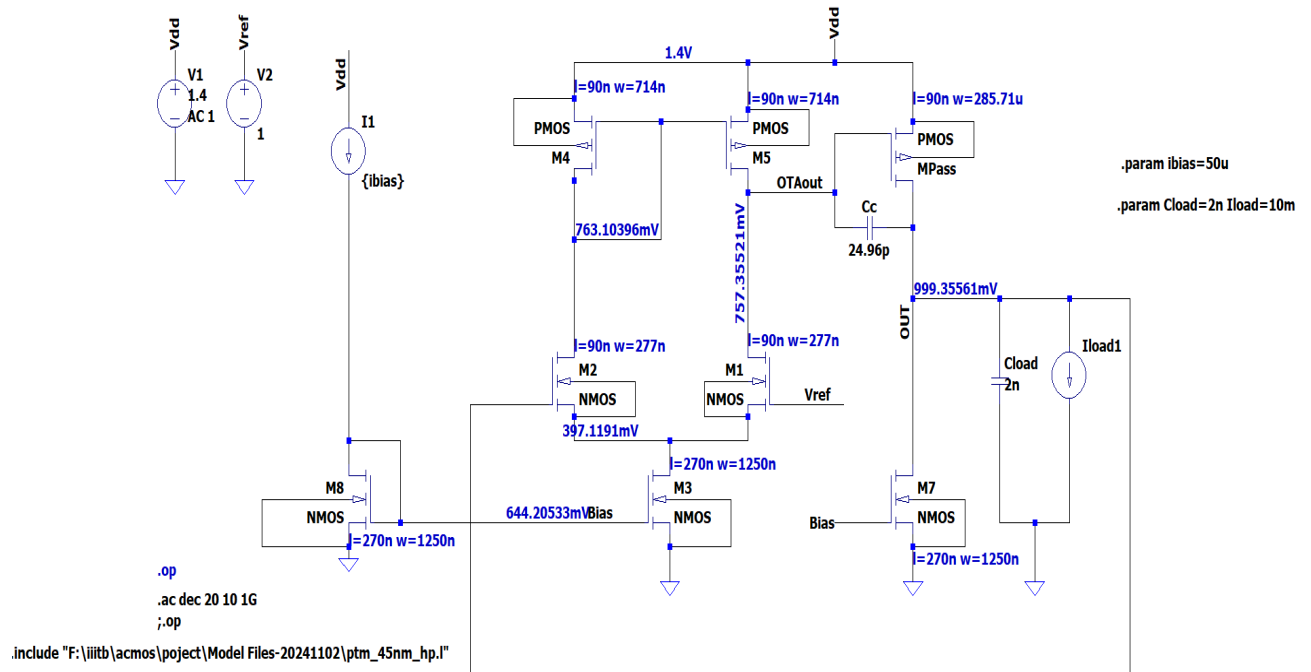


Figure 57: Schematic

C

lose loop psrr plots:-

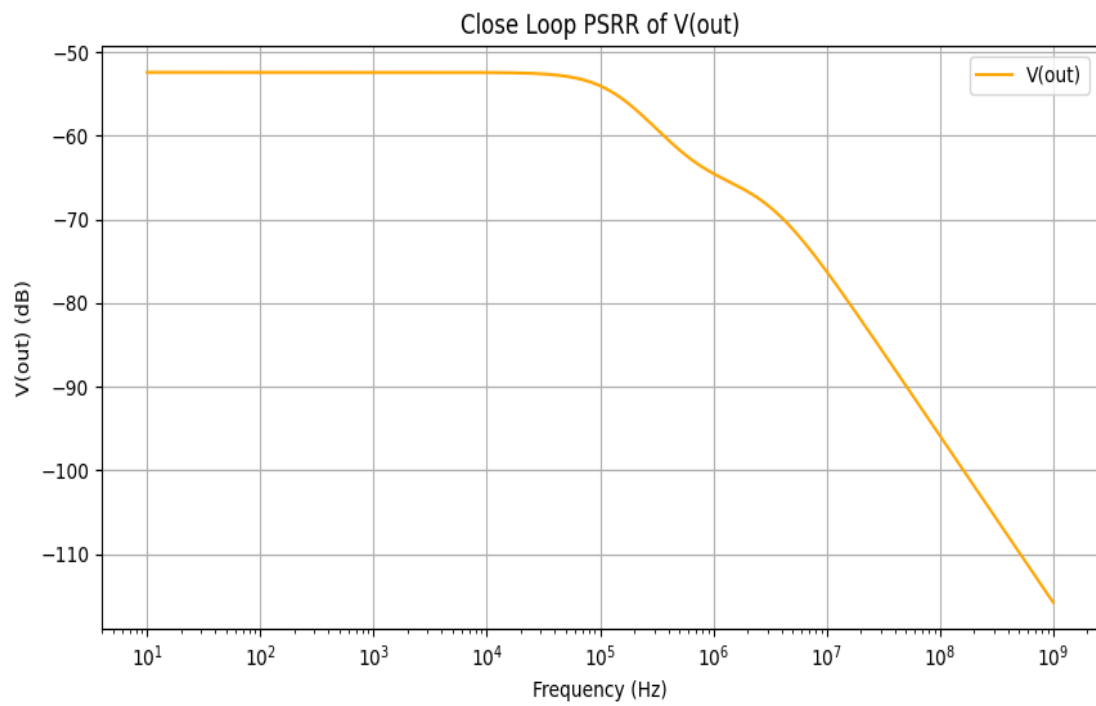


Figure 58: Close loop psrr of LDO

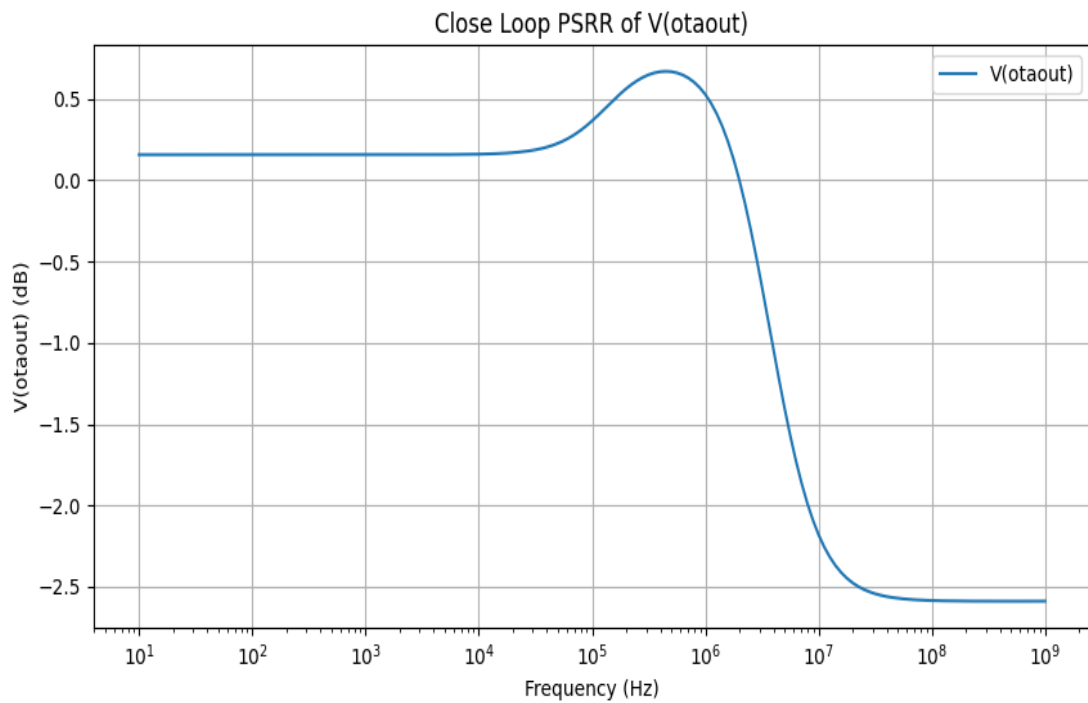


Figure 59: Close Loop PSRR of OTA

## Transient Analysis

### Schematic

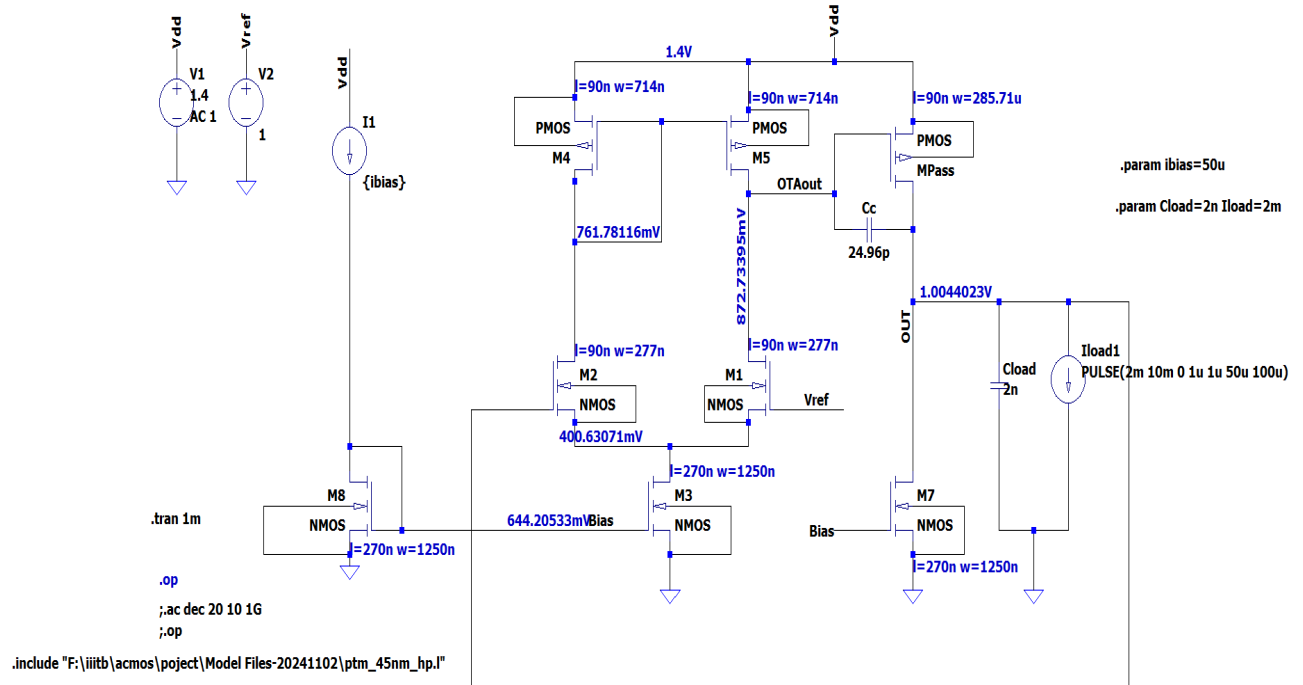


Figure 60: Schematic

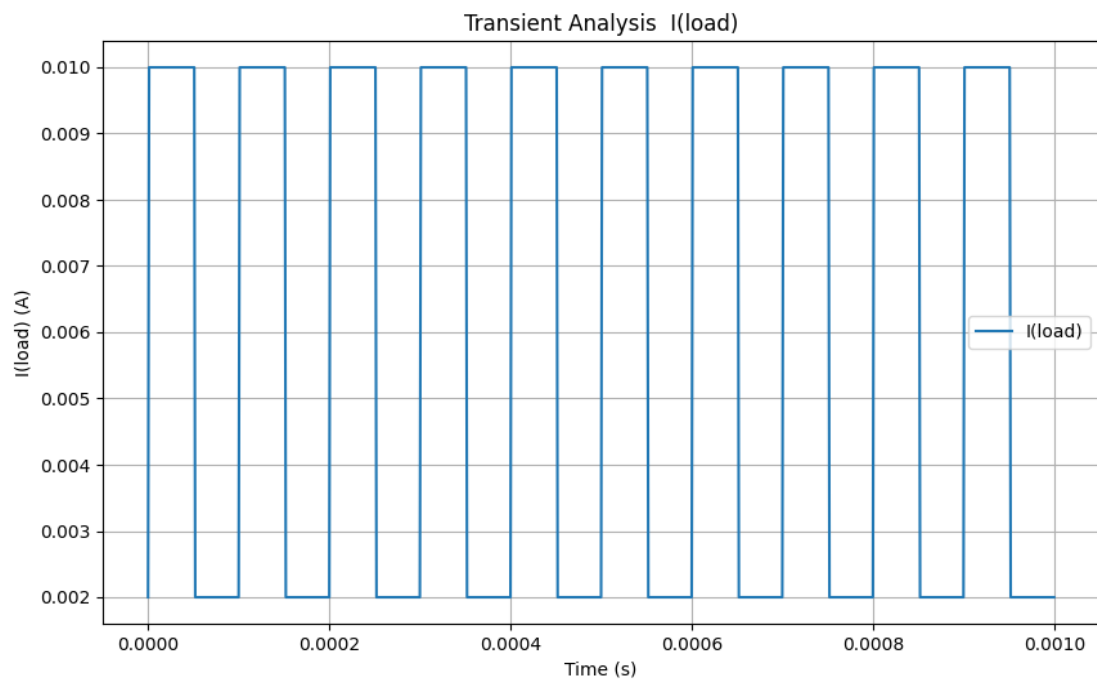
**Iload Vs Time**

Figure 61: Iload Vs Time

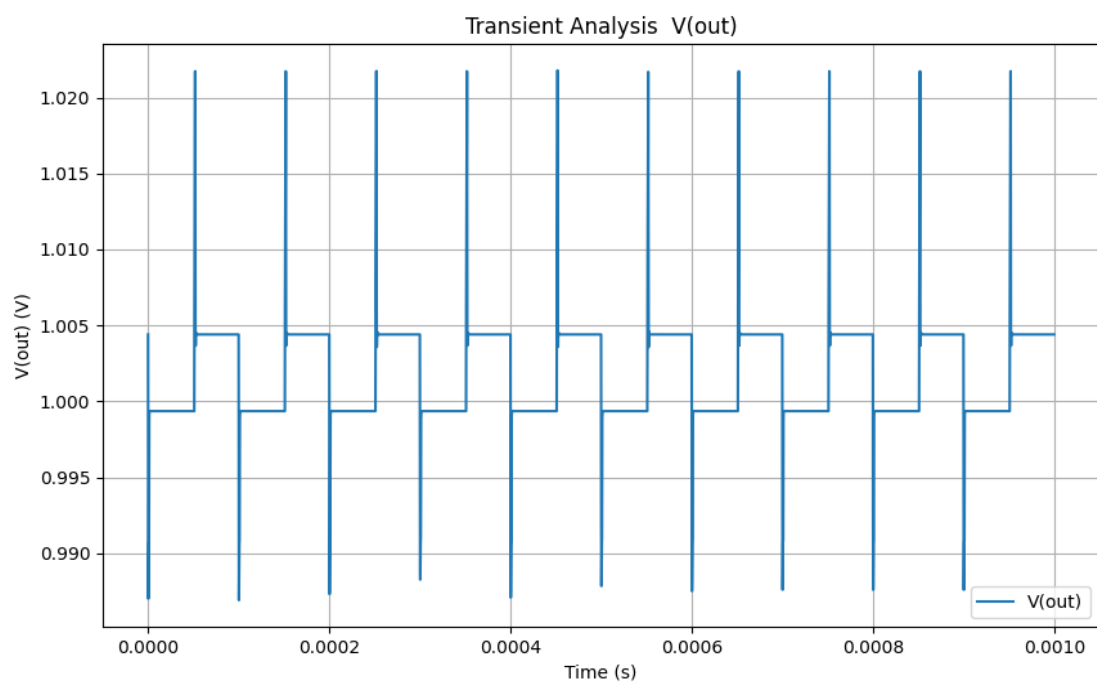
**Vout Vs Time**

Figure 62: Vout Vs Time

## Simulation vs. Hand Calculations

### For Passfet HEAVY LOAD

#### Hand Calculation

- $r_o = 500 \Omega$
- $g_m = 0.1 \text{ A/V}$
- $W_{p1}$  (first pole location) = 9.94k
- $g_m r_o = 50$
- $C_{gg} = 0.569p$
- $C_l = 2n$
- $C_c = 24.96p$

#### Simulation Results from SPICE Error Log:

- $r_o = 1/g_{ds} = 393 \Omega$
- $g_m = 0.102 \text{ A/V}$
- $W_{p1}$  (first pole location) = 10.04k
- $g_m r_o = 40.086$

Table 15: Hand Calculation vs Simulation Results

Parameter	Hand Calculation	Simulation Result	% Difference
$r_o$ (ohm)	500.00	390	22.0%
$g_m$ (A/V)	0.1	0.102	1.9%
$g_m * r_o$	50	40.15	19.7%
$W_{p1}$ (Hz)	9.94k	10.04k	1.01%
$W_{p2}$ (Hz)	50M	51M	1.9%
$W_{ugb}$ (Hz)	9.94M	10.04M	1.01%
$r_{odiff}$ (ohm)	80k	98.619k	57.8%
$g_{mdiff}$ (A/V)	250u	256u	2.4%

max width=								
Name	mpass	m5	m4	m3	m7	m2	m1	m8
Model	pmos	pmos	pmos	nmos	nmos	nmos	nmos	nmos
<b>Id</b>	-1.01E-02	-2.46E-05	-2.46E-05	4.94E-05	5.08E-05	2.46E-05	2.47E-05	5.00E-05
<b>Vgs</b>	-6.43E-01	-6.37E-01	-6.37E-01	6.44E-01	6.44E-01	6.02E-01	6.03E-01	6.44E-01
<b>Vds</b>	-3.87E-01	-6.43E-01	-6.37E-01	3.97E-01	1.01E+00	3.66E-01	3.60E-01	6.44E-01
<b>Vbs</b>	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
<b>Vth</b>	-4.87E-01	-4.84E-01	-4.84E-01	4.69E-01	4.69E-01	4.66E-01	4.66E-01	4.69E-01
<b>Vdsat</b>	-1.72E-01	-1.70E-01	-1.70E-01	1.81E-01	1.82E-01	1.44E-01	1.44E-01	1.82E-01
<b>Gm</b>	1.02E-01	2.56E-04	2.55E-04	4.34E-04	4.46E-04	2.40E-04	2.41E-04	4.40E-04
<b>Gds</b>	2.54E-03	5.07E-06	5.07E-06	3.41E-06	2.03E-06	4.94E-06	5.03E-06	2.21E-06
<b>Gmb</b>	2.16E-02	5.40E-05	5.39E-05	1.04E-04	1.07E-04	5.55E-05	5.56E-05	1.05E-04
<b>Cbd</b>	1.28E-13	3.03E-16	3.03E-16	5.60E-16	4.96E-16	1.25E-16	1.25E-16	5.30E-16
<b>Cbs</b>	2.29E-13	5.71E-16	5.71E-16	1.00E-15	1.00E-15	2.22E-16	2.22E-16	1.00E-15
<b>ro</b>	3.94E+02	1.97E+05	1.97E+05	2.93E+05	4.93E+05	2.02E+05	1.99E+05	4.52E+05
<b>gm*ro</b>	4.02E+01	5.05E+01	5.03E+01	1.27E+02	2.20E+02	4.86E+01	4.79E+01	1.99E+02

Table 16: Transistor Parameter Table

## For Passfet LIGHT LOAD

### Hand Calculation

- $r_o = 2500 \Omega$
- $g_m = 0.02 \text{ A/V}$
- $W_{p1}$  (first pole location) = 10k
- $g_m r_o = 50$
- $C_{gg} = 0.1136p$
- $C_l = 2n$
- $C_c = 24.96p$

### Simulation Results from SPICE Error Log:

- $r_o = 1/g_{ds} = 1503.7 \Omega$
- $g_m = 0.0364 \text{ A/V}$
- $W_{p1}$  (first pole location) = 7.01k
- $g_m r_o = 54.7$

Table 17: Hand Calculation vs Simulation Results

Parameter	Hand Calculation	Simulation Result	% Difference
$r_o$ (ohm)	2500.00	1503.7	39.0%
$g_m$ (A/V)	0.02	0.0364	45%
$g_m * r_o$	50	54.7	8.5%
$W_{p1}$ (Hz)	10k	7.70k	23%
$W_{p2}$ (Hz)	10M	18.2M	45.05%
$W_{ugb}$ (Hz)	10M	7.70M	23 %
$r_{odiff}$ (ohm)	80k	104.24k	23.07%
$g_{mdiff}$ (A/V)	250u	253u	1.185%

max width=								
Name	mpass	m5	m4	m3	m7	m2	m1	m8
Model	pmos	pmos	pmos	nmos	nmos	nmos	nmos	nmos
<b>Id</b>	-2.05E-03	-2.44E-05	-2.50E-05	4.94E-05	5.08E-05	2.50E-05	2.44E-05	5.00E-05
<b>Vgs</b>	-5.28E-01	-6.38E-01	-6.38E-01	6.44E-01	6.44E-01	6.04E-01	5.99E-01	6.44E-01
<b>Vds</b>	-3.82E-01	-5.28E-01	-6.38E-01	4.01E-01	1.02E+00	3.61E-01	4.72E-01	6.44E-01
<b>Vbs</b>	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
<b>Vth</b>	-4.87E-01	-4.86E-01	-4.84E-01	4.69E-01	4.69E-01	4.66E-01	4.65E-01	4.69E-01
<b>Vdsat</b>	-9.28E-02	-1.70E-01	-1.71E-01	1.81E-01	1.82E-01	1.45E-01	1.43E-01	1.82E-01
<b>Gm</b>	3.64E-02	2.53E-04	2.57E-04	4.34E-04	4.46E-04	2.42E-04	2.41E-04	4.40E-04
<b>Gds</b>	6.65E-04	5.30E-06	5.12E-06	3.36E-06	2.03E-06	5.06E-06	4.27E-06	2.21E-06
<b>Gmb</b>	7.50E-03	5.34E-05	5.43E-05	1.04E-04	1.07E-04	5.58E-05	5.56E-05	1.05E-04
<b>Cbd</b>	1.28E-13	3.10E-16	3.03E-16	5.59E-16	4.96E-16	1.25E-16	1.22E-16	5.30E-16
<b>Cbs</b>	2.29E-13	5.71E-16	5.71E-16	1.00E-15	1.00E-15	2.22E-16	2.22E-16	1.00E-15
<b>ro</b>	1.50E+03	1.89E+05	1.95E+05	2.98E+05	4.93E+05	1.98E+05	2.34E+05	4.52E+05
<b>gm*ro</b>	5.47E+01	4.77E+01	5.02E+01	1.29E+02	2.20E+02	4.78E+01	5.64E+01	1.99E+02

Table 18: Transistor Parameter Table



## Stability Analysis

For Heavy load we get the following curve:

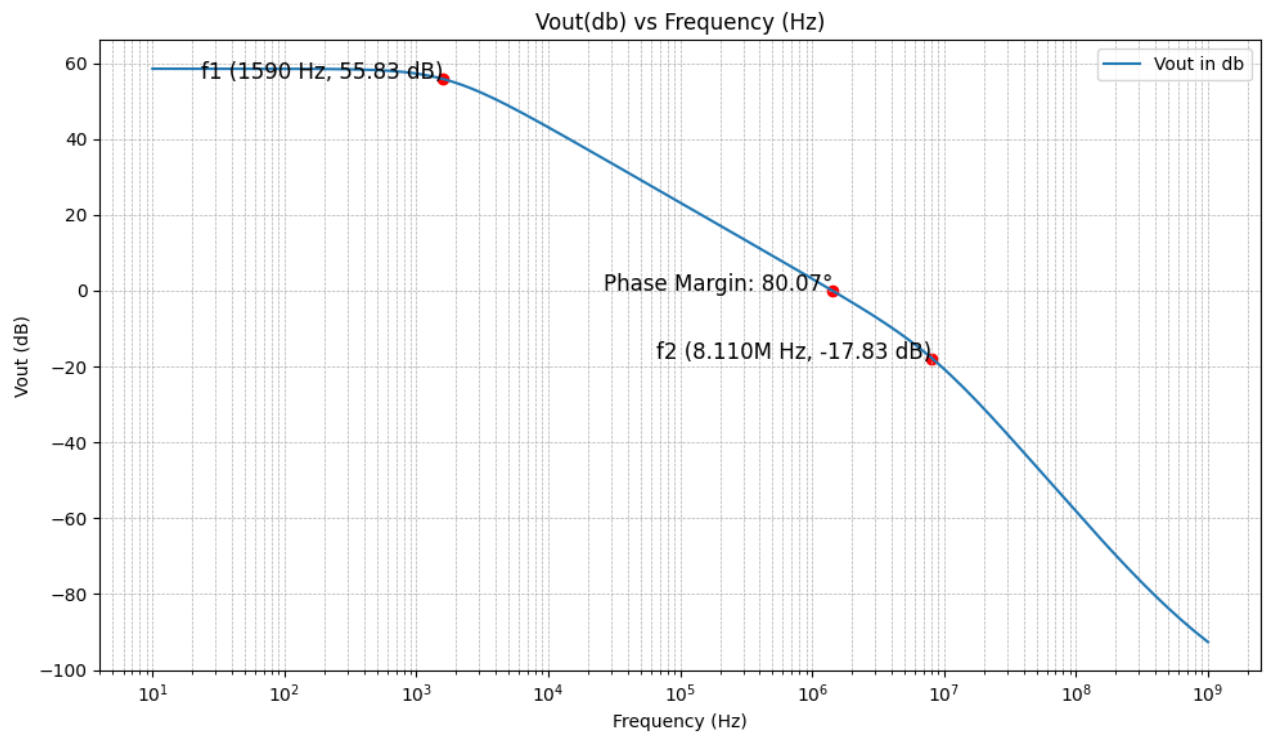


Figure 63: Pole representation

For Light load we get the following curve

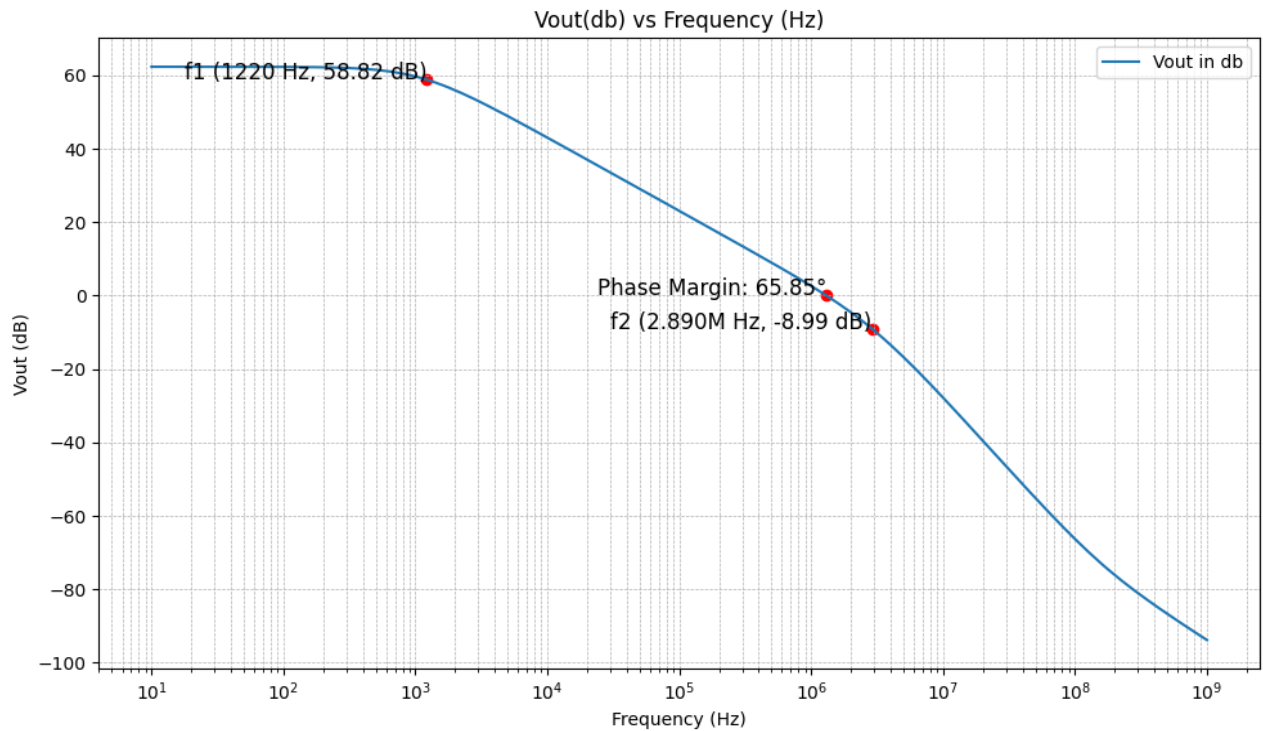


Figure 64: Pole representation

From the above analysis we can see that the unity gain bandwidth is closer to the second pole for the light load case than the heavy load case. From the phase margin also we observe a better phase margin of 80.07 degrees for the heavy load case. From this analysis, we can say that we get a more stable system when we apply heavy load.